



**EE 220**



# Operational Amplifiers

# Operational Amplifiers (Op Amps)

1. Op Amp Characteristics
2. Ideal Op Amp
3. Inverting Amplifier
4. Non-Inverting Amplifier
5. Summing Amplifier
6. Difference Amplifier
7. Voltage Follower
8. Cascaded Op Amps
9. MOSFET

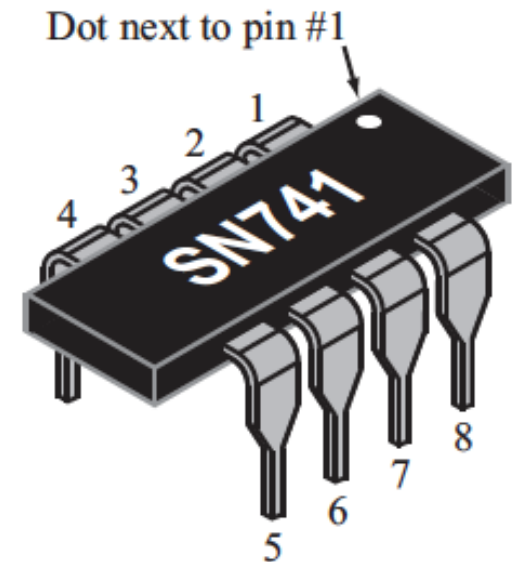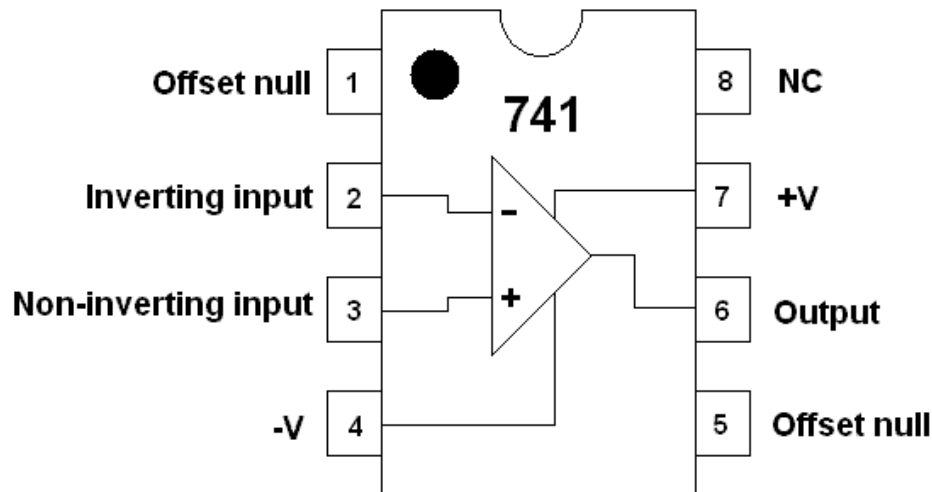
# What is an Op Amp?

- It is an electronic circuit that behaves like a **voltage-controlled voltage source**.
- It is often used to perform mathematical operations such as *inversion*, *addition*, *subtraction*, *multiplication*, *division*, *differentiation* and *integration*.




# Inside The Op Amp

## Schematic Diagram

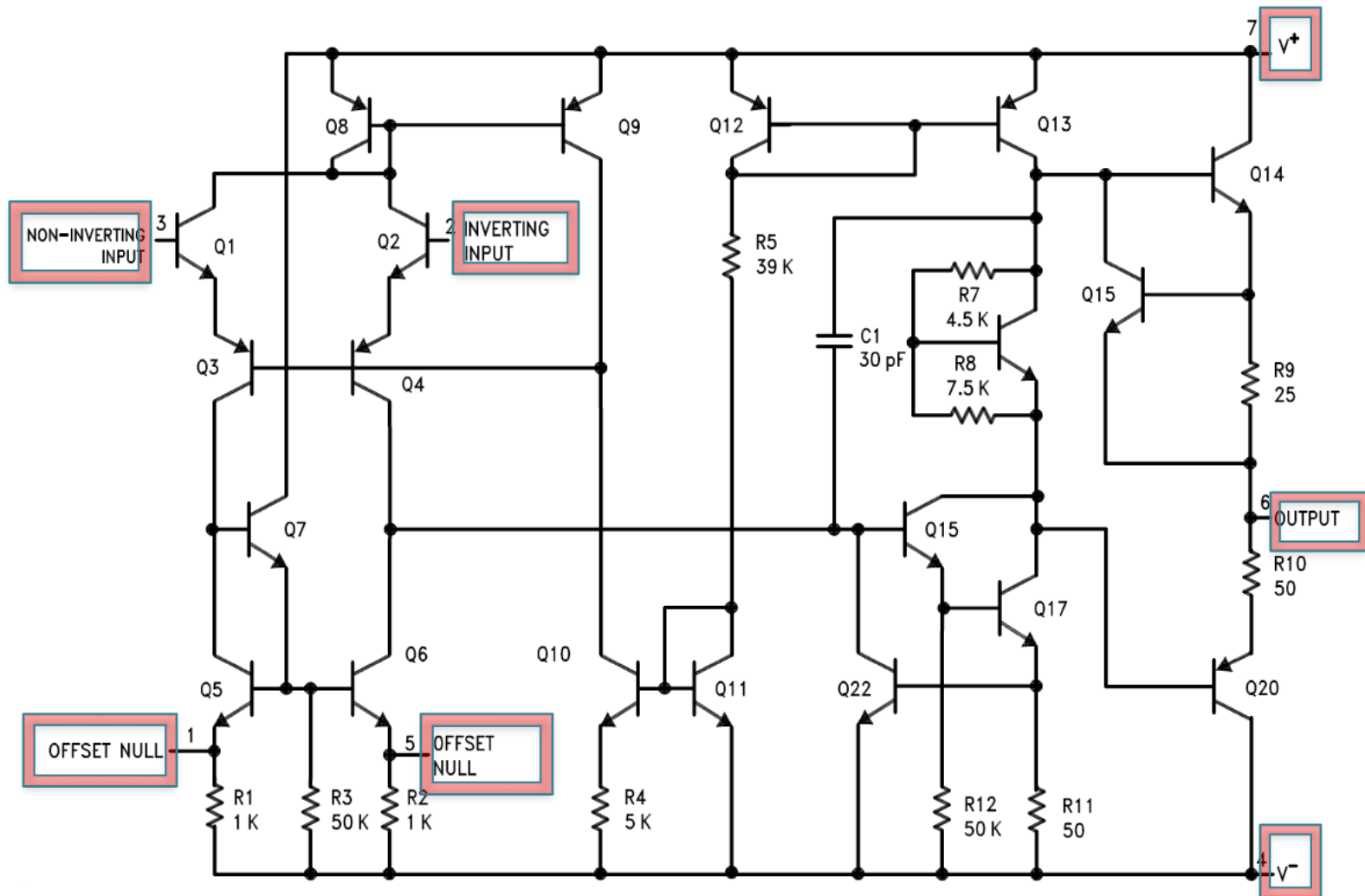

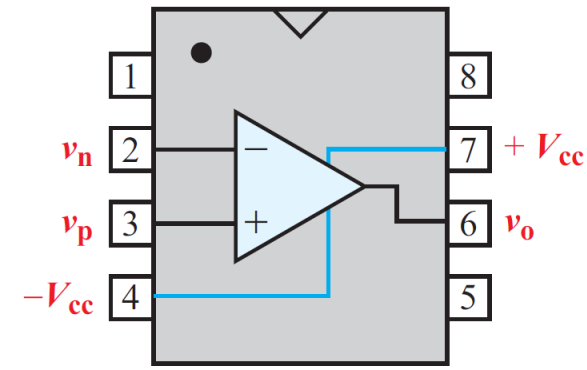
# Operational Amplifier

- Two input terminals, positive (non-inverting) and negative (inverting)
- One output
- Power supply  $+V_{cc}$  and  $-V_{cc}$




(b) Pin diagram

Op Amp showing power supply

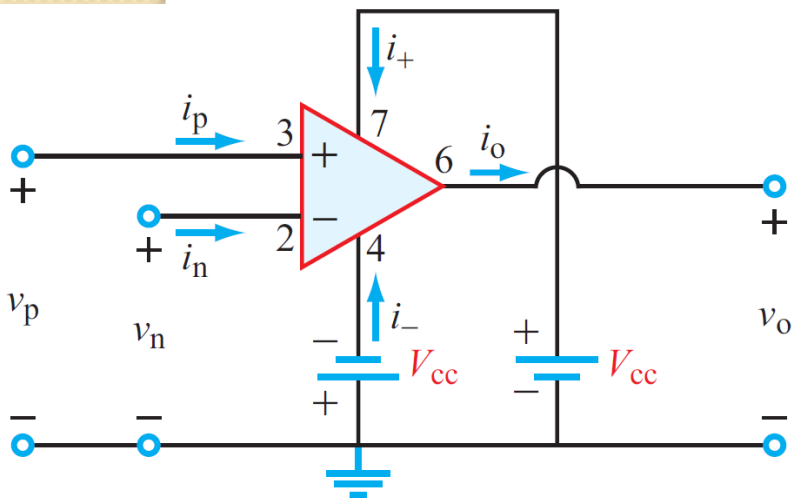

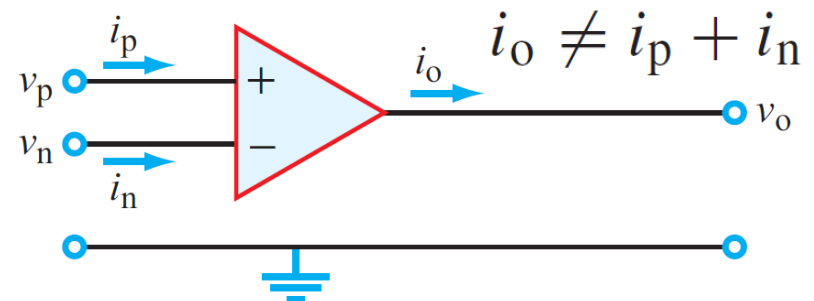Op Amp with power supply not shown (which is how we usually display op amp circuits)





# Op Amp Gain


- Key important aspect of op amp: **high voltage gain** output,

$$v_o = A(v_p - v_n)$$

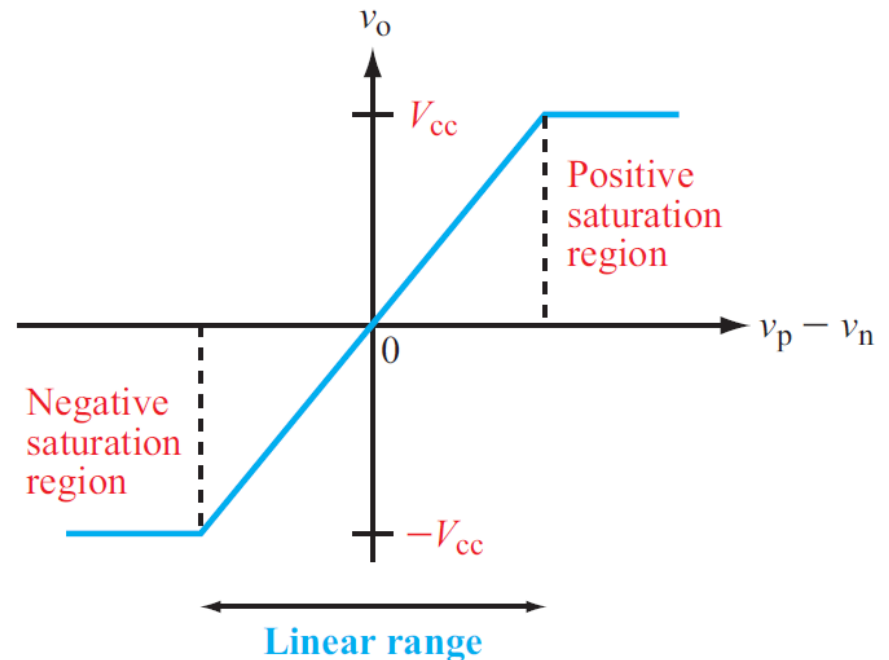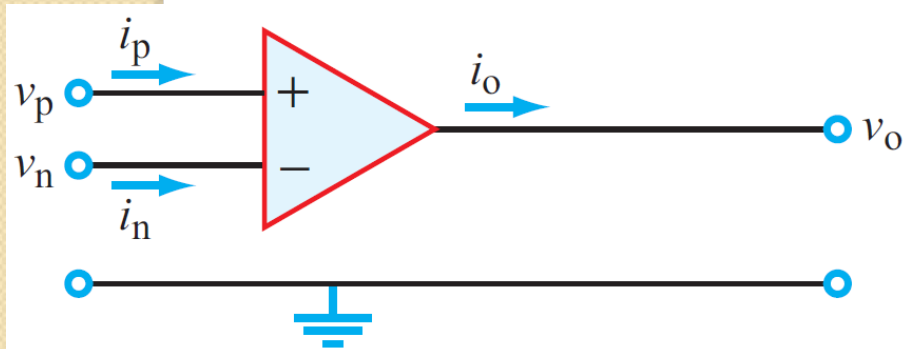- A is the **op-amp gain** (or open-loop gain)
- Linear response




# Op Amp Equivalent Circuit

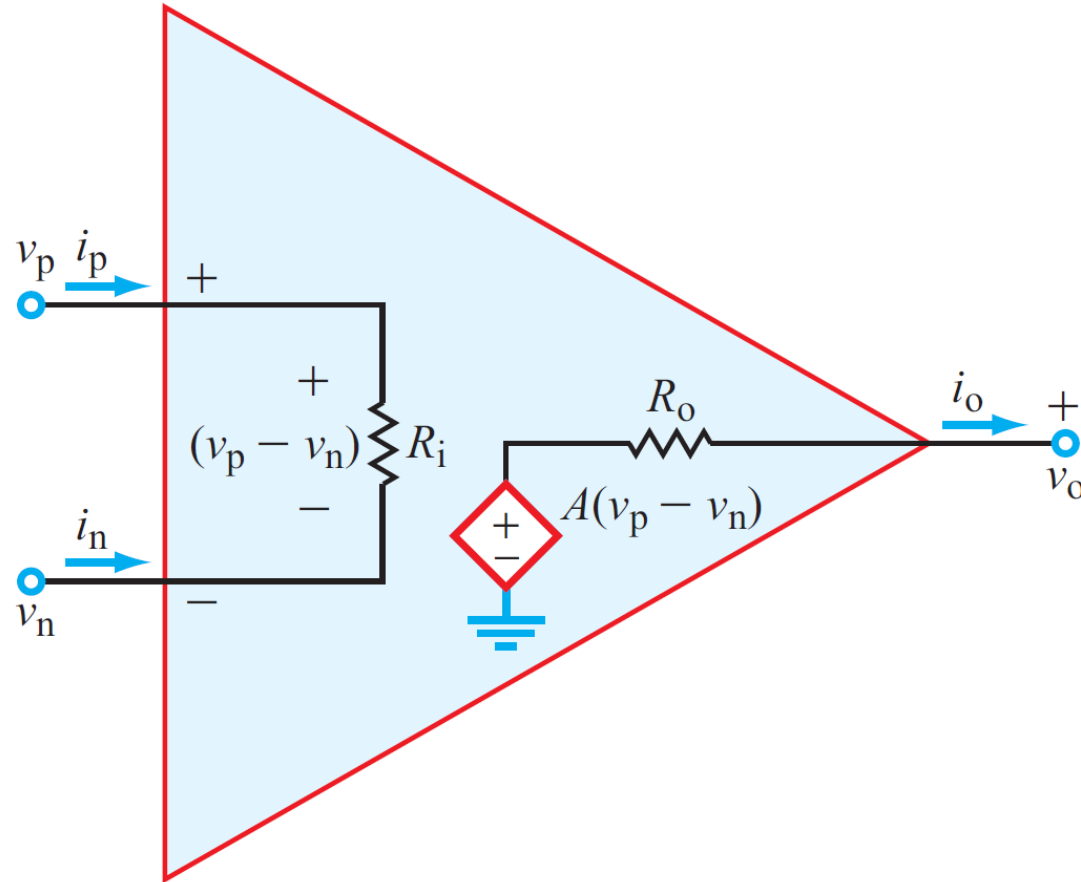

Op-Amp Characteristics	Parameter	Typical Range	Ideal Op Amp
• Linear input–output response	Open-loop gain $A$	$10^4$ to $10^8$ (V/V)	$\infty$
• High input resistance	Input resistance $R_i$	$10^6$ to $10^{13} \Omega$	$\infty \Omega$
• Low output resistance	Output resistance $R_o$	1 to $100 \Omega$	$0 \Omega$
• Very high gain	Supply voltage $V_{cc}$	5 to 24 V	As specified by manufacturer

# Circuit Analysis With Ideal Op-Amps

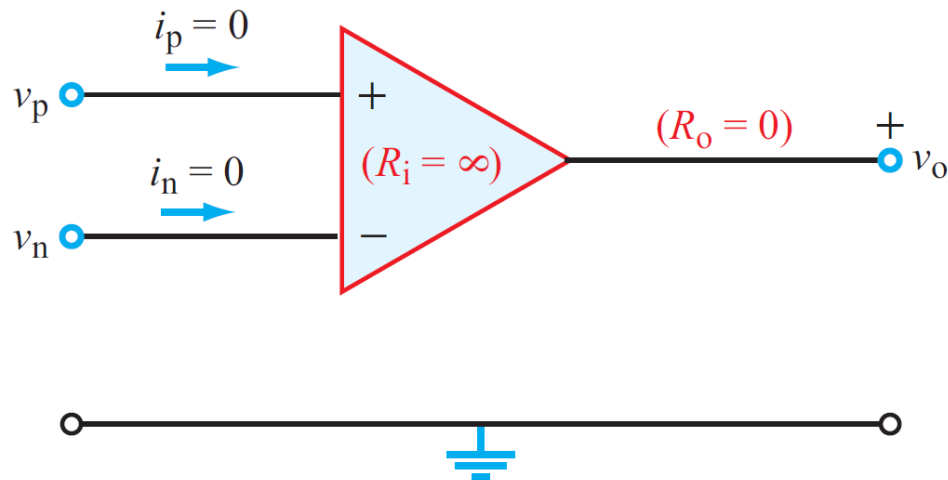

## Ideal Op Amp


- Current constraint  $i_p = i_n = 0$
- Voltage constraint  $v_p = v_n$
- $A = \infty$     $R_i = \infty$     $R_o = 0$

- Use nodal analysis as before.
- $v_p = v_n$  (Ideal op-amp model).
- $i_p = i_n = 0$  (Ideal op-amp model).
- Do not apply KCL at op amp output



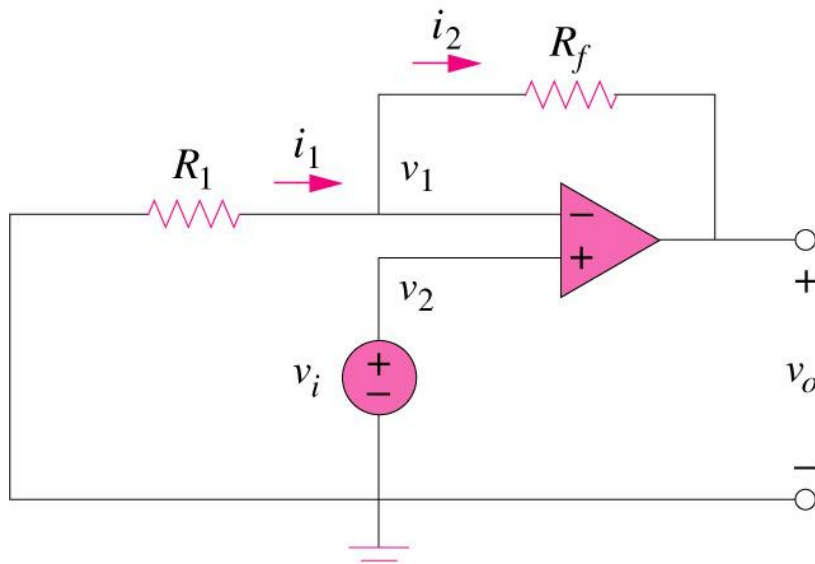
# Non-Inverting Amplifier

- Non-inverting amplifier is designed to produce positive voltage gain.


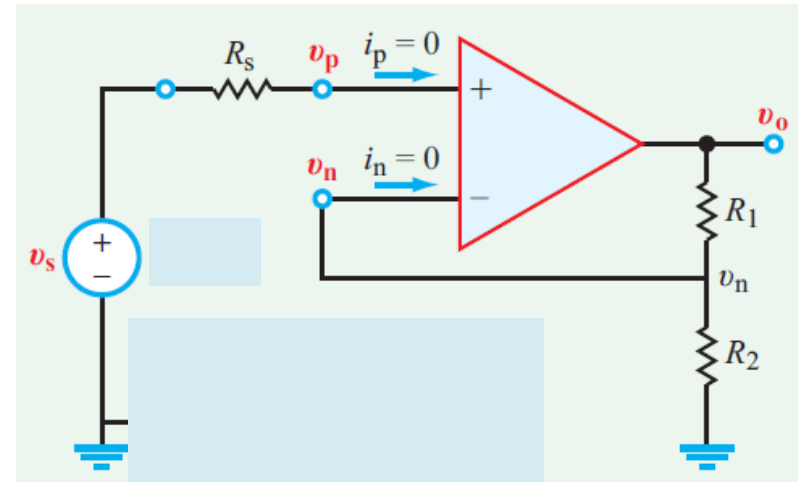
$$v_o = \left( 1 + \frac{R_f}{R_1} \right) v_{in}$$




$$V_o = (1 + R_1/R_2) v_s$$

# Non-Inverting Amplifier
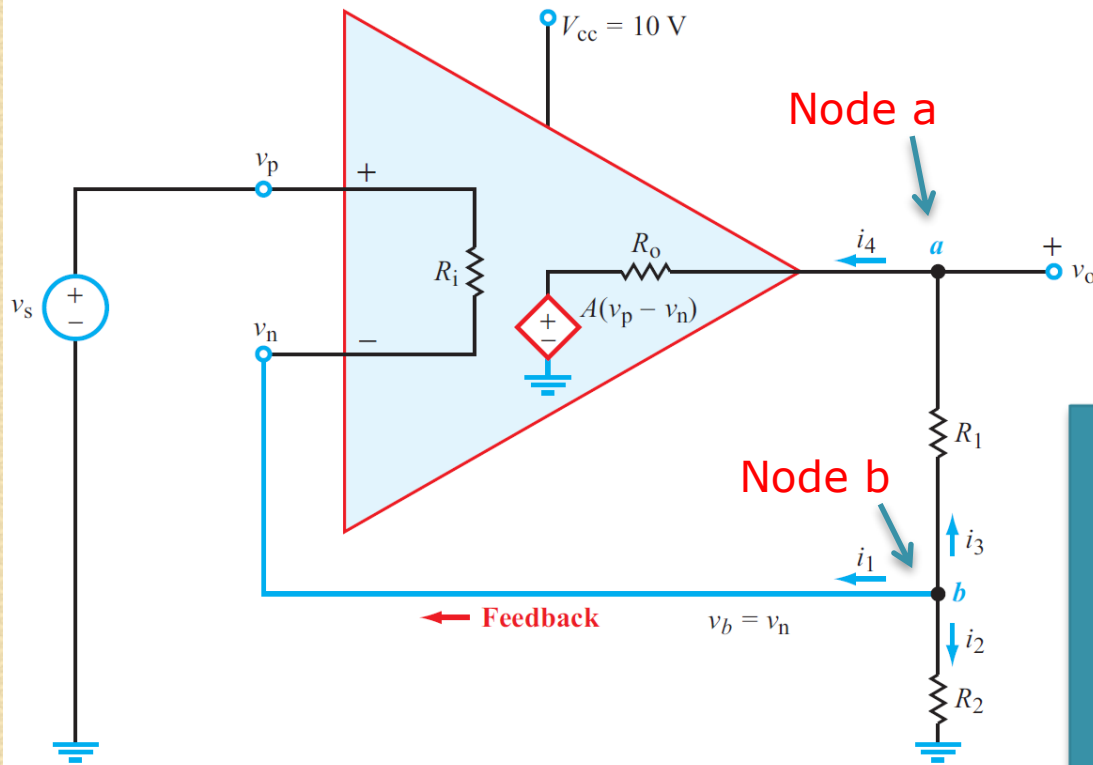
## Example 1:

For  $V_{cc} = 10 \text{ V}$ ,  $A = 10^6$ ,  $R_i = 10^7 \Omega$ ,  $R_o = 10 \Omega$ ,  
 $R_1 = 80 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ ,



**KCL at Node a:**

$$\frac{v_n - v_o}{R_1} = \frac{v_o - A(v_p - v_n)}{R_o}$$

**KCL at Node b:**

$$\frac{v_n - v_p}{R_i} + \frac{v_n}{R_2} + \frac{v_n - v_o}{R_1} = 0$$


**For infinite A:**

$$G = \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_2} = 5$$

$$G = \frac{v_o}{v_s} = \frac{[AR_i(R_1 + R_2) + R_2R_o]}{AR_2R_i + R_o(R_2 + R_i) + R_1R_2 + R_i(R_1 + R_2)} = 4.999975$$
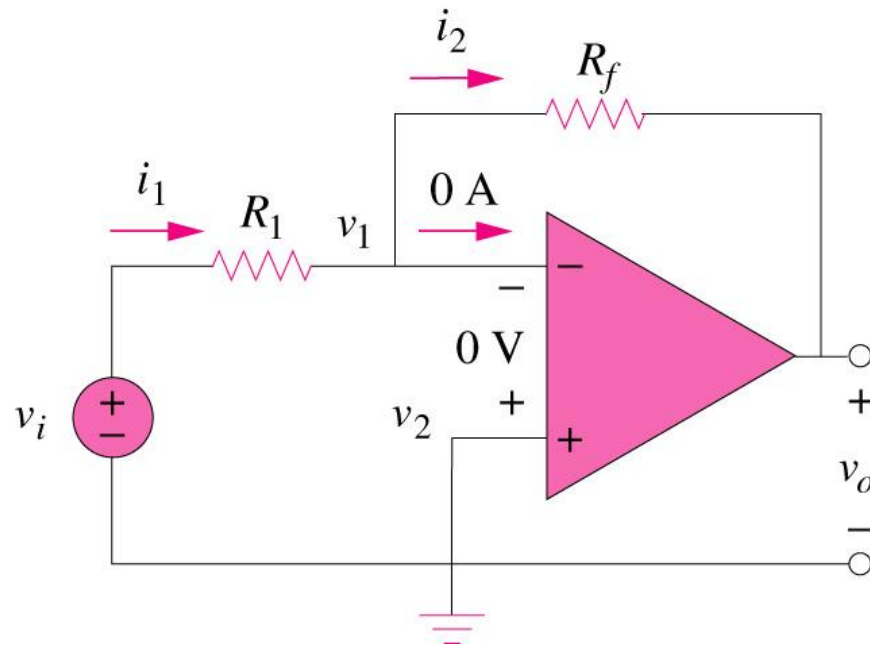
# Inverting Amplifier

- An inverting amplifier reverses the polarity of the input signal while amplifying it.




$$v_o = -\frac{R_f}{R_1} v_i$$

# Inverting Amplifier
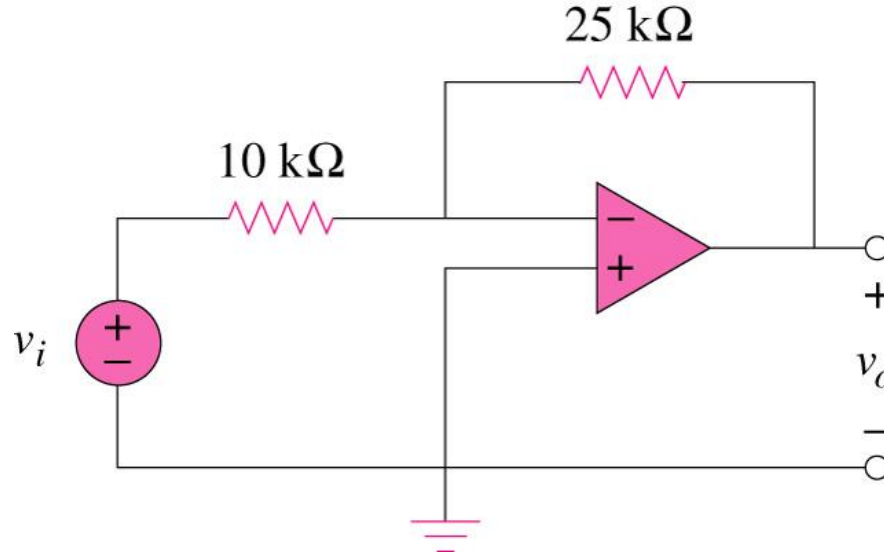
## Example 2:


Refer to the op amp circuit below. If  $v_i = 0.5\text{V}$ , calculate the output voltage  $v_o$  and the current in the  $10\text{ k}\Omega$  resistor.



Answer: (a)  $-1.25\text{V}$ ; (b)  $50\mu\text{A}$
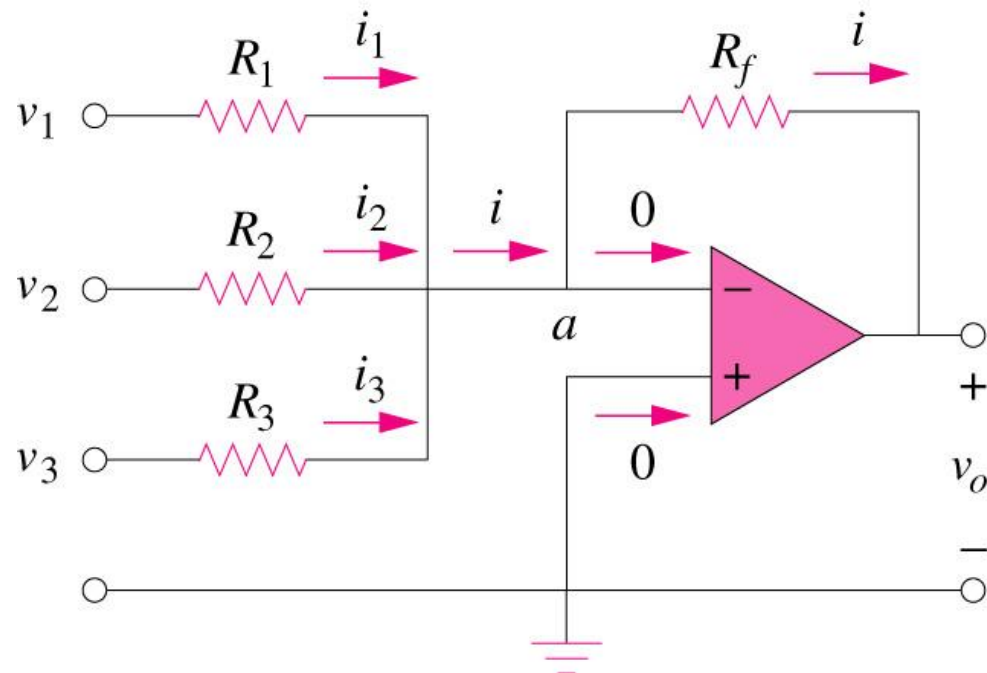
# Summing Amplifier

- Summing Amplifier is an op amp circuit that combines several inputs and produces an output that is equal to the weighted sum of the inputs.




$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$

# Summing Amplifier
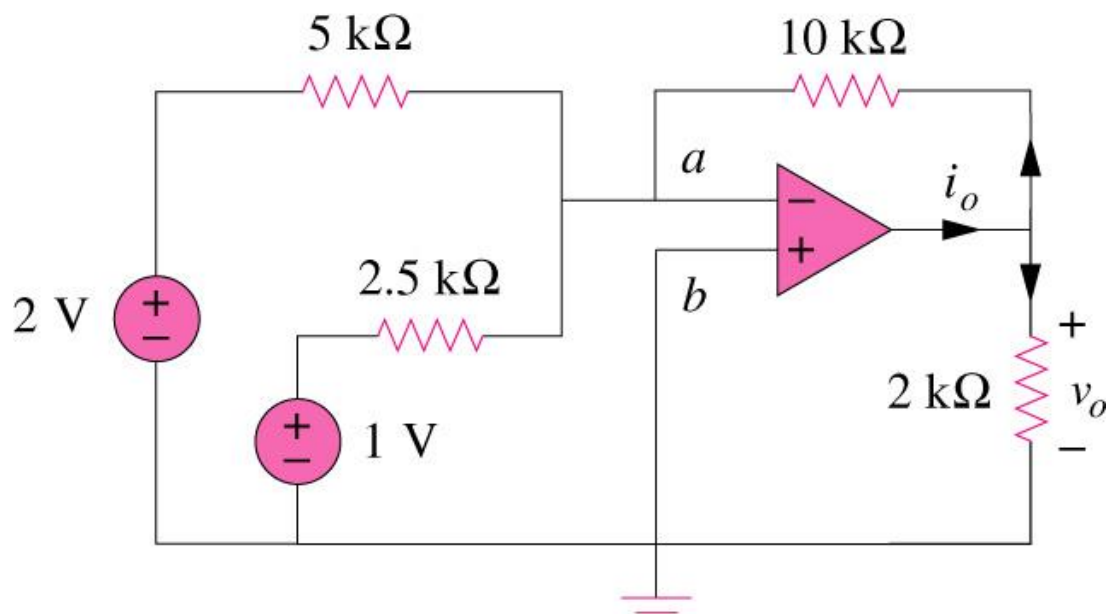
## Example 3:


Calculate  $v_o$  and  $i_o$  in the op amp circuit shown below.



Answer: -3.8V, -1.425mA
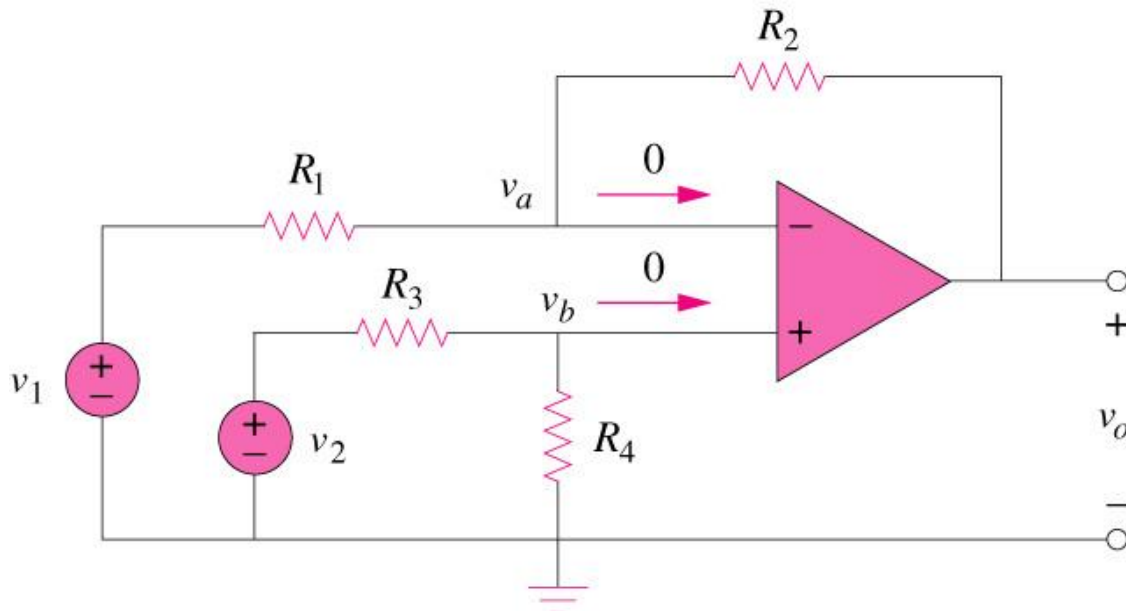
# Difference Amplifier

- Difference amplifier is a device that amplifies the difference between two weighted inputs.



$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1 \Rightarrow v_o = v_2 - v_1, \text{ if } \frac{R_2}{R_1} = \frac{R_3}{R_4} = 1$$




# Voltage Follower/Buffer



$$v_o = \frac{v_s R_L}{R_s + R_L} \quad (\text{without voltage follower})$$

$v_o$  depends on load resistor.

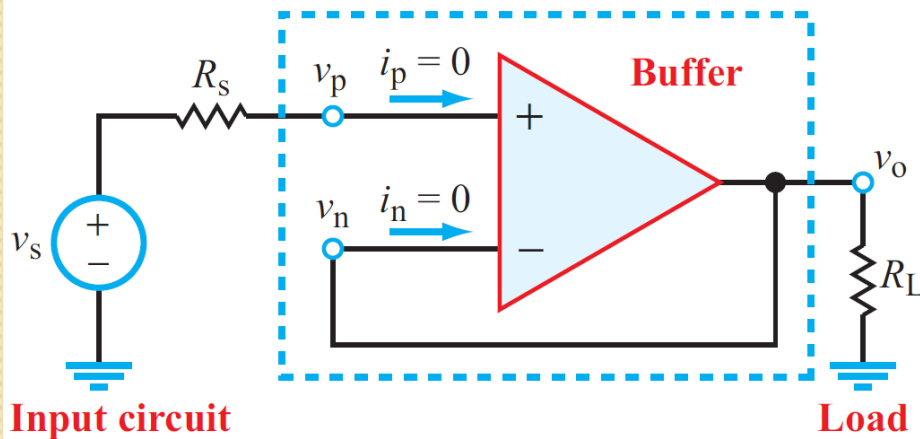


$$v_o = v_p = v_s \quad (\text{with voltage follower})$$

$v_o$  is immune to load resistor.


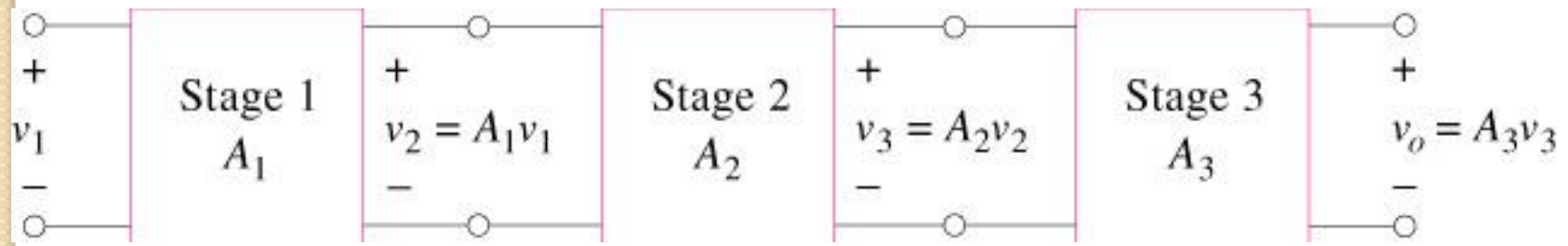
# Cascaded Op Amps


- It is a head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next.



# Cascaded Op Amps
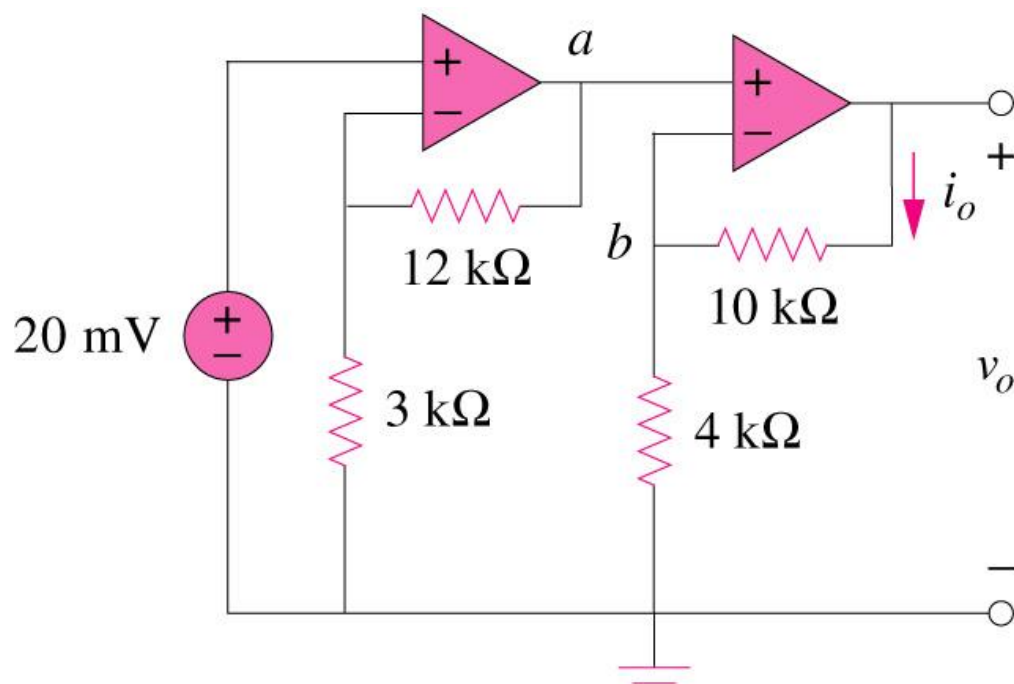
## Example 4:

Find  $v_o$  and  $i_o$  in the circuit shown below.




Answer: 350mV, 25μA

# Cascaded Op Amps
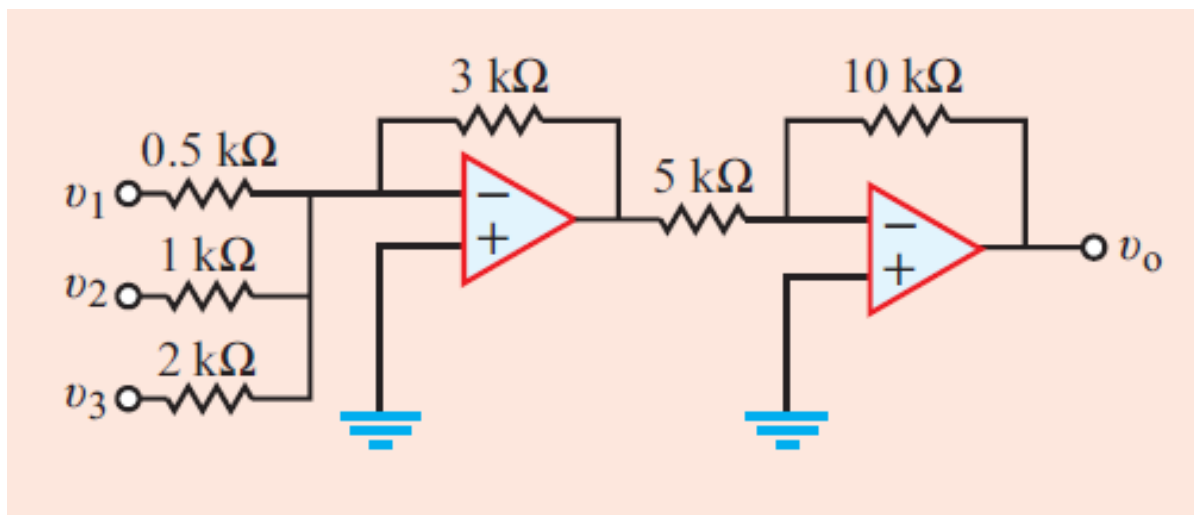
## Example 5:

Find  $v_o$  in terms of  $v_1$ ,  $v_2$  and  $v_3$ .



**Answer:**  $v_o = 12v_1 + 6v_2 + 3v_3$ .



Op-Amp Circuit	Block Diagram
<p>(a)</p> <p><b>Noninverting Amp</b> (<math>v_o</math> independent of <math>R_s</math>)</p>	<p><math>G = \frac{R_1 + R_2}{R_2}</math> <math>v_o = G v_s</math></p>
<p>(b)</p> <p><b>Inverting Amp</b></p>	<p><math>G = -\frac{R_f}{R_s}</math> <math>v_o = G v_s</math></p>
<p>(c)</p> <p><b>Inverting Summing Amp</b></p>	<p><math>G_1 = -R_f/R_1</math> <math>G_2 = -R_f/R_2</math> <math>G_3 = -R_f/R_3</math> <math>v_o = G_1 v_1 + G_2 v_2 + G_3 v_3</math></p>
<p>(d)</p> <p><b>Subtracting Amp</b></p>	<p><math>G_1 = -\frac{R_2}{R_1}</math> <math>G_2 = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right)</math> <math>v_o = G_1 v_1 + G_2 v_2</math></p>
<p>(e)</p> <p><b>Voltage Follower / Buffer</b> (<math>v_o</math> independent of <math>R_s</math> and <math>R_L</math>)</p>	<p><math>G = 1</math> <math>v_o = v_s</math></p>
<p>(f)</p> <p><b>Noninverting Summing Amp</b></p>	<p><math>G_1 = \left(\frac{R_1 + R_2}{R_2}\right) \left(\frac{R_{s1}}{R_{s1} + R_{s2}}\right)</math> <math>G_2 = \left(\frac{R_1 + R_2}{R_2}\right) \left(\frac{R_{s2}}{R_{s1} + R_{s2}}\right)</math> <math>v_o = G_1 v_1 + G_2 v_2</math></p>

# Practice Problems (Chap. 4)




- Solve the following problems: 4, 8, 12, 16, 20, ..., 52.
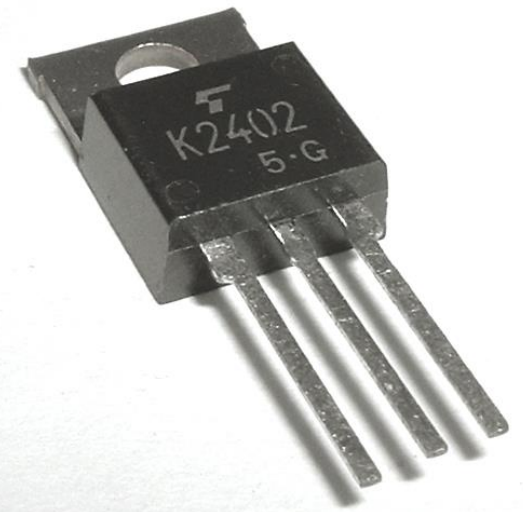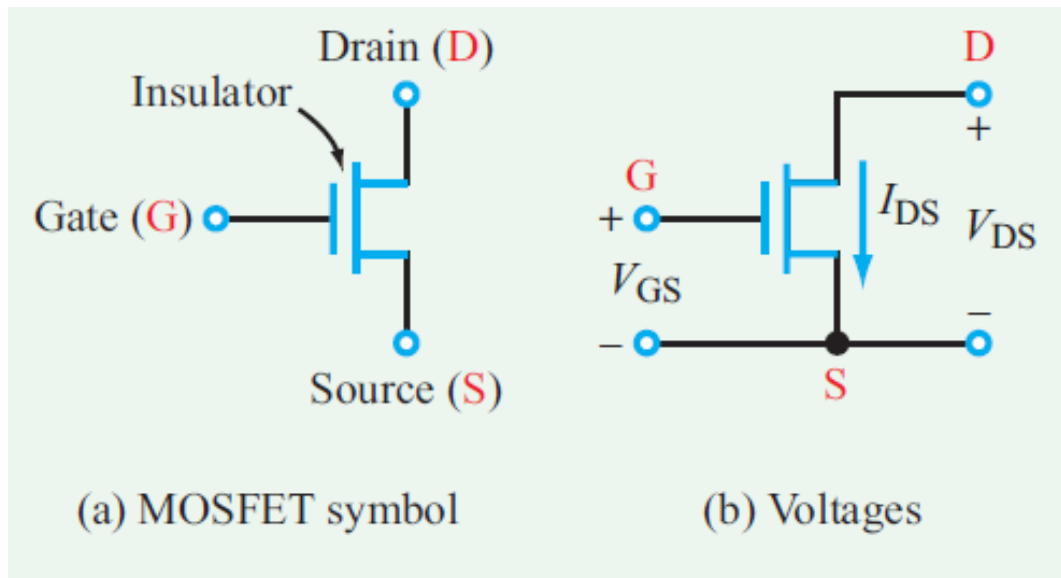
# Another Transistor: the MOSFET


- A MOSFET (metal-oxide semiconductor field-effect transistor) is a voltage-controlled electronic switch.
- A MOSFET has three terminals: the **gate** (G), the **source** (S), and the **drain** (D).
- Because the gate G is separated from the rest of the transistor by the thin insulating layer, no dc current can flow from G to either D or S.



# MOSFET Equivalent Circuit

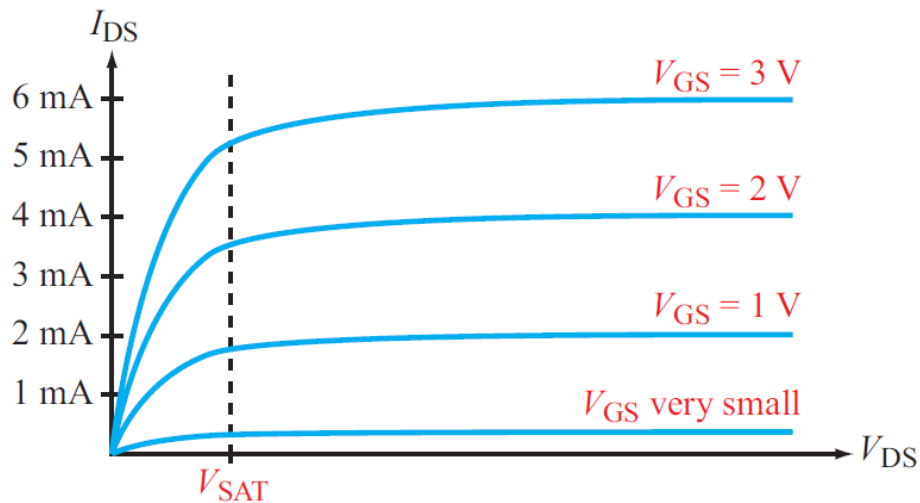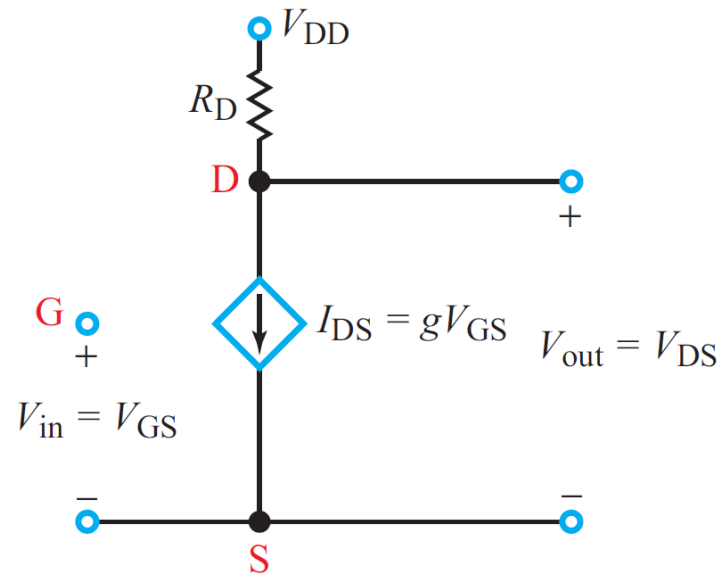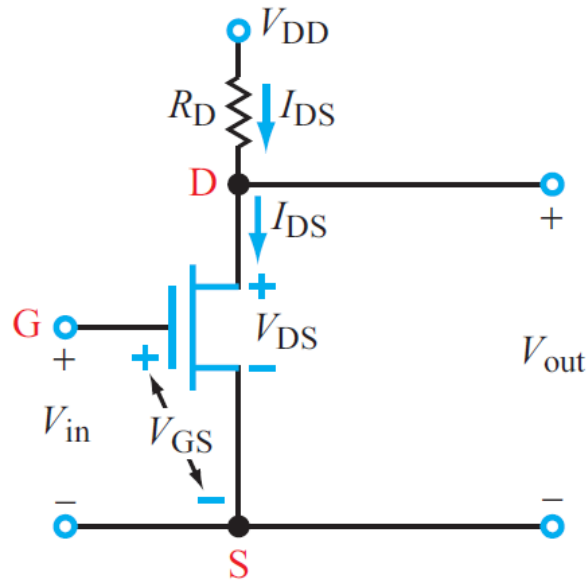



Characteristic curves

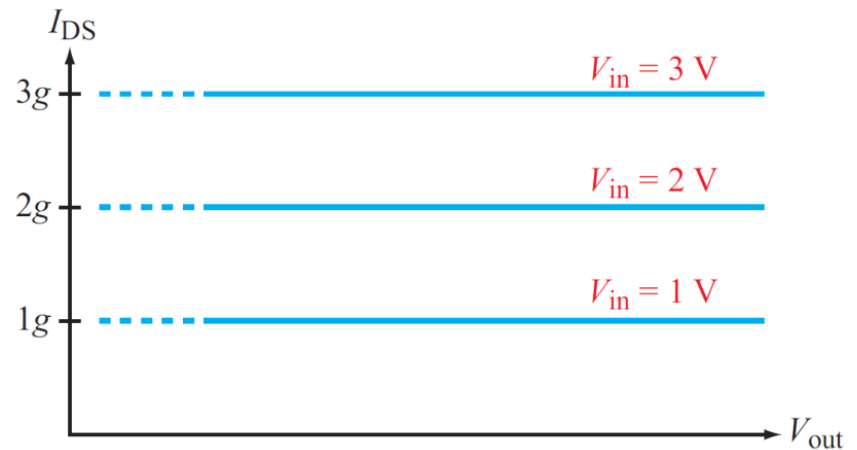



Idealized response



# MOSFETs in Digital Circuits

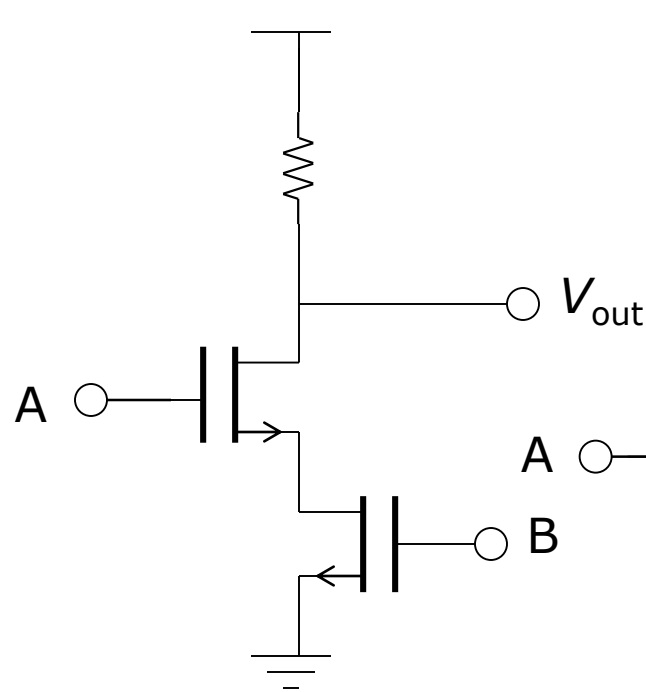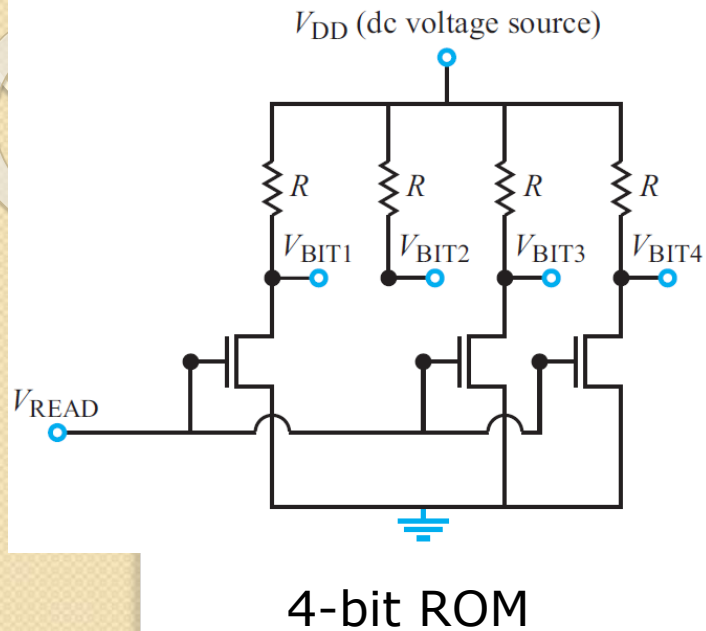

NAND Gate

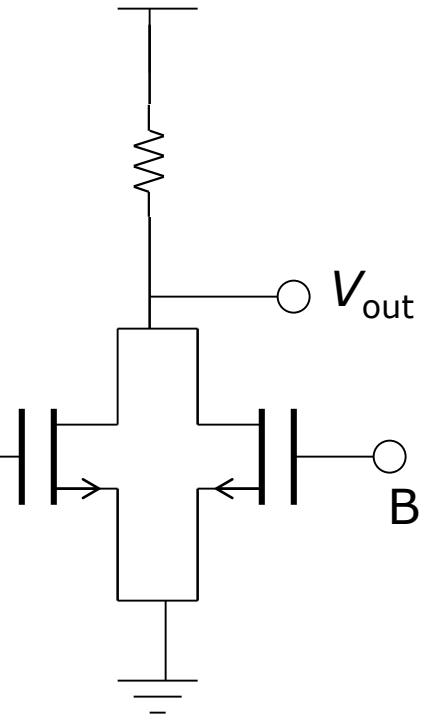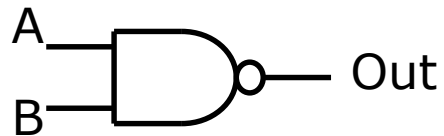

NOR Gate

