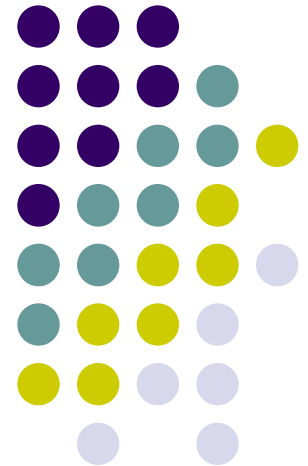



Review of 3-Phase AC Circuits

EE 340

Y. Baghzouz




Advantages of 3-Phase Systems

 






- Can transmit more power for same amount of wire (twice as much as single phase)
- Torque produced by 3ϕ machines is constant
- Three phase machines use less material for same power rating
- Three phase machines start more easily than single phase machines

Balanced 3-Phase Systems


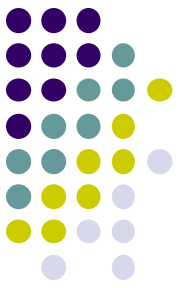


- A balanced 3 phase (ϕ) system has
 - three voltage sources with equal magnitude, but with an angle shift of 120°
 - equal loads on each phase
 - equal impedance on the lines connecting the generators to the loads
- Bulk power systems are almost exclusively 3ϕ
- Single phase is used primarily only in low voltage, low power settings, such as residential and some commercial



3-Phase Voltage Source

     

Neutral Wire Sharing

  

Neutral Current in Balanced Circuit = 0

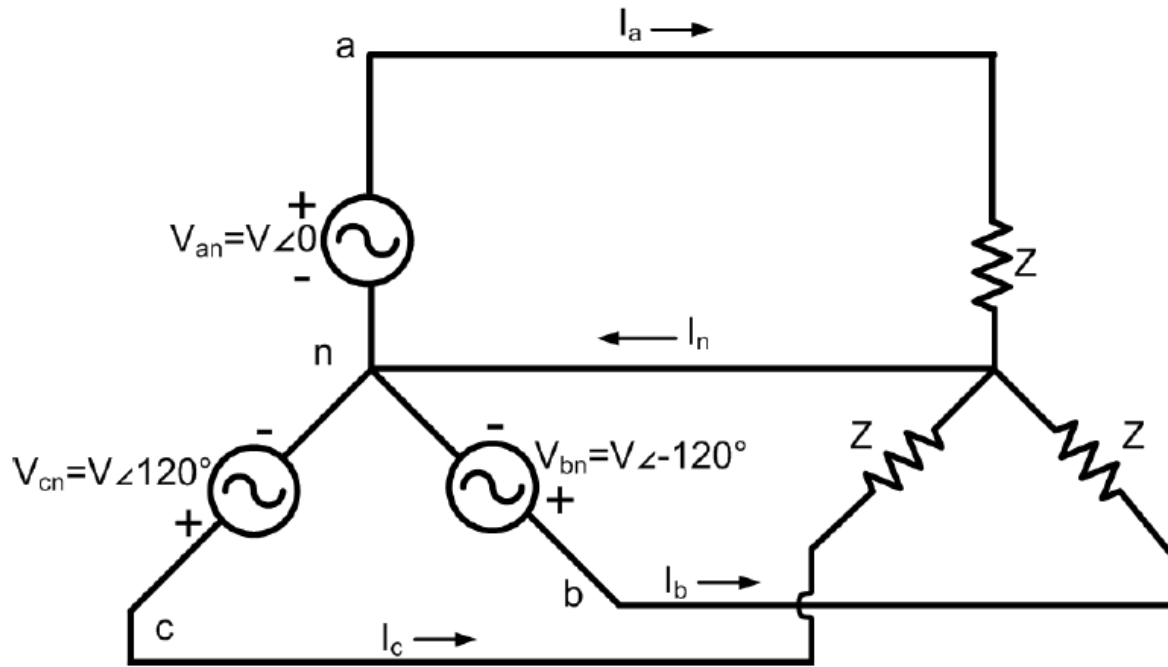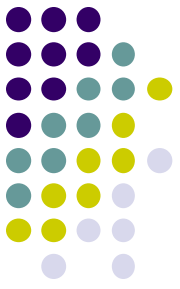


$$I_n = I_a + I_b + I_c$$

$$I_n = \frac{V}{Z} (1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle 120^\circ) = 0$$



Phase Voltages and Line Voltages

 

$$V_{an} = |V| \angle \alpha^\circ$$

$$V_{bn} = |V| \angle \alpha^\circ - 120^\circ$$

$$V_{cn} = |V| \angle \alpha^\circ + 120^\circ$$

($\alpha = 0$ in this case)

$$V_{ab} = V_{an} - V_{bn} = |V|(1 \angle \alpha - 1 \angle \alpha + 120^\circ)$$


$$= \sqrt{3} |V| \angle \alpha + 30^\circ$$

$$V_{bc} = \sqrt{3} |V| \angle \alpha - 90^\circ$$


$$V_{ca} = \sqrt{3} |V| \angle \alpha + 150^\circ$$

Line to line
voltages are
also balanced


Example of Phase and Line Voltages

 


Y-Connected Load

 

Δ -Connected Load

 

Power in Balanced 3-Phase Circuits

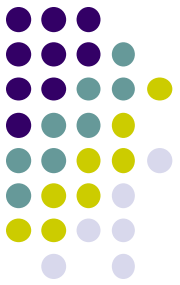


- The real power, reactive power, apparent power, complex power and power factor are the same in each phase.

$$P = 3V_p I \cos(\theta) = \sqrt{3}V_L I \cos(\theta)$$


$$Q = 3V_p I \sin(\theta) = \sqrt{3}V_L I \sin(\theta)$$

$$S = 3V_p I = \sqrt{3}V_L I$$


 
Power measurement in 3-phase 4-wire circuit



 - If the load is balanced, then $P_1 = P_2 = P_3$.
Hence, $P_T = 3P_1$
- If the load is unbalanced, $P_1 \neq P_2 \neq P_3$,
Hence, $P_T = P_1 + P_2 + P_3$



Example: 1

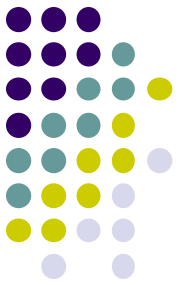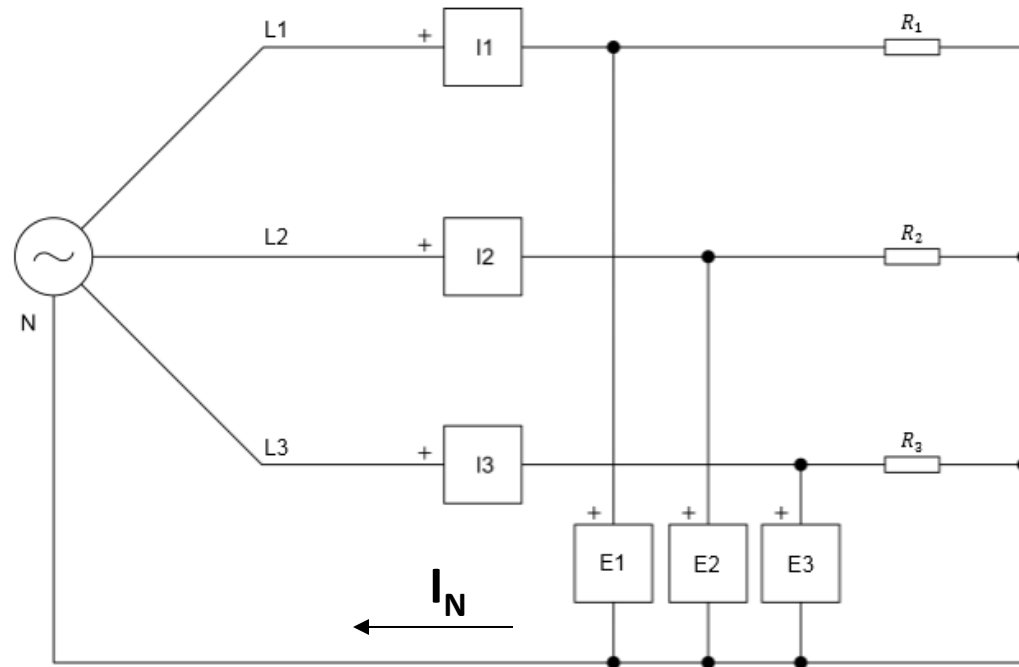

The phase voltage of the positive-sequence balanced source is 120 V. Let $R_1 = 100 \Omega$, $R_2 = 200 \Omega$, $R_3 = 300 \Omega$.

Compute the real power supplied by each phase, the neutral current, and the **current imbalance** which is defined as the maximum percentage deviation of any pair of phase currents relative to the average of the three phases.


Answer:

$$I_1 = 1.2 \text{ A}, I_2 = 0.6 \text{ A}, I_3 = 0.4 \text{ A},$$


$$P_1 = 144 \text{ W}, P_2 = 72 \text{ W}, P_3 = 48 \text{ W},$$

$$I_N = 0.72 \text{ A}, I_{im} = 63.7 \%$$


 
Power measurement in 3-phase 3-wire circuit: the 2-wattmeter method



- $P_T = P_1 + P_2$
- The load can be Y-connected, Δ -connected, balanced, or unbalanced.
- Any one of the 3 phases can be used as a reference.
- If the load is balanced, then $P_1 = P_2 = P_T/2$,

 

Example 2

 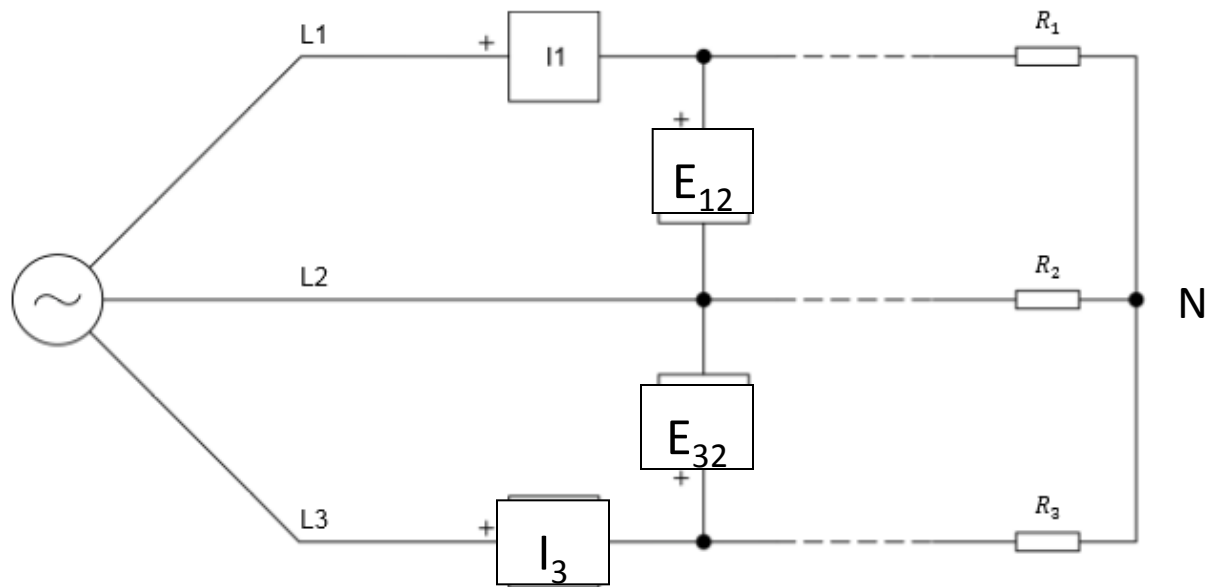

The phase voltage of the positive-sequence balanced source is 120 V. Let $R_1 = 100 \Omega$, $R_2 = 200 \Omega$, $R_3 = 300 \Omega$.

Compute the real power supplied by each of the two wattmeters, the power supplied by each phase, and the **current imbalance**.

Answer:

$$E_1 = 120 \angle 0^\circ \text{ V}, E_2 = 120 \angle -120^\circ \text{ V}, E_3 = 120 \angle +120^\circ \text{ V}, E_{12} = 208 \angle 30^\circ \text{ V}, \\ E_{32} = 208 \angle 90^\circ \text{ V}, E_N = 39.33 \angle -13.9^\circ \text{ V}$$



$$I_1 = 0.823 \angle 6.6^\circ \text{ A}, I_2 = 0.68 \angle -135^\circ \text{ A}, I_3 = 0.50 \angle 130.9^\circ \text{ A},$$

$$P_{12} = 157 \text{ W}, P_{32} = 79 \text{ W}, P_{\text{tot}} = 236 \text{ W}.$$

$$P_1 = 98 \text{ W}, P_2 = 79 \text{ W}, P_3 = 59 \text{ W}, P_{\text{tot}} = 236 \text{ W}$$

$$I_{\text{im}} = 25\%$$

Example 3

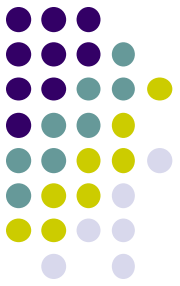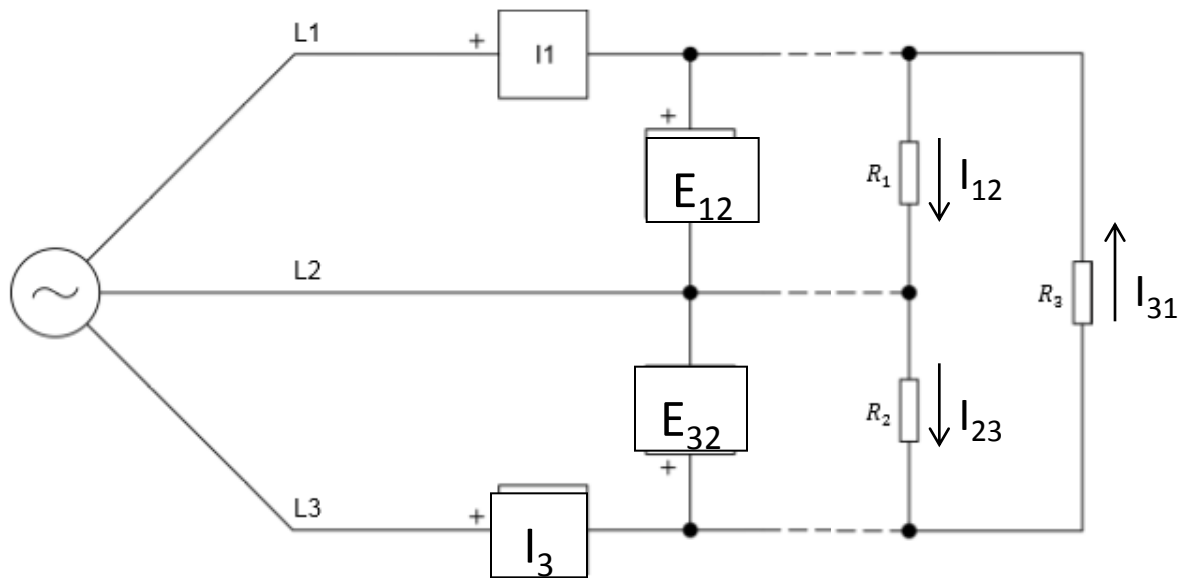

The phase voltage of the positive-sequence balanced source is 120 V. Let $R_1 = 100 \Omega$, $R_2 = 200 \Omega$, $R_3 = 300 \Omega$.

Compute the real power measured by the 2 wattmeter method.

Answer:




$$I_{12} = 2.08 \angle 30^\circ \text{ A}, I_{23} = 1.04 \angle -90^\circ \text{ A}, I_{31} = 0.69 \angle 150^\circ \text{ A},$$

$$I_1 = 2.5 \angle 16.2^\circ \text{ A}, I_3 = 1.51 \angle 113.3^\circ \text{ A},$$

$$P_{12} = 505 \text{ W}, P_{32} = 288 \text{ W}, P_{\text{tot}} = 793 \text{ W},$$

$$\text{Check: } P_{\text{tot}} = 208^2/100 + 208^2/200 + 208^2/300 = 793 \text{ W},$$

Delta-Wye Transformation

   

$\Delta \rightarrow Y$ transformation

$$R1 = \frac{Rb Rc}{Ra + Rb + Rc}$$

$$R2 = \frac{Ra Rc}{Ra + Rb + Rc}$$

$$R3 = \frac{Ra Rb}{Ra + Rb + Rc}$$



$Y \rightarrow \Delta$ transformation

$$Ra = \frac{R1 R2 + R2 R3 + R3 R1}{R1}$$


$$Rb = \frac{R1 R2 + R2 R3 + R3 R1}{R2}$$

$$Rc = \frac{R1 R2 + R2 R3 + R3 R1}{R3}$$

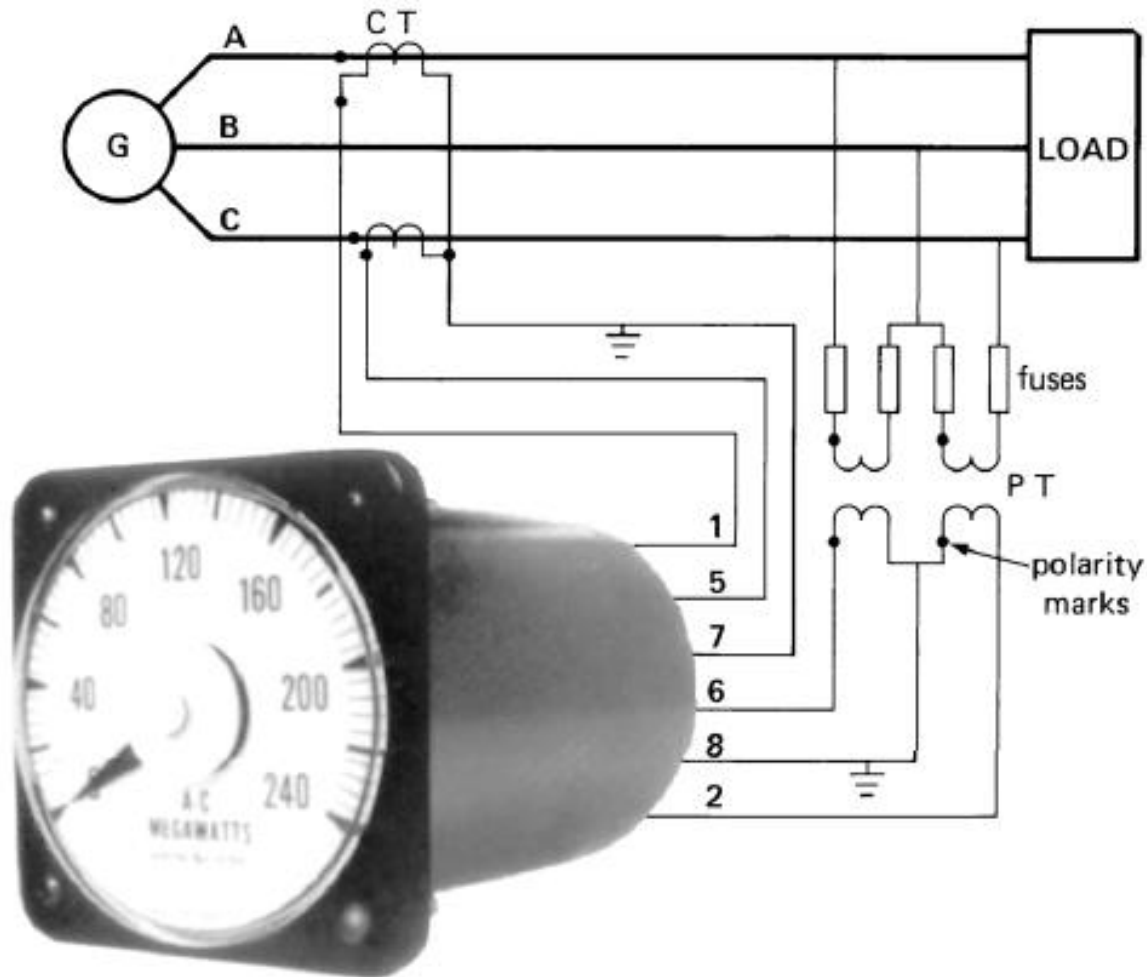 Measuring active power in a high power circuit



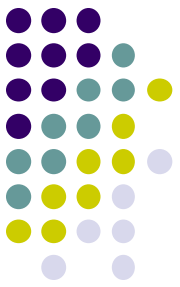Per-Phase Analysis in Balanced 3-Phase Circuits




- Per phase analysis allows analysis of balanced 3ϕ systems with the same effort as for a single phase system
- **To do per phase analysis**
 1. Convert all 3ϕ load/sources to equivalent Y's
 2. Solve phase "a" independent of the other phases
 3. Total system power $S = 3 V_a I_a^*$
 4. If desired, phase "b" and "c" values can be determined by inspection (i.e., $\pm 120^\circ$ degree phase shifts)
 5. If necessary, go back to original circuit to determine line-line values or internal 3ϕ values.


 
Example of per-phase analysis of balanced circuits



- Find the complex power supplied by each of the two sources.



Solution

 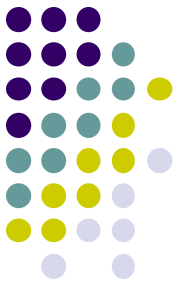

To solve the circuit, write the KCL equation at a'

$$(V'_a - 1\angle 0^\circ)(-10j) + V'_a(3j) + (V'_a - \frac{1}{\sqrt{3}}\angle -30^\circ)(-10j) = 0$$

$$(10j + \frac{10}{\sqrt{3}}\angle 60^\circ) = V'_a(10j - 3j + 10j)$$



$$V'_a = 0.9\angle -10.9^\circ \text{ volts} \quad V'_b = 0.9\angle -130.9^\circ \text{ volts}$$

$$V'_c = 0.9\angle 109.1^\circ \text{ volts} \quad V'_{ab} = 1.56\angle 19.1^\circ \text{ volts}$$

$$S_{Y_{gen}} = 3V_a I_a^* = V_a \left(\frac{V_a - V'_a}{j0.1} \right)^* = 5.1 + j3.5 \text{ VA}$$

$$S_{\Delta_{gen}} = 3V_a'' \left(\frac{V_a'' - V'_a}{j0.1} \right)^* = -5.1 - j4.7 \text{ VA}$$

Example of 3-phase balanced circuit

  

$P_{out} = 3,594 \text{ hp}$
 $\eta = 93\%$
 $PF = 90\%$

3-phase motor:



$P_{out} = 3594 \times 746 = 2,681 \text{ kW}$
 $P_m = P_{out} / 0.93 = 2,883 \text{ kW}$
 $S_m = P_m / 0.9 = 3,203 \text{ kVA}$
 $Q_m = 1,395 \text{ kVAR}$
 $I_m = S_m / (1.73 \times 4000) = 462 \text{ A}$

3-phase capacitor bank:

$Q_c = 1,800 \text{ kVAR}$
 $I_c = Q_c / (1.73 \times 4000) = 260 \text{ A}$


Source Side:

  $Q_s = Q_m - Q_c = -405 \text{ kVAR}$
 $S_s = 2,911 \text{ kVA}$
 $PF_s = 99\% \text{ (lead)}$
 $I_s = S_s / (1.73 \times 4000) = 420 \text{ A}$



Problems from Chap 2:

1, 2, 3, 4, 5, 6.

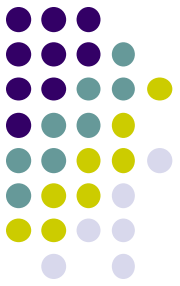

Practice problem



Consider the three-phase 3-wire load that is supplied by a balanced positive-sequence source where the rms values of phase voltages are equal to 120 V, with phase “a” voltage is taken as a reference. The load impedances across phases a-b, b-c, and c-a are purely resistive as follows: $R_{ab} = 60\Omega$, $R_{bc} = 90\Omega$, $R_{ca} = \infty$ (i.e, open circuit).

1) Calculate the power measured by wattmeter P_1 .

$$P_1 = \dots\dots\dots W$$

2) Calculate the power measured by wattmeter P_2 .

$$P_2 = \dots\dots\dots W$$

3) Calculate the rms value of current I_b .

$$I_b = \dots\dots A$$

4) Repeat the above when R_{ca} is replaced by 120Ω .


$$P_1 = \dots\dots\dots W$$

$$P_2 = \dots\dots\dots W$$


$$I_b = \dots\dots\dots A$$

Answer: (rounded to nearest integer)

 1) $P_1 = 721 W$, 2) $P_2 = 481 W$, 3) $I_b = 5 A$, 4) $P_1 = 901 W$, $P_2 = 661 W$, $I_b = 5 A$



Homework Assignment # 2

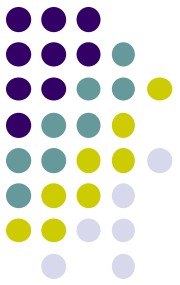

A 3-phase power supply is feeding an unbalanced resistive load as shown below.

- 1) Determine the real and reactive power **supplied** by each phase.
- 2) It is desired to balance the load and eliminate any reactive power supplied or absorbed by the phase voltages. This can be achieved by installing a delta-connected bank of reactive elements in parallel with the load as shown (i.e., the source currents will be balanced and in-phase with their respective phase voltages). Calculate the values of such reactive elements.

