

## EE 340 – Spring 2017 – Last Assignment

Consider a 6-mile long 12.47 kV distribution feeder that serves a load of 9 MVA with 0.8 power factor. Assume the feeder is balanced and has a series impedance of  $0.5 + j1 \Omega/\text{mile}$ . The voltage at the substation is supplied by a stiff source at 1.0 p.u. Further assume that the load is of constant power type and it is distributed equally at 3 concentration points located at 2 mi, 4 mi, and 6 mi from the substation. Use Powerworld to answer the following questions:

- a) Determine the voltage at the 3 load points, and power loss in the feeder.
- b) It is desired to keep the voltage levels within  $\pm 5\%$  of the nominal value by placing a capacitor bank at the middle node. Determine the minimum size of such capacitor bank, and the new power loss (use increments of 0.3 MVAR).
- c) If capacitor banks are placed at each of the 3 load points and provide 100% of the local load reactive power demand, determine the new voltage at the three node points, and new power loss.