

EE 340 – Spring 2017 – Assignment # 3

Consider a 500 kV transmission line with total series impedance = $j100\Omega$ and total shunt admittance = 0.0008 S . the line is connected to a stiff source that is fixed at the sending end ($V_s = 1\text{ pu}$). Assume the load is of constant power type.

1) Plot the receiving end voltage as a function of load real power for a) 0.9 power factor (lag), b) unity power factor, and c) 0.9 power factor (lead).

2) Plot the source reactive power Q_s as a function of receiving end voltage for the following load powers: a) $P = 0\text{ MW}$, b) $P = 500\text{ MW}$, c) $P = 1000\text{ MW}$ and d) $P = 1500\text{ MW}$, e) 2000 MW .