

EE 340 – HW # 3

Consider a 3-phase, 370 km (230 mi) long transmission line that has a flat horizontal spacing with 7.25 m (or 23.8 ft.) between conductors. The conductor type is ACSR-Rook with resistance is 0.1603 Ω /mi, GMR = .0327 ft., diameter = 0.977 in, and ampacity = 785 A. The line-to-line voltage at the sending end is fixed at 245 kV.

- 1) Calculate the sending-end current and power, and receiving-end voltage under no load. Determine the shunt reactor that is needed such that $V_R = 1.05 V_S$.
- 2) Assume the load is purely resistive (i.e., unity power factor). Calculate the following: a) power delivered to the load and load current when $V_R = 0.95 V_S$. b) Power delivered to the load and V_R when I_R reaches 785 A. c) V_R and I_R when the power delivered to the load reaches its maximum value. d) Plot V_R as a function of the power delivered to the load.
- 3) Repeat 2) after placing a series capacitor that compensates 70% of the line series reactance.



Note:

$$\begin{aligned}\sinh(x + iy) &= \sinh x \cos y + i \cosh x \sin y \\ \cosh(x + iy) &= \cosh x \cos y + i \sinh x \sin y.\end{aligned}$$