


EE 742

# Chapter 3: Power System in the Steady State

Y. Baghzouz

# Transmission Line Model

Distributed Parameter Model:

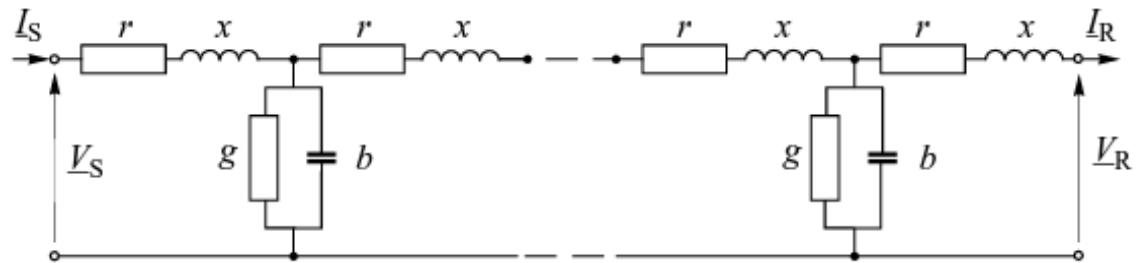


Terminal Voltage/Current Relations:

$$\begin{bmatrix} \underline{V}_S \\ \underline{I}_S \end{bmatrix} = \begin{bmatrix} \cosh \underline{\gamma} l & \underline{Z}_C \sinh \underline{\gamma} l \\ \sinh \underline{\gamma} l / \underline{Z}_C & \cosh \underline{\gamma} l \end{bmatrix} \begin{bmatrix} \underline{V}_R \\ \underline{I}_R \end{bmatrix},$$

Characteristic impedance:  $\underline{Z}_C = \sqrt{\underline{z}/\underline{y}}$

Propagation constant:  $\underline{\gamma} = \sqrt{\underline{z}\underline{y}}$

$\pi$  equivalent Circuit:

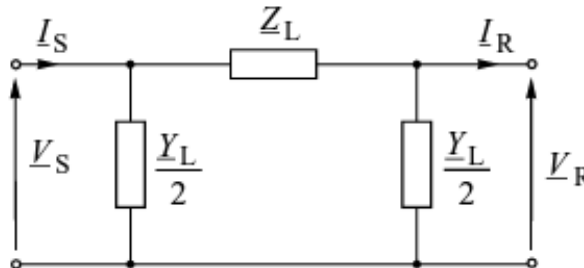

$\pi$  equivalent Circuit parameters:  $\underline{Z}_L = \underline{Z} \frac{\sinh \underline{\gamma} l}{\underline{\gamma} l}, \quad \underline{Y}_L = \underline{Y} \frac{\tanh(\underline{\gamma} l / 2)}{\underline{\gamma} l / 2},$

where  $\underline{Z} = \underline{z}l$  is the total series impedance and  $\underline{Y} = \underline{y}l$  is the total shunt admittance:

# Transmission Line Model

- Simplified models for medium and short lines:
  - Medium line ( 50 mi <  $l$  < 150 mi):  $\underline{Z}_L = \underline{Z}, \quad \underline{Y}_L = \underline{Y}.$
  - Short line (  $l$  < 50 mi):  $\underline{Z}_L = \underline{Z}, \quad \underline{Y}_L = 0.$
- In a typical line,  $g$  can be neglected.  $r$  can also be neglected (since  $r \ll x$ ), then the line becomes lossless and the characteristic impedance becomes a pure real number (  $Z_c = (L/C)^{1/2}$  ), while propagation constant become pure imaginary number (  $\gamma = j\beta = j\omega(LC)^{1/2}$  ). The voltage/current equations become

$$\underline{V}_S = \underline{V}_R \cos \beta l + j Z_C \underline{I}_R \sin \beta l$$

$$\underline{I}_S = \underline{I}_R \cos \beta l + j ( \underline{V}_R / Z_C ) \sin \beta l,$$


- Note that the voltage and current vary sinusoidally along the line length. The wavelength of the full cycle is  $\lambda = 2\pi/\beta$ .

# Surge Impedance Loading (SIL)

- Power delivered at rated voltage to a load whose impedance is equal to the surge impedance:

$$P_{\text{SIL}} = \frac{V_n^2}{Z_C}$$

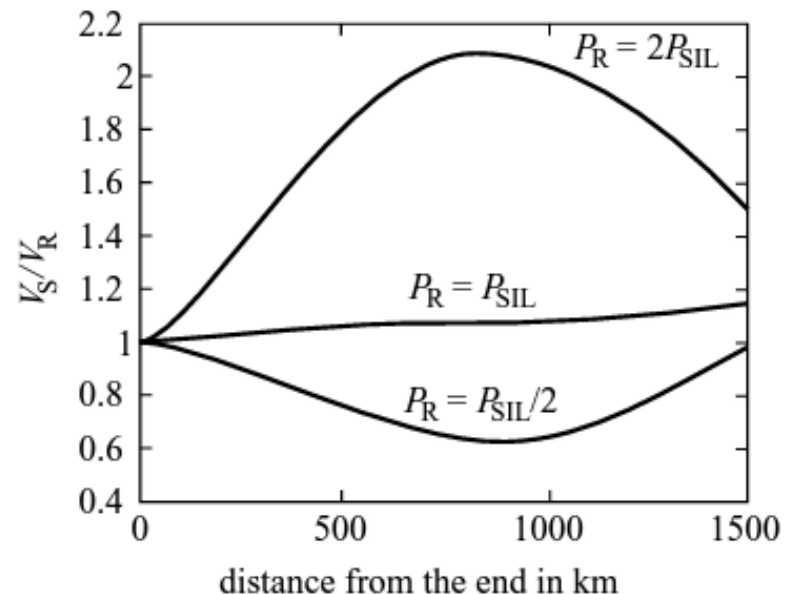- Under such condition
  - The voltage and current profiles are flat
  - The reactive power loss in the line is zero.
- In reality, the loading is rarely equal to this “natural load”.
- Voltage variation with loading (see fig.)



# Real Power Transmission

- Complex power at receiving end (assuming lossless line):

$$\underline{S}_R = \underline{V}_R \underline{I}_R^* = \frac{V_R V_S}{Z_C \sin \beta l} e^{j(\pi/2 - \delta_{SR})} - \frac{V_R^2 \cos \beta l}{Z_C \sin \beta l} e^{j\pi/2}.$$

- Real power at receiving end:

$$P_R = \text{Re} [S] = \frac{V_S V_R}{Z_C \sin \beta l} \sin \delta_{SR},$$

- Maximum power at receiving end

$$P_{R,\max} = \frac{V_S V_R}{Z_C \sin \beta l} \approx \frac{P_{\text{SIL}}}{\sin \beta l}.$$

- For lines less than 150 miles,

$$\sin \beta l \cong \beta l, \quad \cos \beta l \approx 1, \quad Z_C \sin \beta l \cong \sqrt{\frac{L}{C}} \omega \sqrt{LC} l = \omega L l = X,$$

$$P_R \cong \frac{V_S V_R}{X} \sin \delta_{SR},$$

# Reactive Power Considerations

- Complex power at receiving end (assuming lossless line):

$$\underline{S}_R = \underline{V}_R \underline{I}_R^* = \frac{V_R V_S}{Z_C \sin \beta l} e^{j(\pi/2 - \delta_{SR})} - \frac{V_R^2 \cos \beta l}{Z_C \sin \beta l} e^{j\pi/2}.$$

- Reactive power at receiving end:

$$Q_R = \text{Im} [\underline{V}_R \underline{I}_R^*] = \frac{V_S V_R}{Z_C \sin \beta l} \cos \delta_{SR} - \frac{V_R^2 \cos \beta l}{Z_C \sin \beta l} = \frac{V_R}{Z_C \sin \beta l} (V_S \cos \delta_{SR} - V_R \cos \beta l).$$

- Approximate expression of lines less than 150 mi long:


$$Q_R \cong \frac{V_R}{X} (V_S \cos \delta_{SR} - V_R). \quad Q_S \cong \frac{V_S}{X} (V_S - V_R \cos \delta_{SR}).$$

- And for small transmission angles,

$$Q_R \approx \frac{V_R (V_S - V_R)}{X}, \quad Q_S \approx \frac{V_S}{X} (V_S - V_R).$$
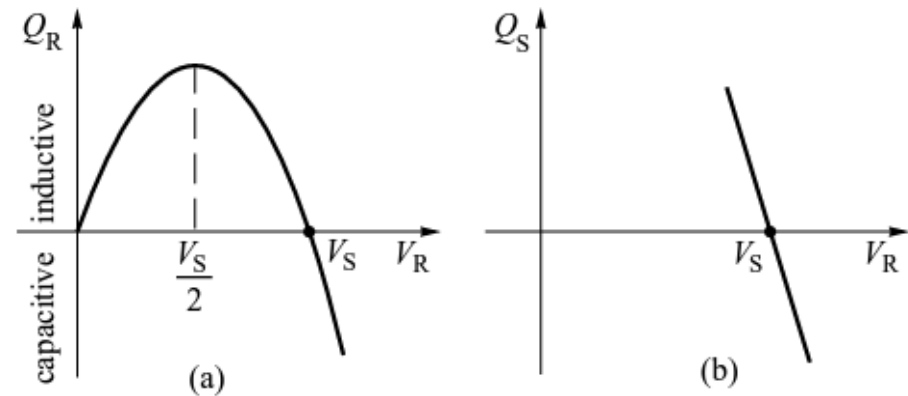
# Reactive Power Considerations


- Change in  $Q_R$  and in  $Q_S$  (when the influence of real power flow is neglected)



- Reactive power loss under the presence of real power flow:

$$\Delta Q = Q_S - Q_R = \frac{V_S^2 \cos \beta l - 2 V_S V_R \cos \delta_{SR} + V_R^2 \cos \beta l}{Z_C \sin \beta l}.$$
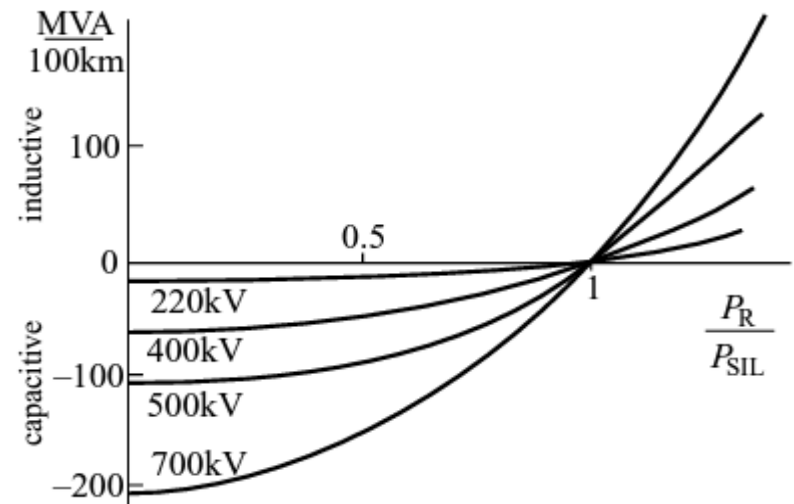
$$\Delta Q(P_R) \approx \frac{2 P_{SIL}}{\sin \beta l} \left[ \cos \beta l - \sqrt{1 - \left( \frac{P_R \sin \beta l}{P_{SIL}} \right)^2} \right].$$



## Homework # 2


Consider a 500 kV, 60 Hz transmission line that is 250 mi long. Assume the line parameters are as follows: resistance  $r=0.018 \text{ } \Omega/\text{mi}$ , reactance  $x= 0.47 \text{ } \Omega/\text{mi}$ , suceptance  $b=7.5 \text{ } \mu\text{S}/\text{mi}$ , receiving end voltage is fixed at rated value (i.e., 288.7 kV/phase), receiving end power = 300 MW/phase @ unity power factor. Calculate the following:

- a) Voltage at the sending end.
- b) Real and reactive power supplied at the sending end.
- c) Recalculate the above using the approximate (lossless) line model.



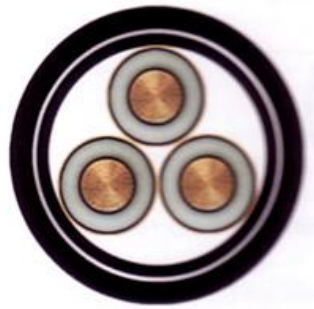
# Underground cables

- Modeled the same way as overhead lines
- The typical per-unit series reactance of a cable is about half of that of an overhead line of the same rating.
- The per-unit charging current of a cable is about 30 times larger than that of an overhead line of the same rating – thus severely limiting transmission capacity.




# Transformers

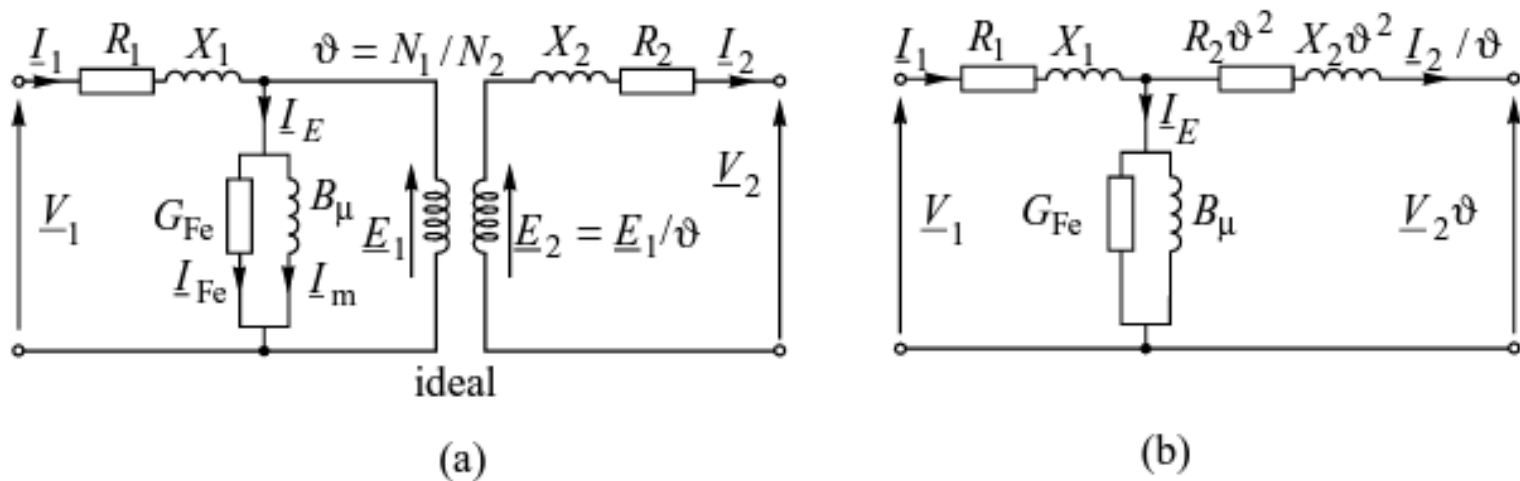


- Equivalent circuit (see above figure)
- Approximate equivalent  $\pi$  circuit (see figure below)
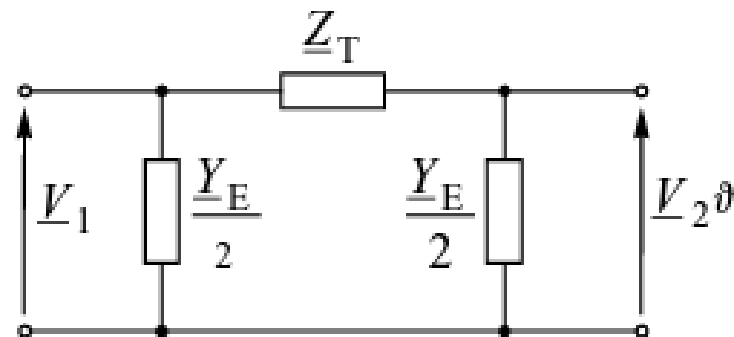
$$\underline{Z}_T = \underline{Z}_1 + \underline{Z}_2 = R + jX, \quad Y_E = G_{FE} + jB_\mu.$$




# Transformers

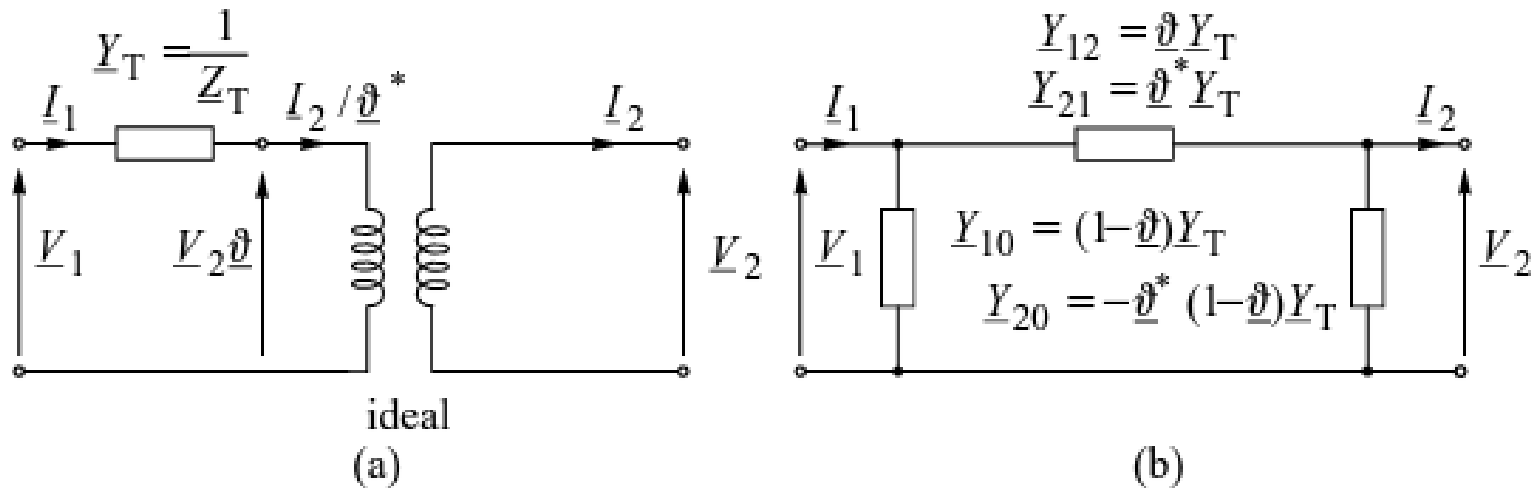

- Equivalent circuit with off-nominal turn ratio (including phase shift)  $\rightarrow$  turn ratio is represented by a complex number. Herein, the shunt branch is ignored.

$$\begin{bmatrix} \underline{I}_1 \\ -\underline{I}_2/\vartheta^* \end{bmatrix} = \begin{bmatrix} \underline{Y}_T & -\underline{Y}_T \\ -\underline{Y}_T & \underline{Y}_T \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \vartheta \underline{V}_2 \end{bmatrix} \rightarrow \begin{bmatrix} \underline{I}_1 \\ -\underline{I}_2 \end{bmatrix} = \begin{bmatrix} \underline{Y}_T & -\vartheta \underline{Y}_T \\ -\vartheta^* \underline{Y}_T & \vartheta^* \vartheta \underline{Y}_T \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix}.$$
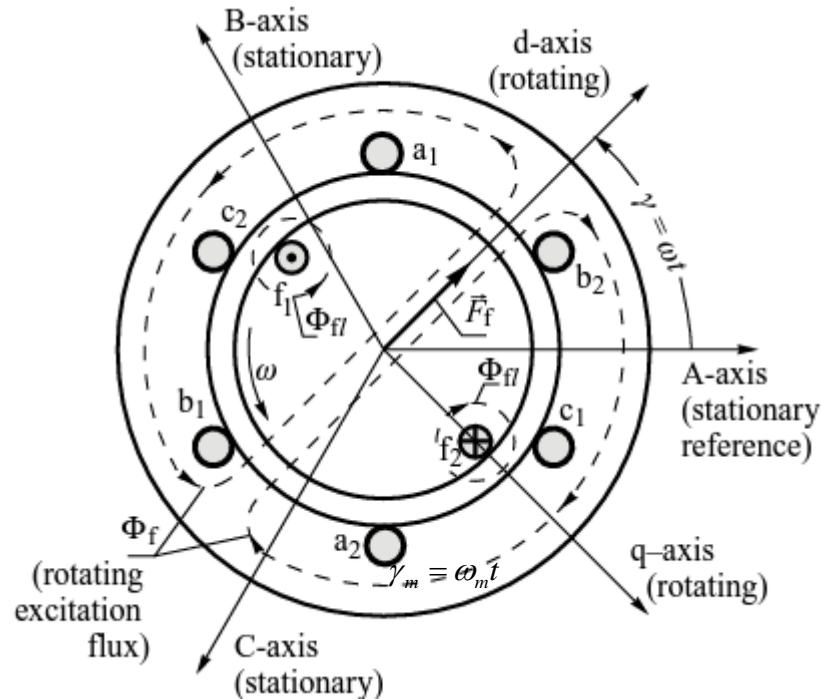
# Synchronous Generators: 2-pole round rotor



- For a 2-pole machine: velocity  $\omega_m = \omega_e$ , and angle  $\gamma_m = \gamma_e$ ,  $\gamma = \omega t$
- Rotor flux produced by field current :  $\Phi_f = \frac{F_f}{\Re} = \frac{N_f i_f}{\Re}$ ,
- Flux linkage induced in phase a (ref.):  $\Psi_{fA}(t) = N_\phi \Phi_f \cos(\omega t) = \Psi_{fA} \cos(\omega t)$
- Induced emfs (internal voltages) in stator windings:

$$e_{fA} = -\frac{d\Psi_{fA}(t)}{dt} = \omega M_f i_f \sin \omega t, \quad e_{fB} = -\frac{d\Psi_{fB}(t)}{dt} = \omega M_f i_f \sin \left( \omega t - \frac{2\pi}{3} \right)$$



$$e_{fC} = -\frac{d\Psi_{fC}(t)}{dt} = \omega M_f i_f \sin \left( \omega t - \frac{4\pi}{3} \right).$$

Mutual inductance:  $M_f = N_\phi N_f / \Re$
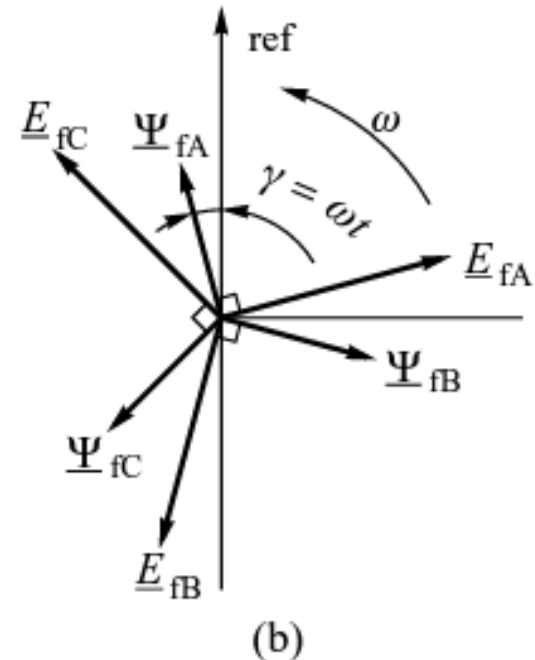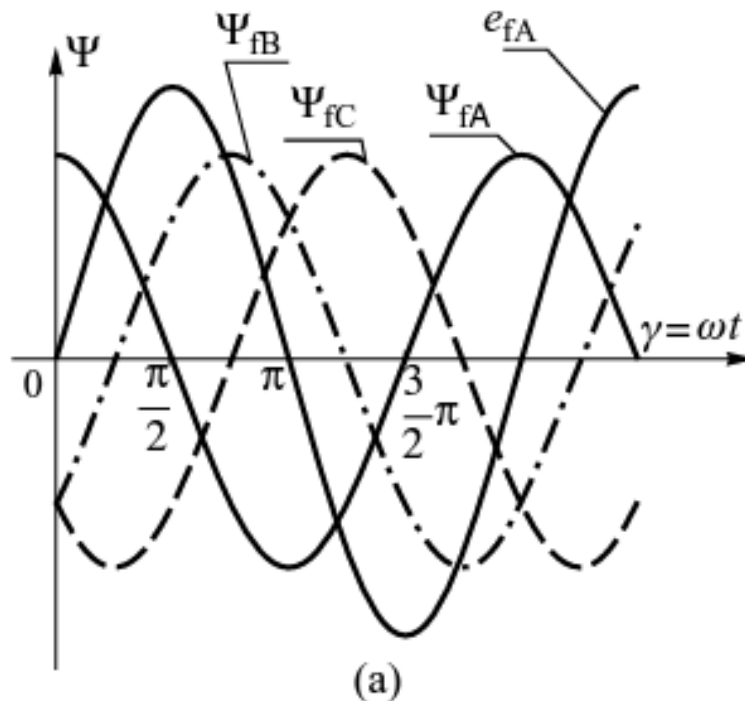
# Synchronous Generator under no-load


- Time variation of flux linkages and induced emfs (fig. a)
- Phasor representation of flux linkages and induced emfs (fig. b)
- RMS value of each emf:

$$E_f = \frac{1}{\sqrt{2}} \omega \Psi_{fa} = \frac{1}{\sqrt{2}} \omega N_\phi \Phi_f = \frac{1}{\sqrt{2}} \omega M_f i_f \cong 4.44 f M_f i_f.$$


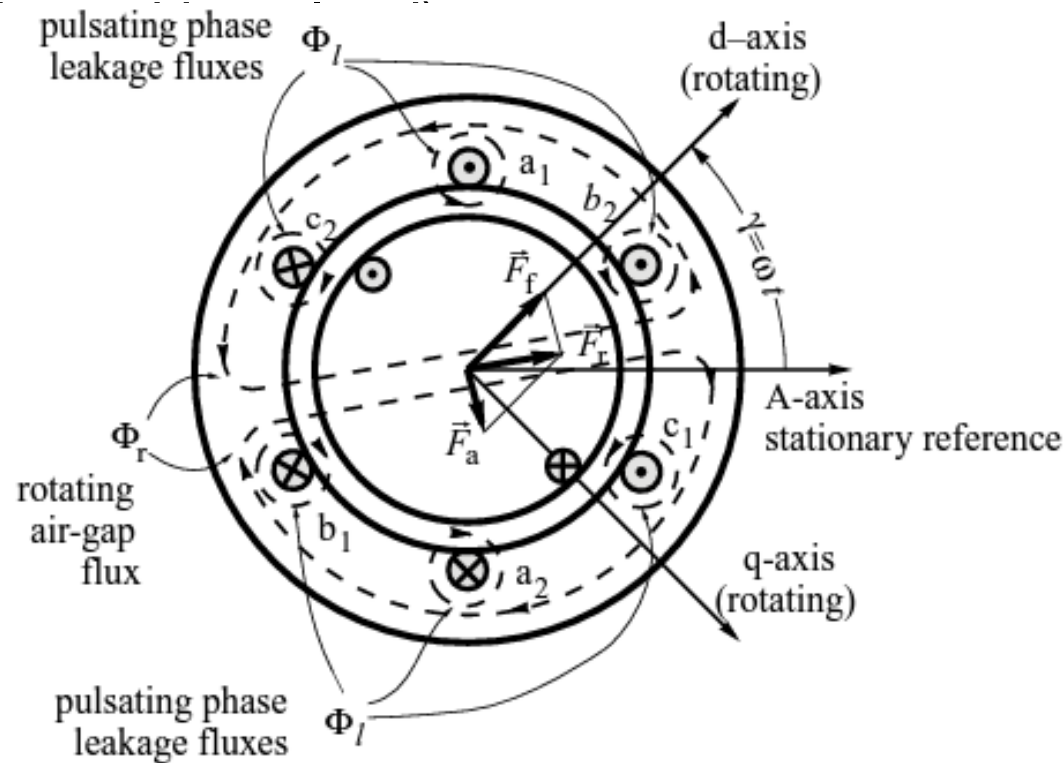
# Synchronous generator – armature reaction

- The stator phase currents produce pulsating phase mmfs that are shifted in both space and time.
- The resultant stator mmf  $F_a$  is constant ( $=1.5 N_a I_m$ ) and rotates with angular velocity  $\omega$  (i.e., stationary w.r.t. the field mmf  $F_f$ ).  $N_a$  is the effective number of turns per phase per pole ( $4N_\phi/4p$ )
- The new air-gap flux mmf  $F_r$  is equal to the vector sum of  $F_a$  and  $F_f$  (weaker



# Equivalent Circuit

- Total mmf in phase “a”:

$$F_{rA}(t) = F_f \cos \omega t + F_a \cos(\omega t - \lambda) = N_f i_f \cos \omega t + 1.5 N_a I_m \cos(\omega t - \lambda).$$

- Flux linkage in phase “a”:

$$\Psi_{rA}(t) = N_\phi \frac{F_{rA}(t)}{\mathfrak{R}} = M_f i_f \cos \omega t + L_a I_m \cos(\omega t - \lambda),$$

- Induced emf in phase “a”:

$$M_f = N_\phi N_f / \mathfrak{R}, \quad L_a = 1.5 N_a N_\phi / \mathfrak{R}$$

$$e_{rA} = -\frac{d\Psi_{rA}}{dt} = \omega M_f i_f \sin \omega t + \omega L_a I_m \sin(\omega t - \lambda) = e_{fA}(t) + e_{aA}(t),$$

- Phasor form:

$$\underline{E}_r = \underline{E}_f + \underline{E}_a = \underline{E}_f - j X_a \underline{I},$$

- Terminal voltage (after taking stator winding resistance and leakage flux into account):


$$\underline{V}_g = \underline{E}_f - j X_a \underline{I} - j X_l \underline{I} - R \underline{I} = \underline{E}_f - j X_d \underline{I} - R \underline{I},$$

# Equivalent circuit

- Armature reaction (or magnetizing) reactance:  $X_a$
- Leakage reactance:  $X_l$
- Synchronous reactance (or d-axis synchronous reactance):

$$X_d = X_a + X_l$$

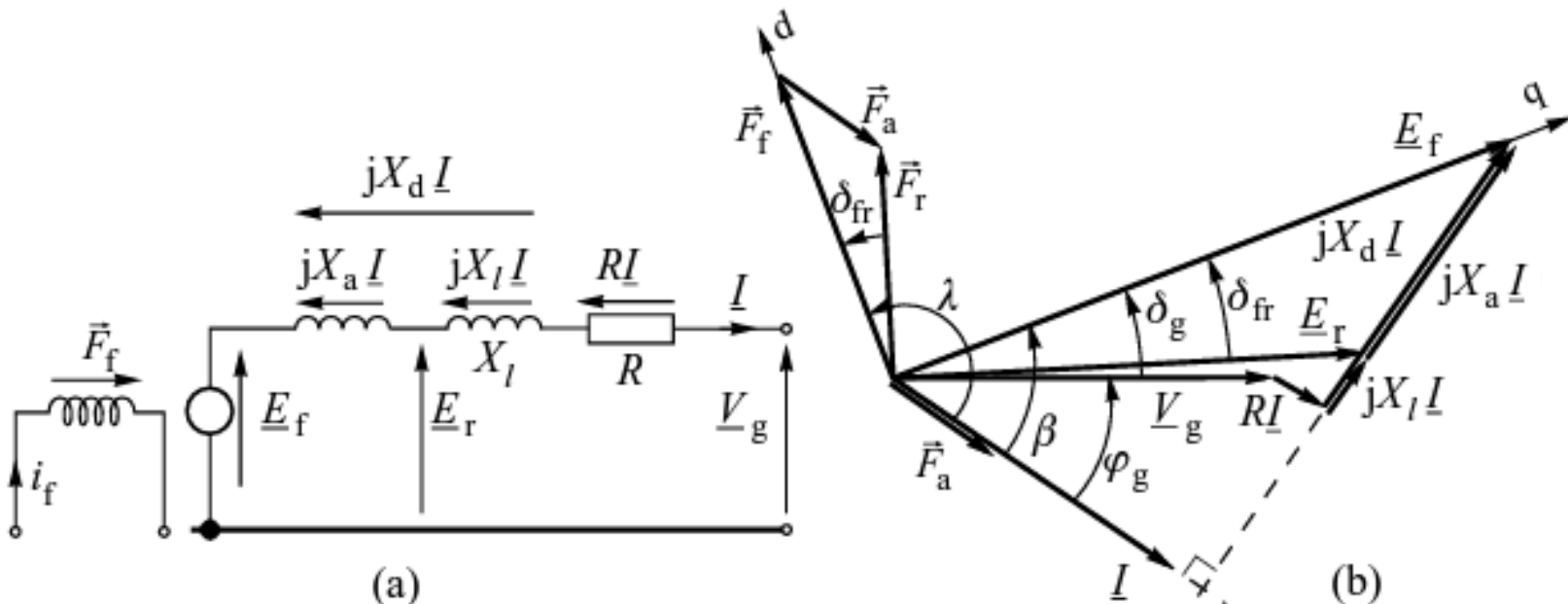- Internal emf (or voltage behind the synchronous reactance):  $E_f$





# Electromagnetic Torque

- For the rotor speed to be constant, the two opposing mechanical torque  $\tau_m$  and electromagnetic torque  $\tau$  must be equal.
- Neglecting the mechanical losses, the air gap power must equal the mechanical power:  $\tau_m \omega_m = 3E_f I \cos \beta$  (where  $\beta$  is the angle of  $I$  with respect to  $E_f$ )
- For a machine with  $p$ -poles, the electromagnetic torque can be written in a number of forms ( note:  $\lambda = \pi/2 + \beta$ , and the torque angle  $\delta_{fr}$  is the angle between  $F_r$  and  $F_f$ )

$$\tau = \frac{3}{4} p \Phi_f N_\phi I_m \cos \beta.$$

$$\tau = \frac{\pi}{8} p^2 \Phi_f F_a \sin \lambda = \frac{\pi}{8} p^2 \frac{F_f F_a}{\Re} \sin \lambda,$$


$$\tau = \frac{\pi}{8} p^2 F_r \frac{F_f}{\Re} \sin \delta_{fr} = \frac{\pi}{8} p^2 F_r \Phi_f \sin \delta_{fr},$$

$$\tau = \frac{\pi}{2} F_r \Phi_f \sin \delta_{fr}. \quad \leftarrow \text{for a 2-pole machine}$$


# Homework # 3

- Consider a cylindrical 2-pole, 60 Hz, 25 kV, 200 MVA generator . The per-unit values of  $R$ ,  $X_a$  and  $X_l$  are 0.05, 0.8 and 0.1, respectively. The generator is delivering  $0.8 + j0.5$  pu of complex power to the network and the terminal voltage is at 1 pu. Calculate the following:
  - $E_f$  and  $E_r$
  - $\delta_g$  and torque angle  $\delta_{fr}$
  - $\lambda$  and internal power factor angle  $\beta$
  - Real and reactive power losses in the generator
  - Airgap power and mechanical torque (ignore mech. losses).

# Salient pole machines – 2 poles

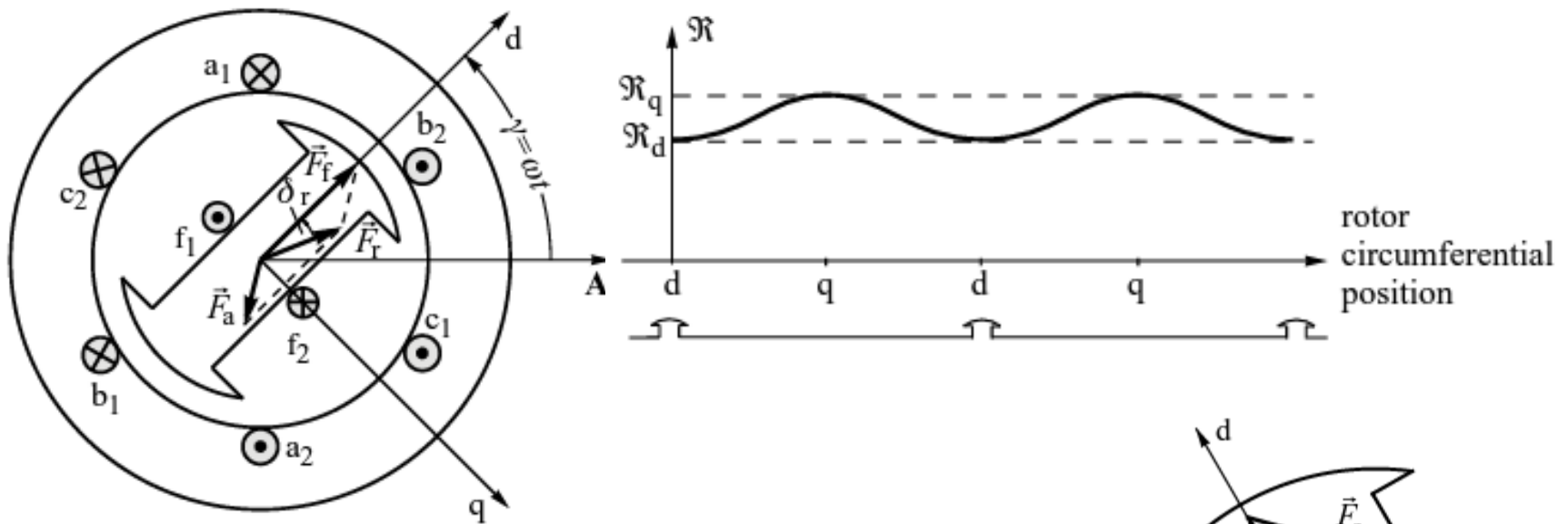

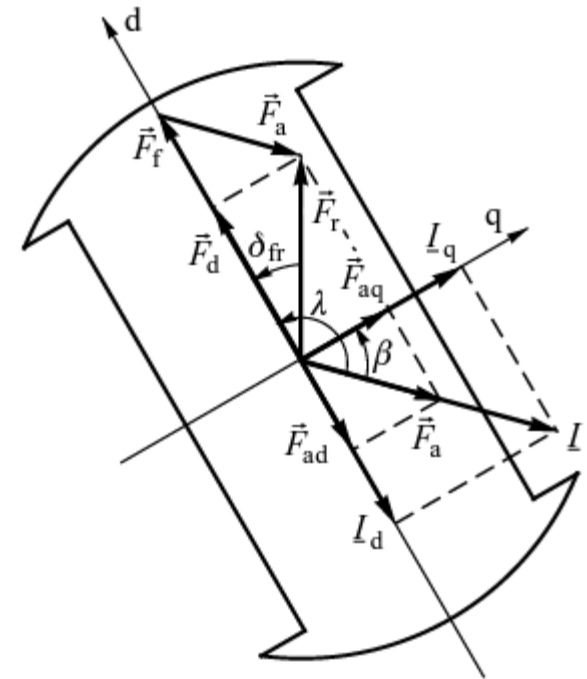- Non-uniform air gap, hence variable reluctance.
- $\rightarrow$  Decomposition of mmfs and current into d-component and q-component.
- Let  $X_{ad}$  and  $X_{aq}$  represent the direct-axis and quadrature-axis armature reaction reactances.



# Salient pole machines – 2 poles

- Resultant air gap emf:

$$\underline{E}_r = \underline{E}_f + \underline{E}_{aq} + \underline{E}_{ad} = \underline{E}_f - jX_{ad}\underline{I}_d - jX_{aq}\underline{I}_q.$$

- Resultant terminal voltage:

$$\begin{aligned}\underline{V}_g &= \underline{E}_r - jX_l\underline{I} - R\underline{I} = \underline{E}_f - jX_{ad}\underline{I}_d - jX_{aq}\underline{I}_q - jX_l(\underline{I}_d + \underline{I}_q) - R\underline{I} \\ &= \underline{E}_f - j(X_{ad} + X_l)\underline{I}_d - j(X_{aq} + X_l)\underline{I}_q - R\underline{I},\end{aligned}$$

$$\underline{E}_f = \underline{V}_g + jX_d\underline{I}_d + jX_q\underline{I}_q + R\underline{I},$$

$$\underline{E}_f = \underline{V}_g + R\underline{I} + jX_q\underline{I} + j(X_d - X_q)\underline{I}_d = \underline{E}_Q + j(X_d - X_q)\underline{I}_d,$$

Herein,  $\underline{E}_Q = \underline{V}_g + (R + jX_q)\underline{I}$ . and  $X_d$  and  $X_q$  are the direct- and quadrature-axis synchronous reactances.

- Note:  $X_d > X_q$  because the reluctance along the q-axis is highest.
- Note: for a round rotor,  $X_d = X_q$ , and  $E_Q = E_f$ .



# Phasor Diagram and Equivalent Circuit

d-axis:  $E_d = V_d + RI_d + X_q I_q = 0$

q-axis:  $E_q = V_q + RI_q - X_d I_d = E_f$ .

$$V_d = -V_g \sin \delta_g, \quad V_q = V_g \cos \delta_g$$
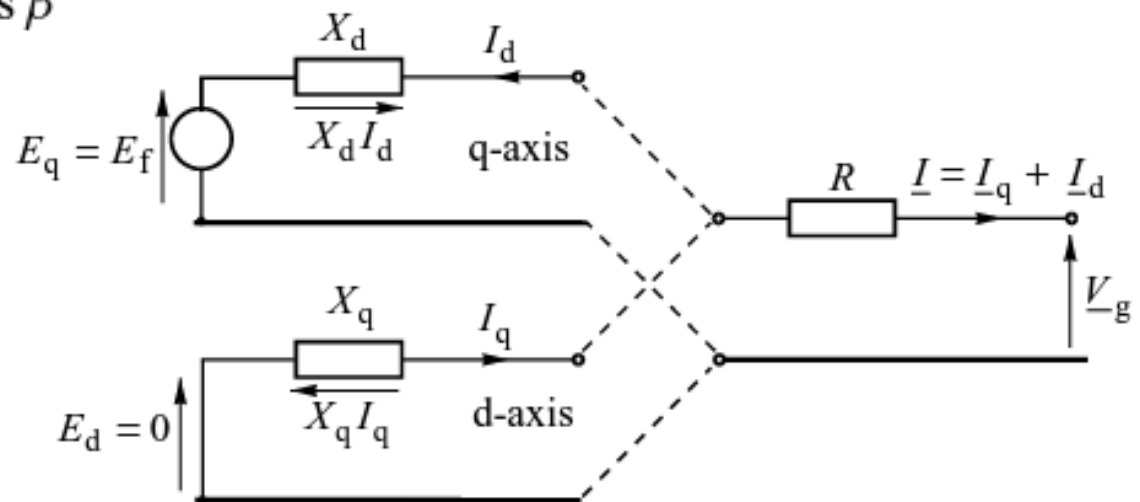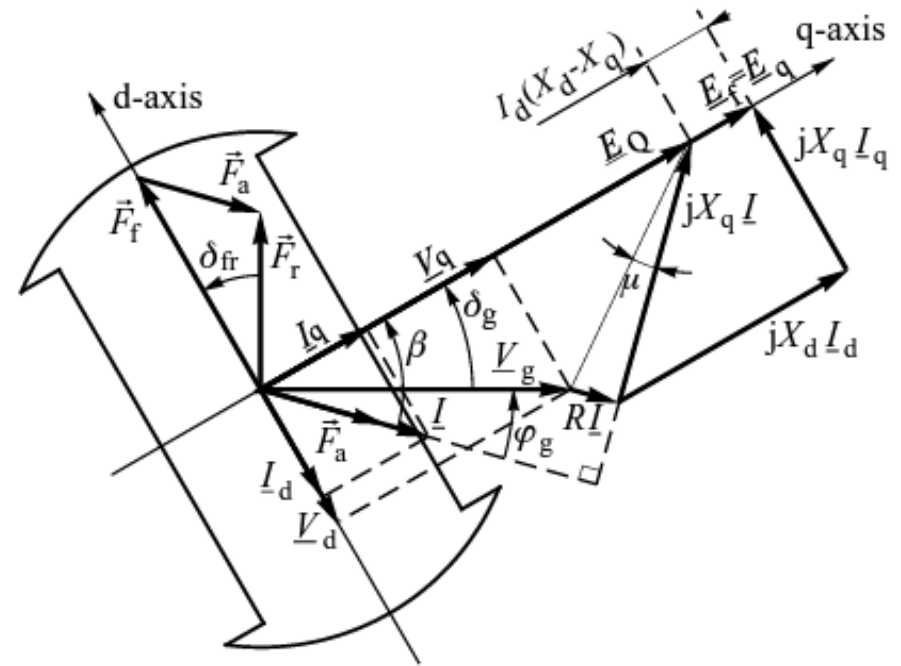
$$I_d = -I \sin \beta, \quad I_q = I \cos \beta$$



# Torque

- Electromagnetic torque of a generator with 2-pole salient rotor (see derivation on pp. 88)

$$\tau = \frac{\pi}{2} \Phi_f F_r \sin \delta_{fr} + \frac{\pi}{4} F_r^2 \frac{\Re_q - \Re_d}{\Re_q \Re_d} \sin 2\delta_{fr}.$$



Synchronous torque



Reluctance torque

# Generator-transformer unit



- The generator impedance is increased by the transformer impedance. For the round rotor machine;

$$\underline{V} = \underline{E}_f - jX_d \underline{I} - R \underline{I} - jX_T \underline{I} - R_T \underline{I} = \underline{E}_f - j(X_d + X_T) \underline{I} - (R + R_T) \underline{I},$$

- For the salient rotor machine

$$\begin{aligned} \underline{V}_g &= \underline{E}_f - jX_d \underline{I}_d - jX_q \underline{I}_q - R \underline{I} - X_T \underline{I} - R_T \underline{I} \\ &= \underline{E}_f - jX_d \underline{I}_d - jX_q \underline{I}_q - R \underline{I} - X_T (\underline{I}_d + \underline{I}_q) - R_T \underline{I}. \end{aligned}$$

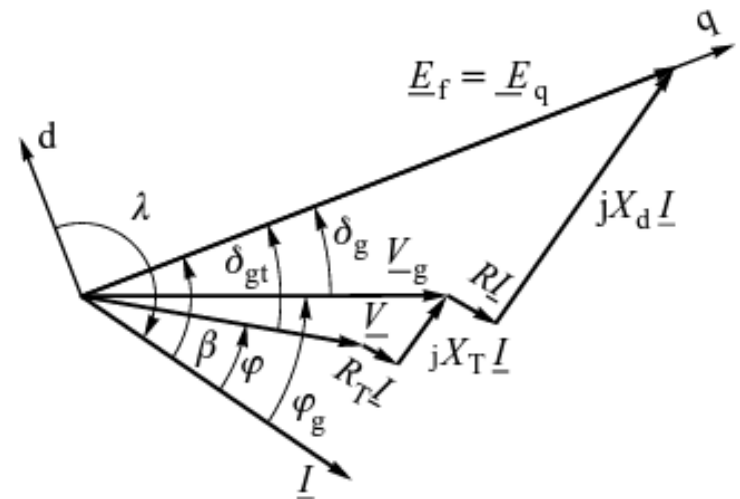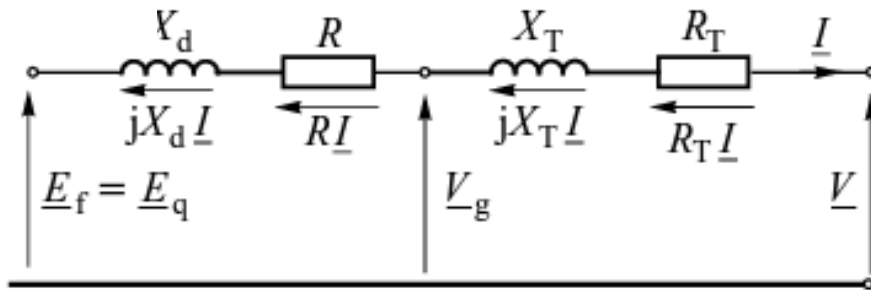Including network impedance is achieved by adding  $X_s$  and  $R_s$  in series.



# Real and reactive power of generator-transformer unit

- Real power (see pp. 91):  $P = V_d I_d + V_q I_q$        $z^2 = r^2 + x_d x_q$ .

$$P = \frac{E_q V}{z} \frac{x_q}{z} \sin \delta_{gt} + \frac{1}{2} \frac{V^2}{z} \frac{x_d - x_q}{z} \sin 2\delta_{gt} + \frac{E_q V}{z} \frac{r}{z} \cos \delta_{gt} - \frac{V^2}{z} \frac{r}{z}.$$

- For a round rotor machine and when neglecting the resistance:

$$P = \frac{E_q V}{x_d} \sin \delta_{gt}.$$

- Reactive power (see pp. 92):  $Q = V_d I_q - V_q I_d$

$$Q = \frac{E_q V}{z} \frac{x_q}{z} \cos \delta_{gt} - \frac{V^2}{z} \frac{x_d \sin^2 \delta_{gt} + x_q \cos^2 \delta_{gt}}{z} - \frac{E_q V}{z} \frac{r}{z} \sin \delta_{gt}.$$


- For a round rotor machine and when neglecting the resistance:

$$Q = \frac{E_q V}{x_d} \cos \delta_{gt} - \frac{V^2}{x_d}.$$


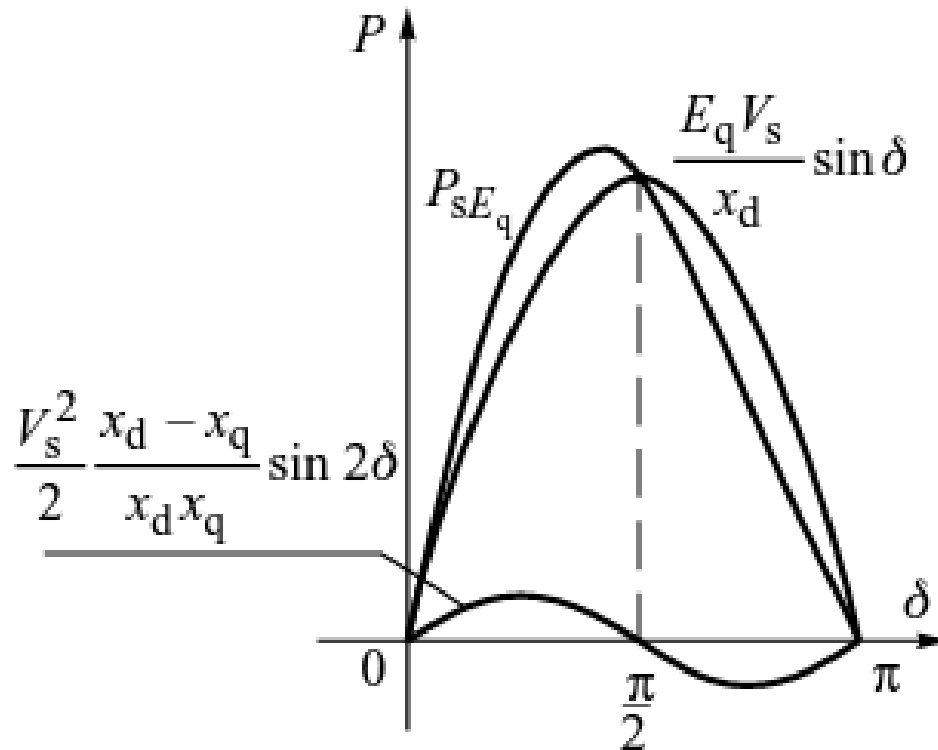
# Power-angle characteristic of generator with salient rotor


- When  $r$  is ignored and  $E_q$  is held constant, then the power contains two terms. The latter (i.e., reluctance term) deforms the sinusoid. Hence peak power occurs at an angle that is less than  $90^\circ$ .



# Homework # 4


- Consider a 25 kV, 230 MVA generator with salient-pole rotor. The per-unit values of  $R$ ,  $X_d$  and  $X_q$  are 0.05, 0.93 and 0.69, respectively. The generator is delivering  $0.6 + j0.3$  pu of complex power to the network and the terminal voltage is at 1 pu.
  - Determine the d-axis and q-axis components of the generator current, terminal voltage, and internal emf.
  - Calculate the active and reactive powers supplied by the generator using the expressions in the previous slides and compare to the above values.
  - Finally, determine the maximum power and corresponding angle  $\delta$  if the  $E$  and  $V$  are held constant.
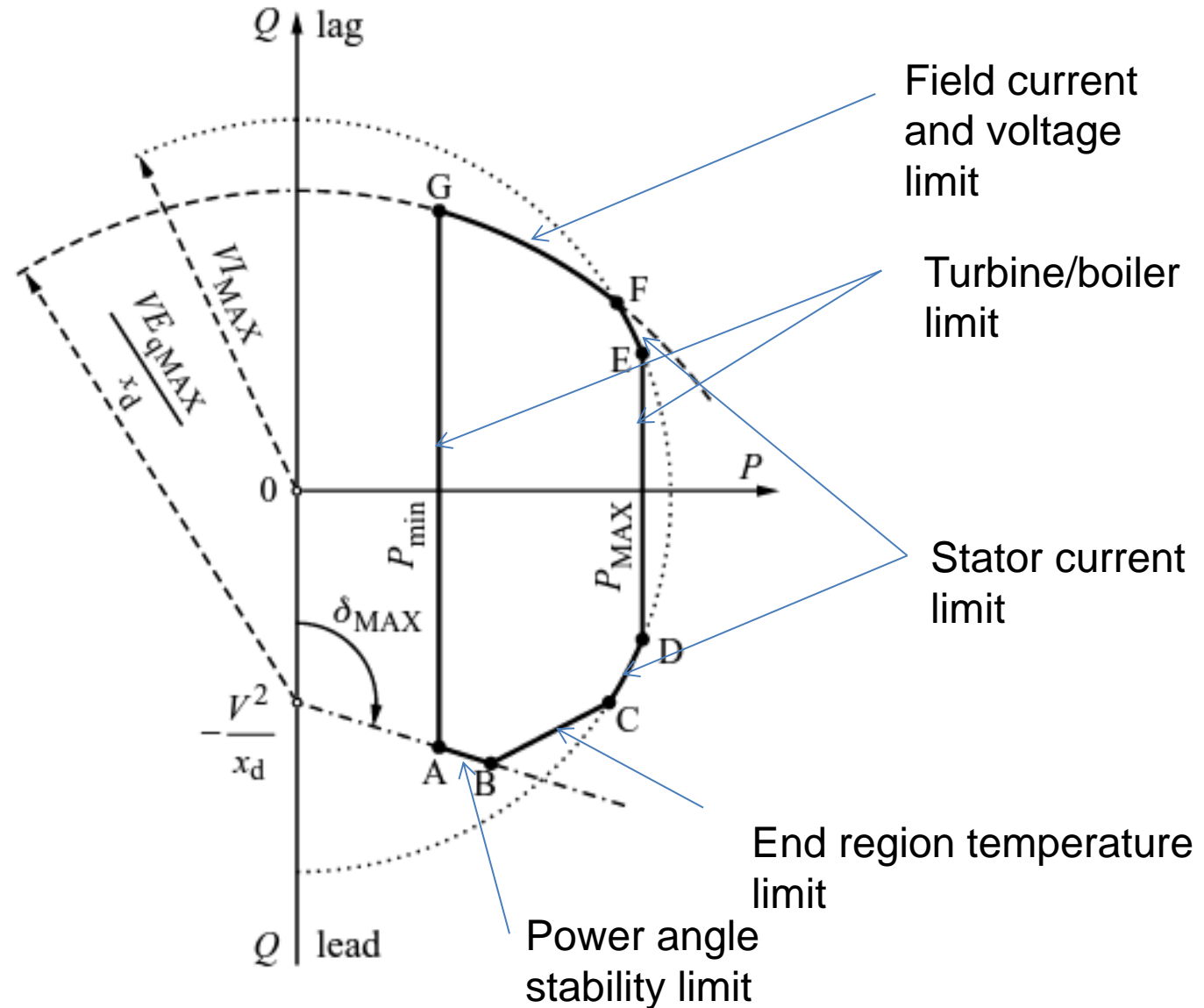
# Real and reactive power capability curves


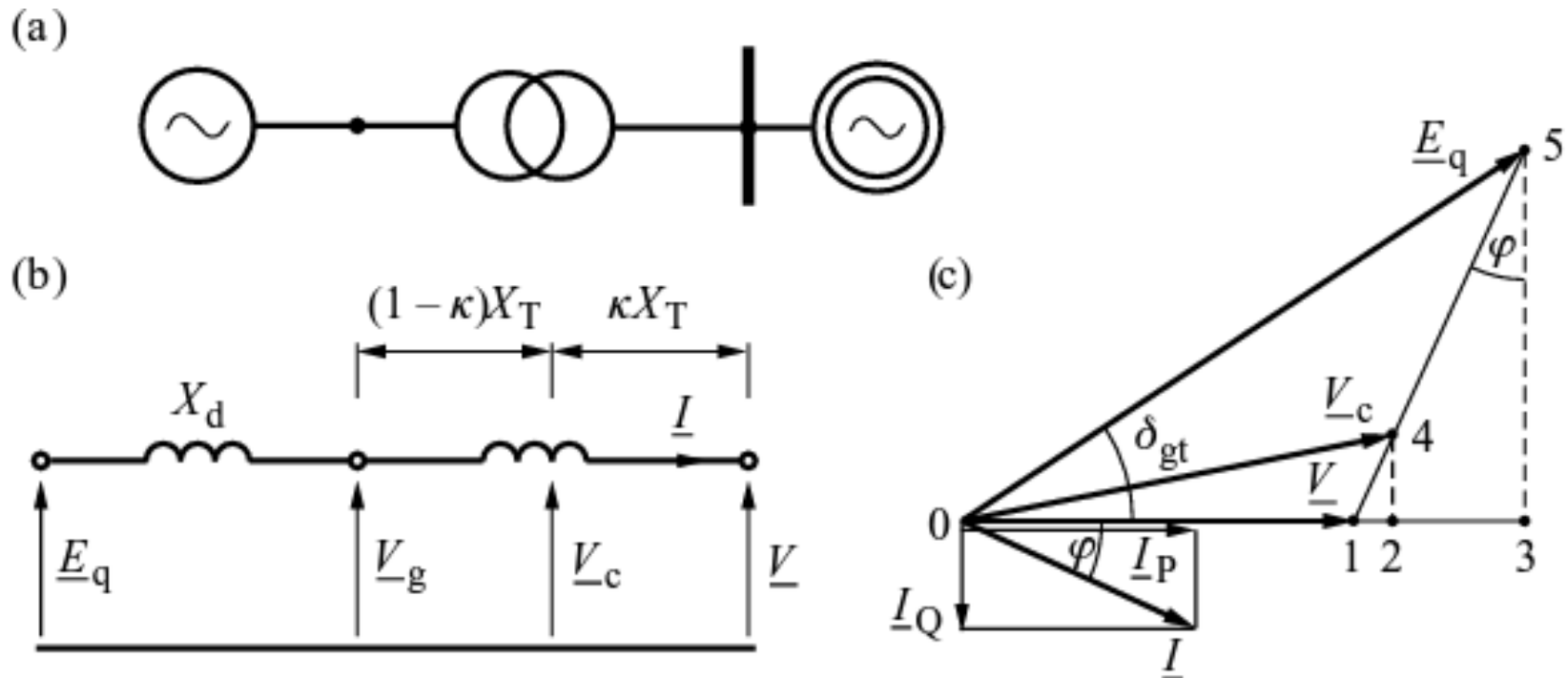
# Voltage-reactive power capability curve


- Consider a round rotor generator connected to a power system through a transformer.
- Voltage is to be regulated at a fictitious point ( $V_c$ ) within the transformer.




# $V(Q)$ Generator Curves

- Curve I: Field current less than its maximum value (eqn. 3.105)
- Curve II: Maximum field current (eqn. 3.106)
- Curve III: Maximum power angle (eqn. 3.107)
- Curve IV: Maximum stator current (eqn. 3.108)

(a)  $P = 0$

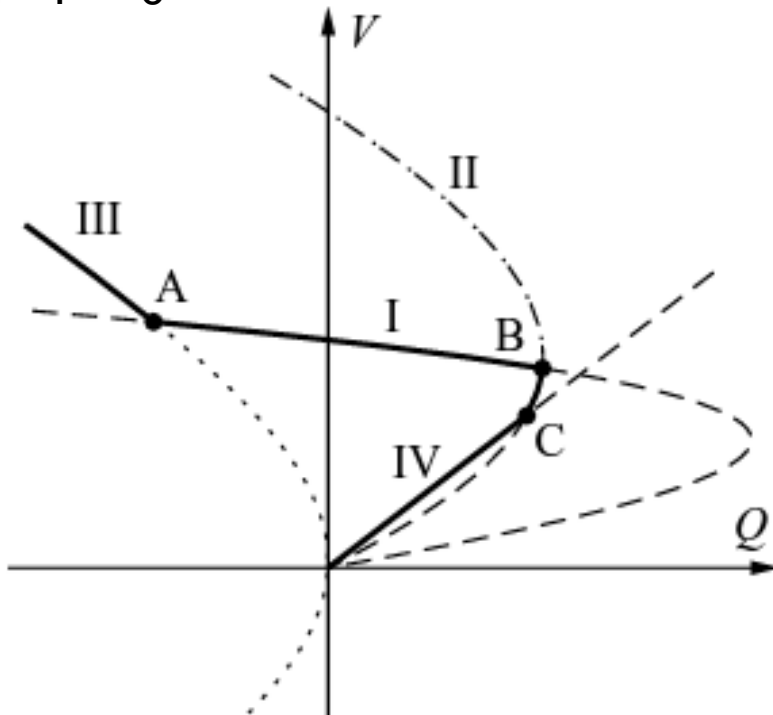


(b)  $P \neq 0$

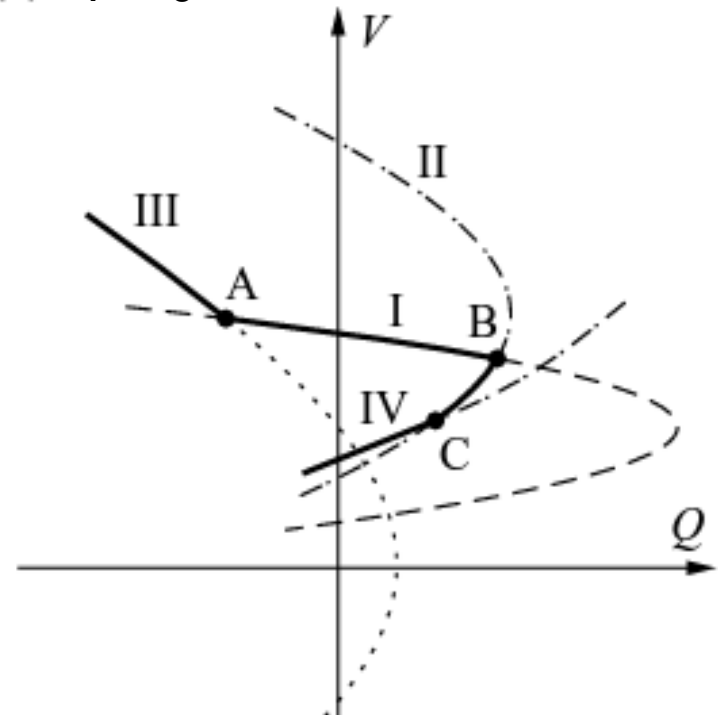
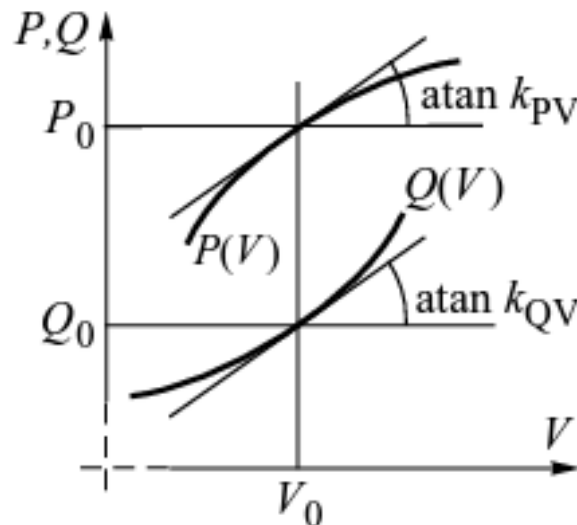
# Power System Loads



- Only simple static composite load models are described (dynamic models will be seen in later chapters).
- The active and reactive power demand of a static composite load depends on the voltage and frequency.
- *Voltage and frequency sensitivity*: slope of load-voltage or load-frequency characteristics (see fig. below)

$$k_{PV} = \frac{\Delta P / P_0}{\Delta V / V_0}, \quad k_{QV} = \frac{\Delta Q / Q_0}{\Delta V / V_0}, \quad k_{Pf} = \frac{\Delta P / P_0}{\Delta f / f_0}, \quad k_{Qf} = \frac{\Delta Q / Q_0}{\Delta f / f_0},$$



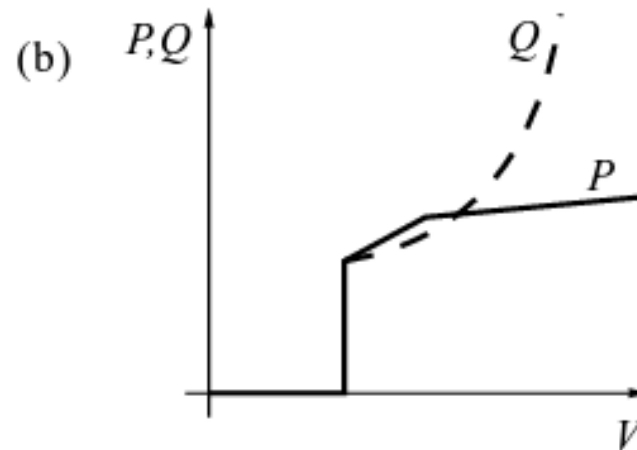
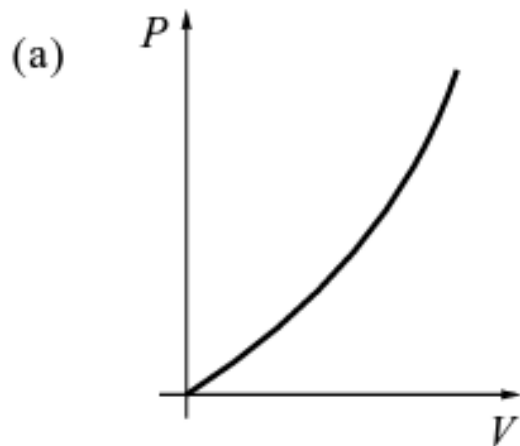
# Lighting and heating load characteristics

- Voltage characteristics of incandescent and fluorescent bulbs (see fig. below)
- Heating load equipped with thermostat is considered a constant power load. If not, its is considered a constant resistance load.



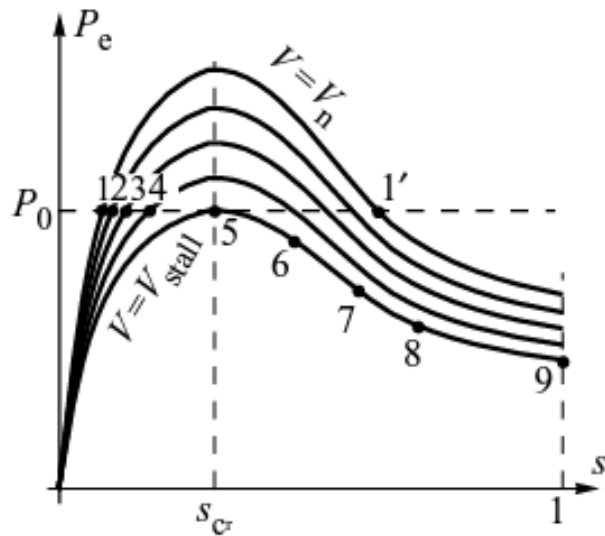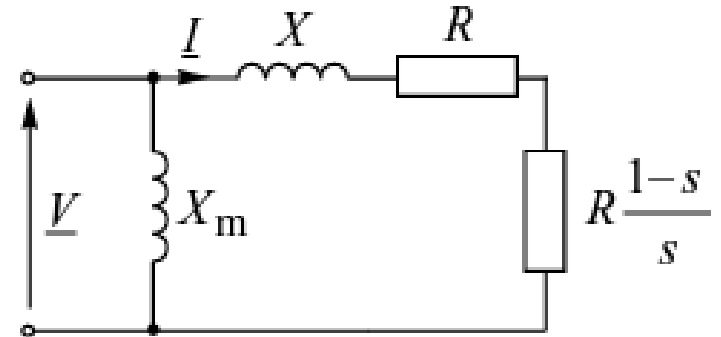
# Induction Motors


- Equivalent circuit with stator impedance neglected.
- Voltage characteristic under constant load torque.



(a)

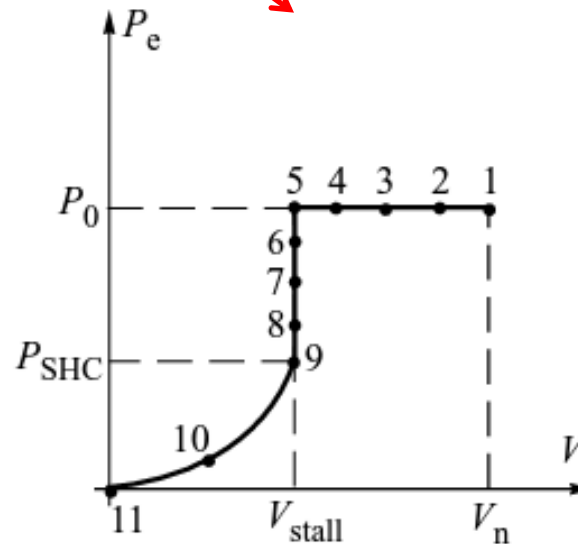


(b)

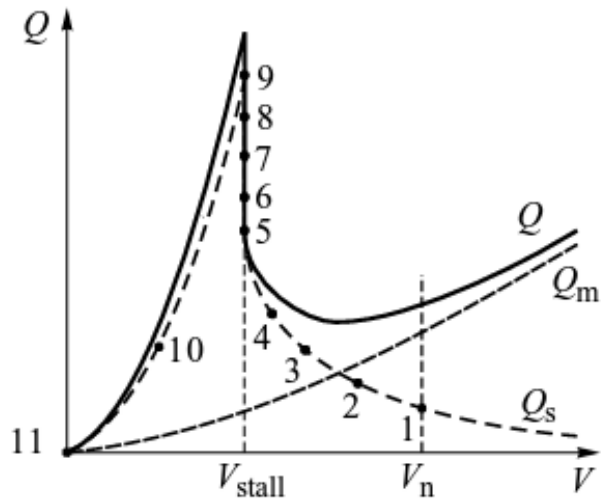


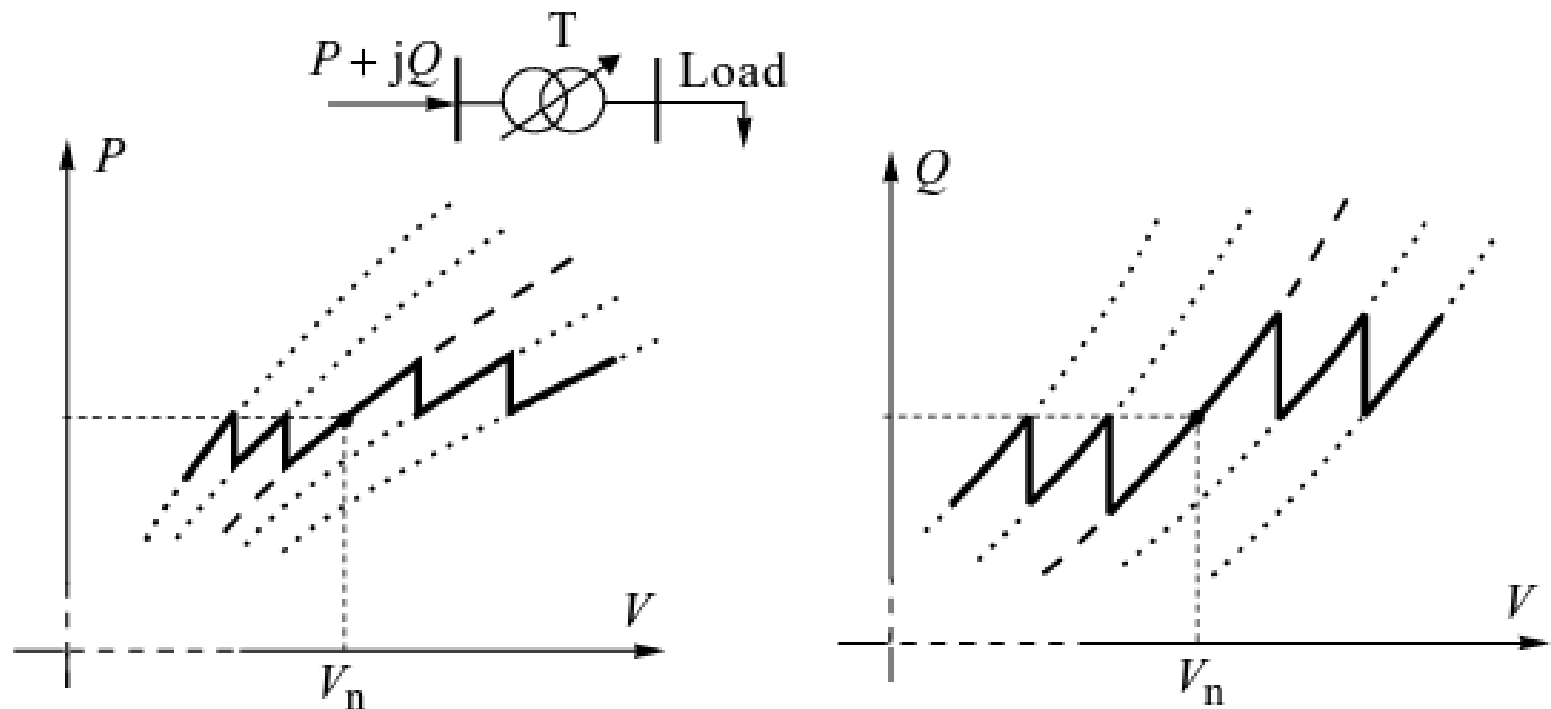
# Influence of tap-changing transformer on composite load voltage characteristics



# ZIP and Exponential and Frequency-Dependent Load Models

- ZIP model:

$$P = P_0 \left[ a_1 \left( \frac{V}{V_0} \right)^2 + a_2 \left( \frac{V}{V_0} \right) + a_3 \right]$$
$$Q = Q_0 \left[ a_4 \left( \frac{V}{V_0} \right)^2 + a_5 \left( \frac{V}{V_0} \right) + a_6 \right],$$

- Exponential model:  $P = P_0 \left( \frac{V}{V_0} \right)^{n_p}$  and  $Q = Q_0 \left( \frac{V}{V_0} \right)^{n_q}$ ,

$$P = P(V) \left[ 1 + k_{\text{Pf}} \frac{\Delta f}{f_0} \right]$$

- Frequency dependent model:

$$Q = Q(V) \left[ 1 + k_{\text{Qf}} \frac{\Delta f}{f_0} \right],$$

# Network Equations

- Bus admittance matrix

$$\begin{bmatrix} \underline{I}_1 \\ \vdots \\ \underline{I}_i \\ \vdots \\ \underline{I}_N \end{bmatrix} = \begin{bmatrix} \underline{Y}_{11} & \cdots & \underline{Y}_{1i} & \cdots & \underline{Y}_{1N} \\ \vdots & \ddots & \vdots & & \vdots \\ \underline{Y}_{i1} & \cdots & \underline{Y}_{ii} & \cdots & \underline{Y}_{iN} \\ \vdots & & \vdots & & \vdots \\ \underline{Y}_{N1} & \cdots & \underline{Y}_{Ni} & \cdots & \underline{Y}_{NN} \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \vdots \\ \underline{V}_i \\ \vdots \\ \underline{V}_N \end{bmatrix} \quad \text{or} \quad \underline{I} = \underline{YV}.$$

- Bus impedance matrix

$$\begin{bmatrix} \underline{V}_1 \\ \vdots \\ \underline{V}_i \\ \vdots \\ \underline{V}_N \end{bmatrix} = \begin{bmatrix} \underline{Z}_{11} & \cdots & \underline{Z}_{1i} & \cdots & \underline{Z}_{1N} \\ \vdots & \ddots & \vdots & & \vdots \\ \underline{Z}_{i1} & \cdots & \underline{Z}_{ii} & \cdots & \underline{Z}_{iN} \\ \vdots & & \vdots & & \vdots \\ \underline{Z}_{N1} & \cdots & \underline{Z}_{Ni} & \cdots & \underline{Z}_{NN} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \vdots \\ \underline{I}_i \\ \vdots \\ \underline{I}_N \end{bmatrix} \quad \text{or} \quad \underline{V} = \underline{ZI},$$

# Power flow equations

$$\underline{I}_i = \underline{Y}_{ii} \underline{V}_i + \sum_{j=1; j \neq i}^N \underline{Y}_{ij} \underline{V}_j,$$

$$\underline{S}_i = P_i + jQ_i = \underline{V}_i \underline{I}_i^* = V_i e^{j\delta_i} \left[ Y_{ii} V_i e^{-j(\delta_i + \theta_{ii})} + \sum_{j=1; j \neq i}^N V_j Y_{ij} e^{-j(\delta_j + \theta_{ij})} \right]$$

$$= V_i^2 Y_{ii} e^{-j\theta_{ii}} + V_i \sum_{j=1; j \neq i}^N V_j Y_{ij} e^{j(\delta_i - \delta_j - \theta_{ij})}.$$

$$P_i = V_i^2 Y_{ii} \cos \theta_{ii} + \sum_{j=1; j \neq i}^N V_i V_j Y_{ij} \cos(\delta_i - \delta_j - \theta_{ij})$$

$$Q_i = -V_i^2 Y_{ii} \sin \theta_{ii} + \sum_{j=1; j \neq i}^N V_i V_j Y_{ij} \sin(\delta_i - \delta_j - \theta_{ij}).$$