

Diode Rectifiers

EE 442-642

Half-Bridge Rectifier Circuit: R and R-L Load

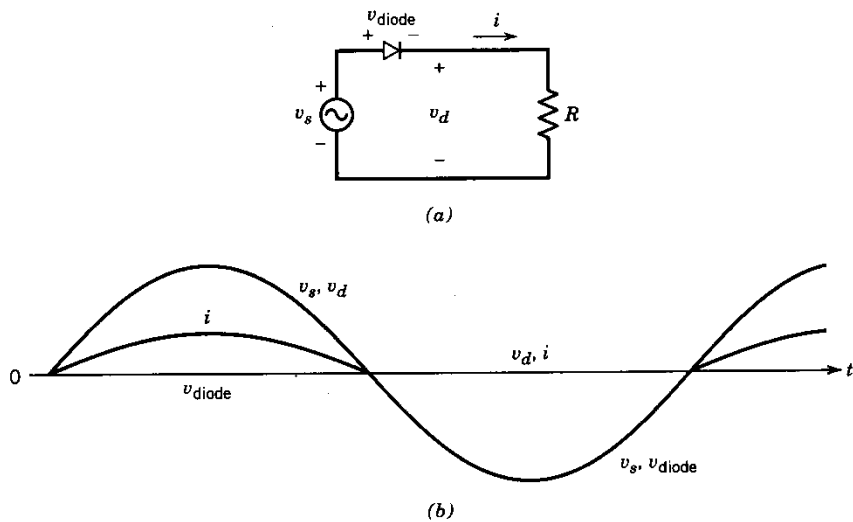


Figure 5-2 Basic rectifier with a load resistance.


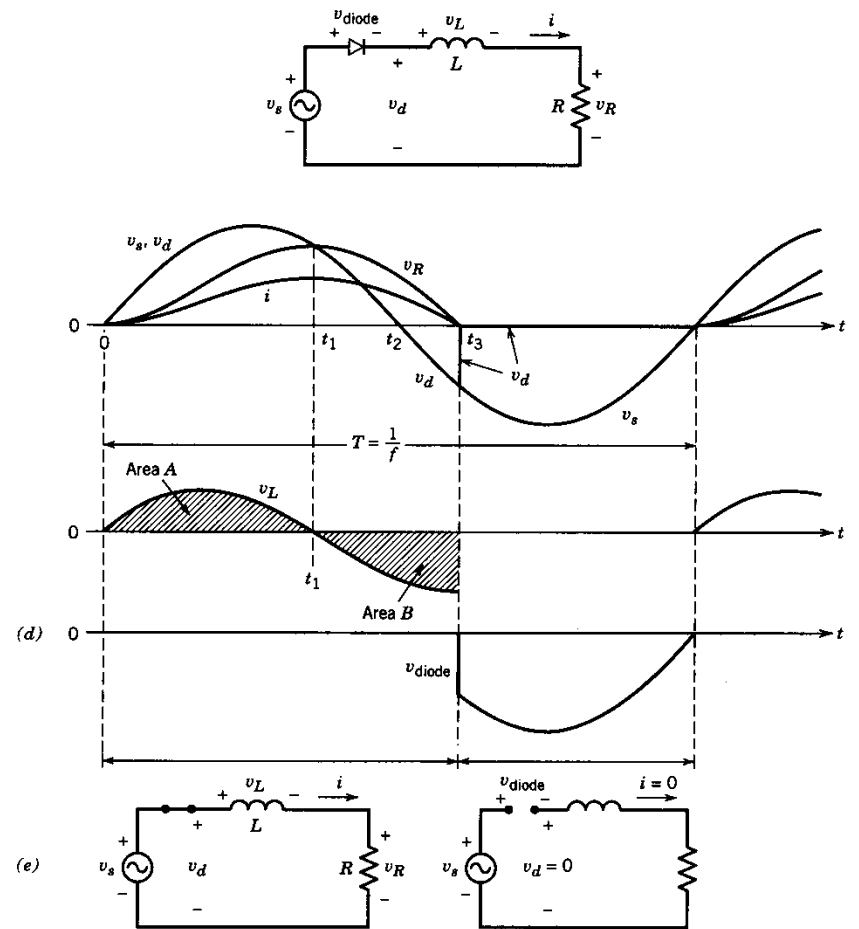



Figure 5-3 Basic rectifier with an inductive load.

Current continues to flow for a while even after the input voltage has gone negative.

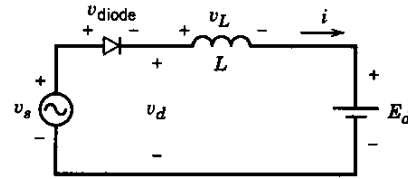
Half Bridge Rectifier Circuit: Load with dc back-emf




(a)

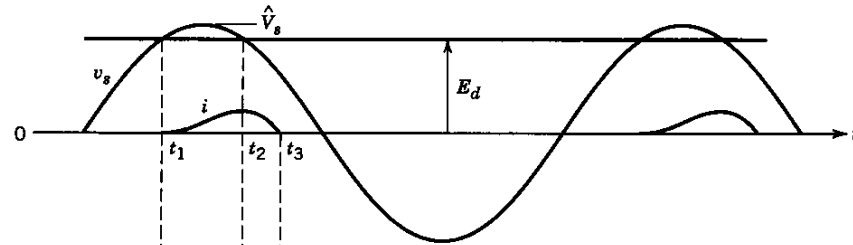

(b)

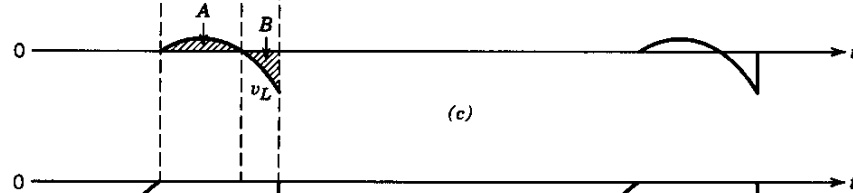


(c)

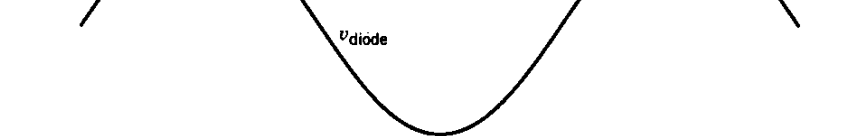


(d)

- Current begins to flow when the input voltage exceeds the dc back-emf.
- Current continues to flow for a while even after the input voltage has gone below the dc back-emf.


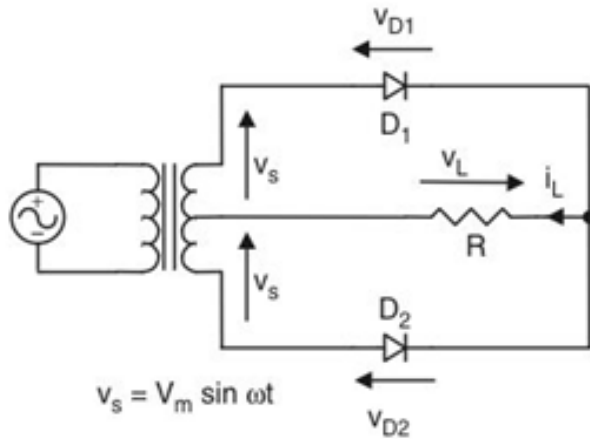
Full-wave Rectifier with Center tap Transformer



- The DC currents of the two half-wave rectifiers are equal and opposite, Hence, there is no DC current for creating a transformer core saturation problem.
- Each diode carries half of the load average current, but the same peak load current.
- Note that the V_{RRM} rating of the diodes must be chosen to be higher than $2V_m$ to avoid reverse breakdown.
- The center-tap transformer is considered bulky with additional losses.

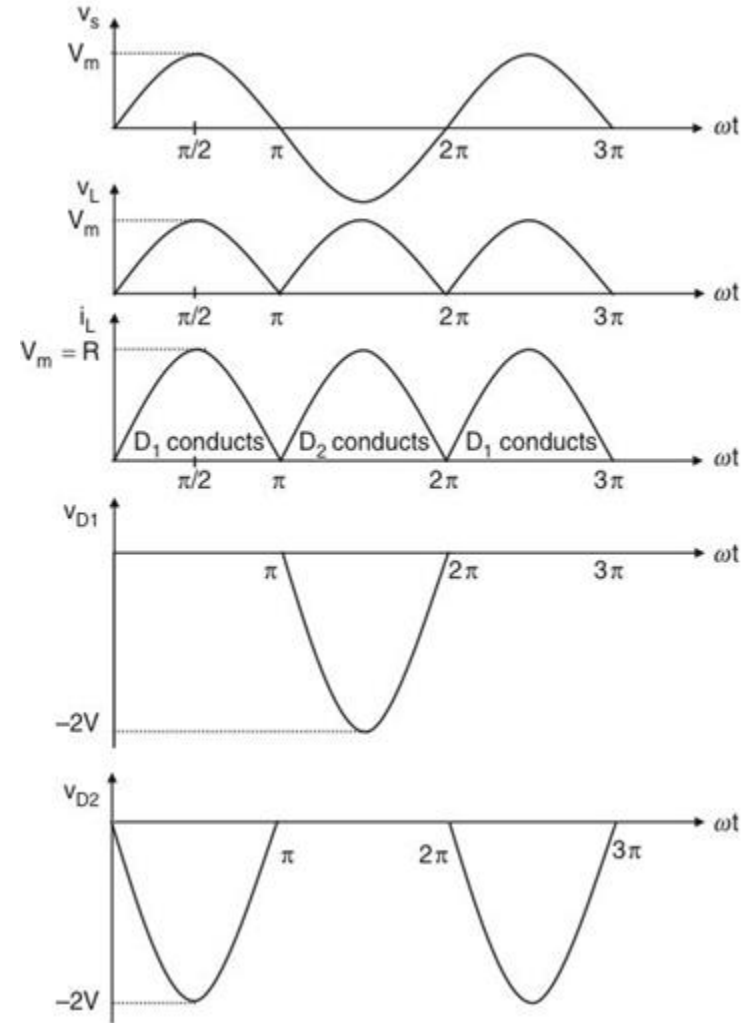

Full Bridge Rectifier – Simple R Load

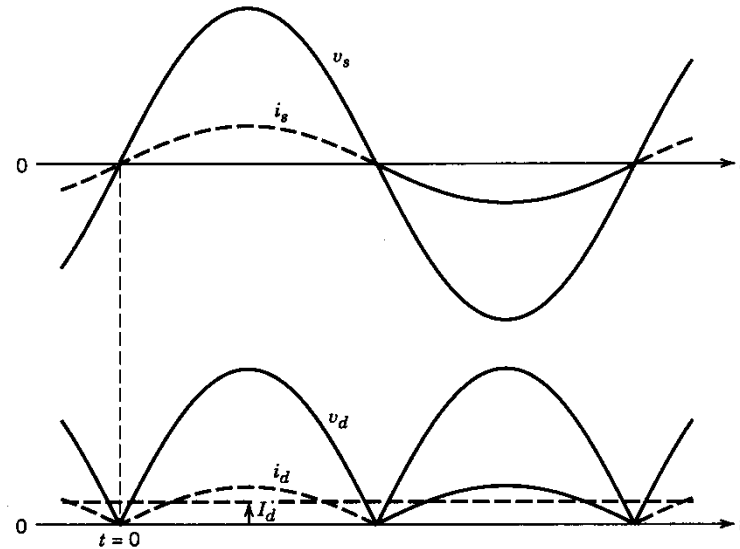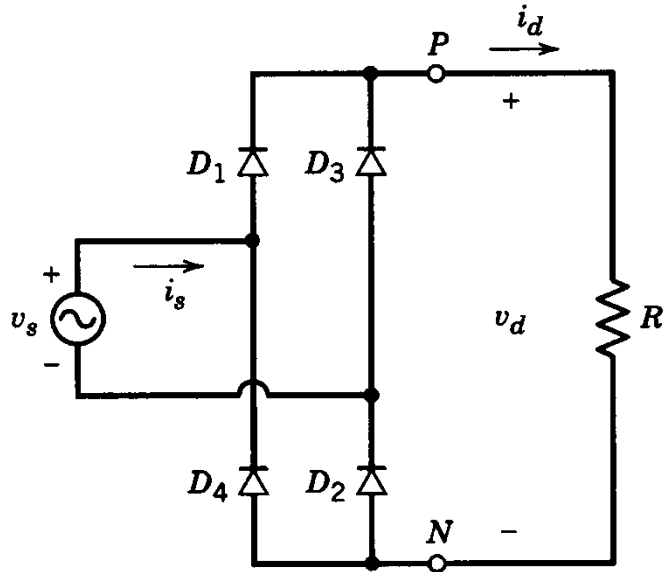

Average value of output voltage: $V_{do} = (2\sqrt{2} / \pi)V_s \approx 0.9V_s = (2 / \pi)V_m = 0.637V_m$

where V_s and V_m are the RMS and peak values of input voltage.


Rectification Ratio = $P_{dc}/P_{ac} = 0.81$ or 81%

Form Factor (FF) of DC side voltage (or current) = $V_{rms}/V_{dc} = 1.11$

Ripple Factor = rms value of AC component/DC component = $(FF^2-1)^{1/2} = 0.48$

Filters

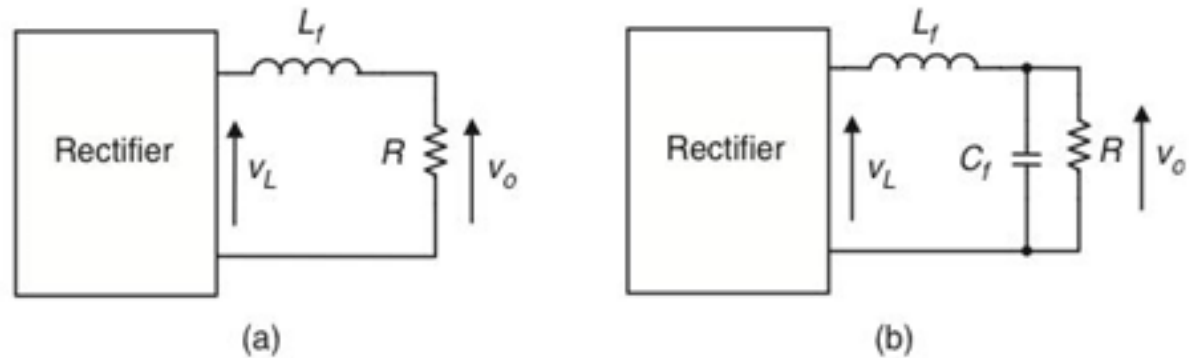- Filters are employed in rectifier circuits for smoothing out the dc output voltage of the load.




- Ripple Reduction Factor at f_r : $\frac{v_o}{v_L} = \frac{R}{\sqrt{R^2 + (2\pi f_r L_f)^2}}$ $\frac{v_o}{v_L} = \left| \frac{1}{1 - (2\pi f_r)^2 L_f C_f} \right|$

$$\int \sin b_1 x \sin b_2 x \, dx = \frac{\sin((b_2 - b_1)x)}{2(b_2 - b_1)} - \frac{\sin((b_1 + b_2)x)}{2(b_1 + b_2)} + C \quad (\text{for } |b_1| \neq |b_2|)$$

$$\int \sin a_1 x \cos a_2 x \, dx = -\frac{\cos((a_1 - a_2)x)}{2(a_1 - a_2)} - \frac{\cos((a_1 + a_2)x)}{2(a_1 + a_2)} + C \quad (\text{for } |a_1| \neq |a_2|)$$

Inductor DC Filter

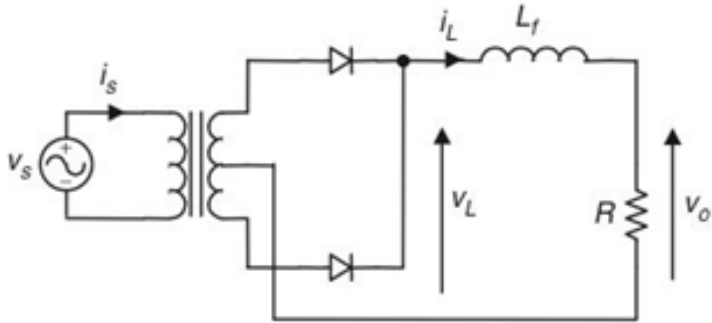

- Minimum value of inductance required to maintain a continuous current is known as the critical inductance L_C :


$$\text{Full-wave } L_C = \frac{R}{6\pi f_i}$$

- The choice of the input inductance depends on the required ripple factor. Ripple voltage of a rectifier without filtering:


$$v_{L_n} = \frac{-4V_m}{\pi(n^2 - 1)} \quad \text{RF} = \sqrt{2 \sum_{n=2,4,8} \left(\frac{1}{n^2 - 1} \right)^2}$$

- Considering only the lowest-order harmonic ($n = 2$), the output ripple factor of a simple inductor-input dc filter is
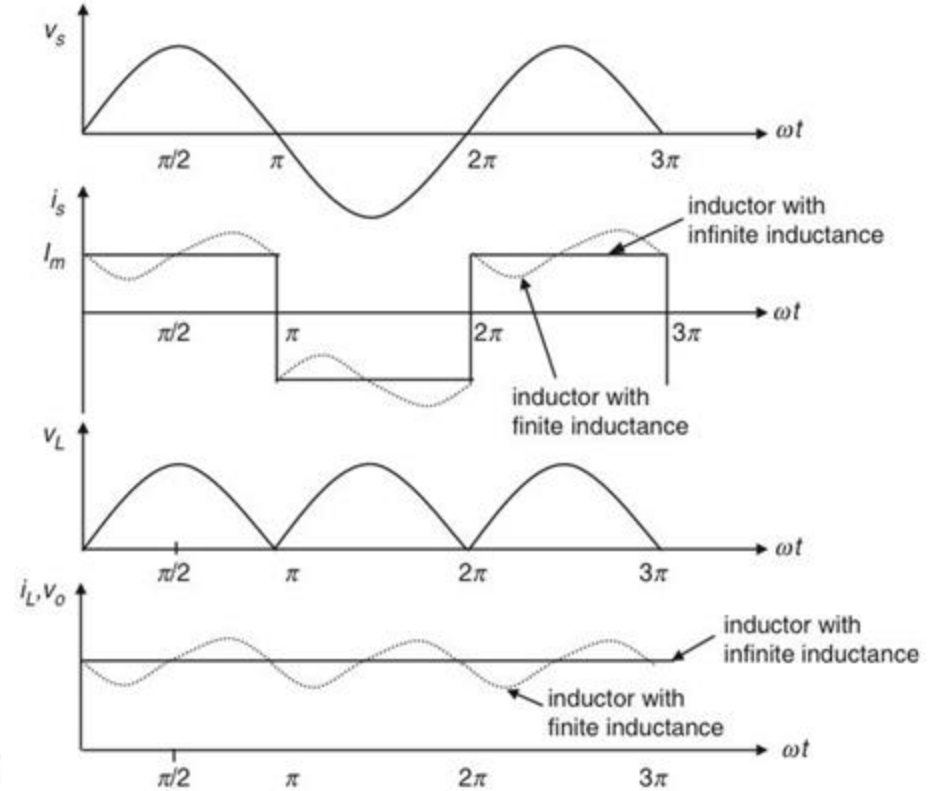
$$\text{Filtered } \text{RF} = \frac{0.4714}{\sqrt{1 + (4\pi f_i L_f / R)^2}}$$




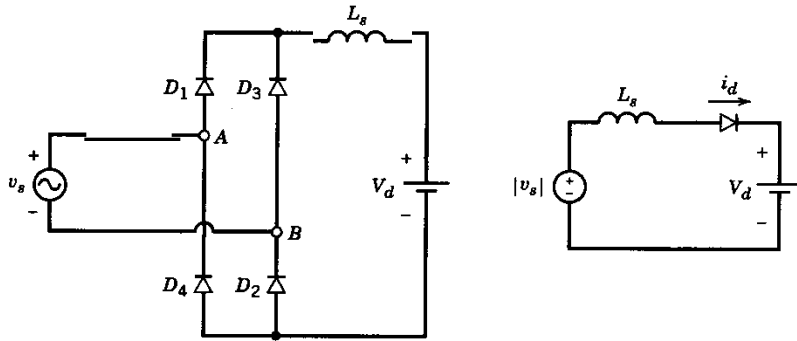Full Bridge Rectifier with dc-side Voltage




(a)

(b)



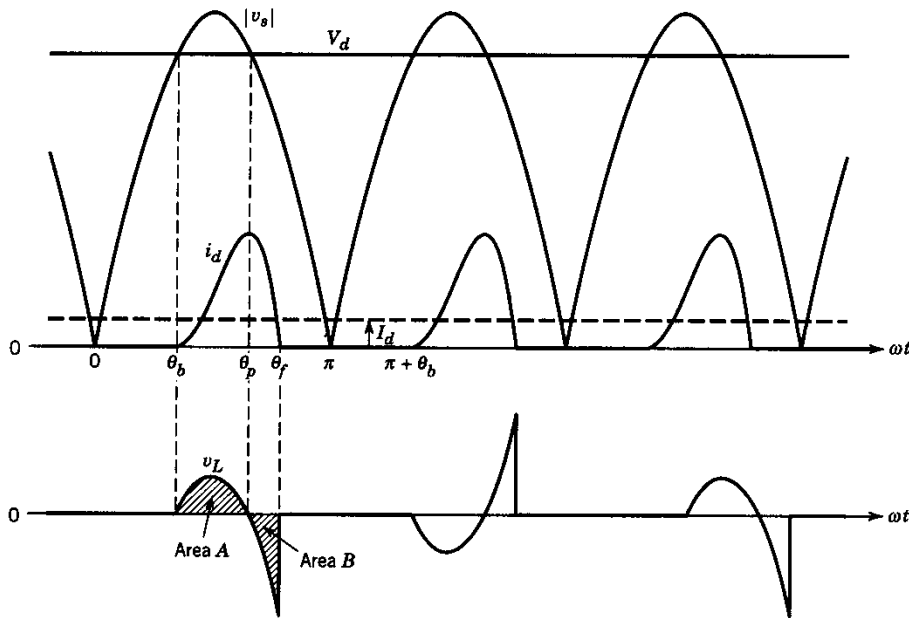


(c)

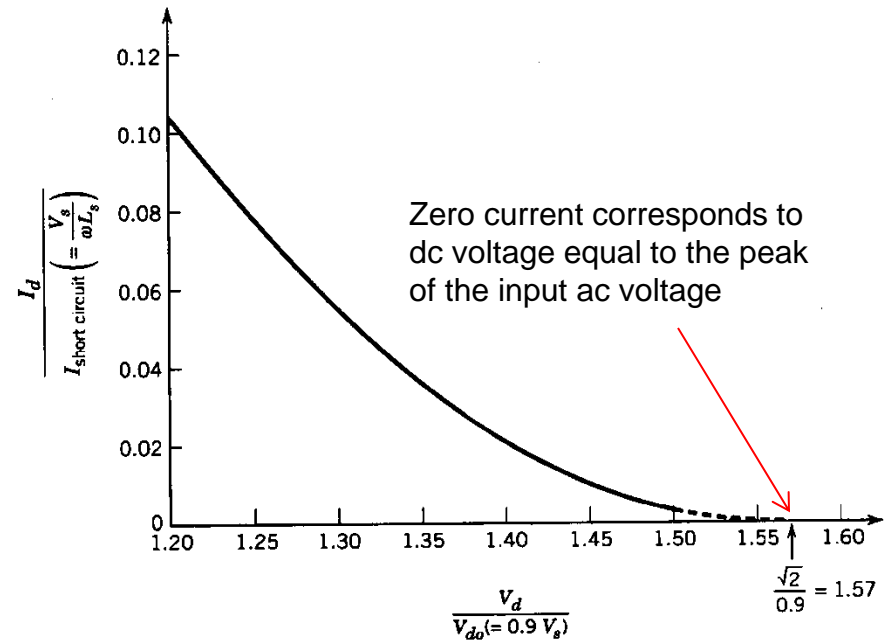Average value of DC-side current (obtained numerically):



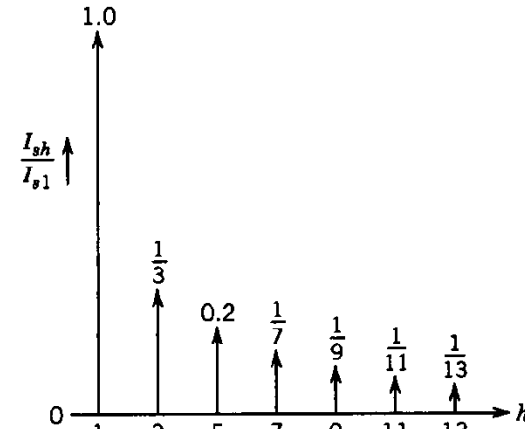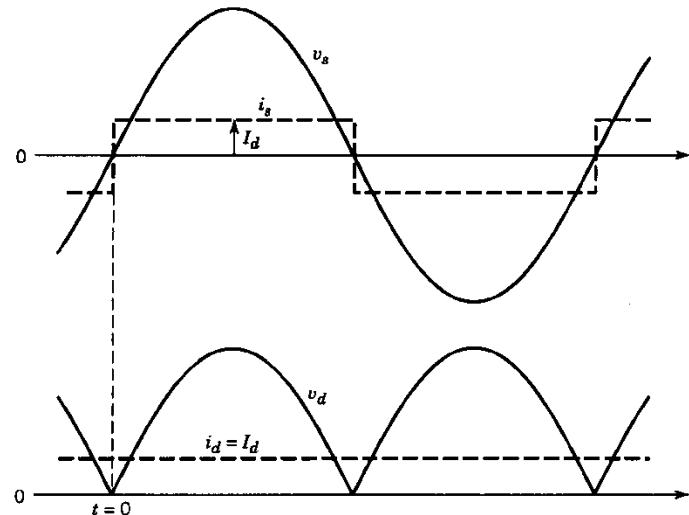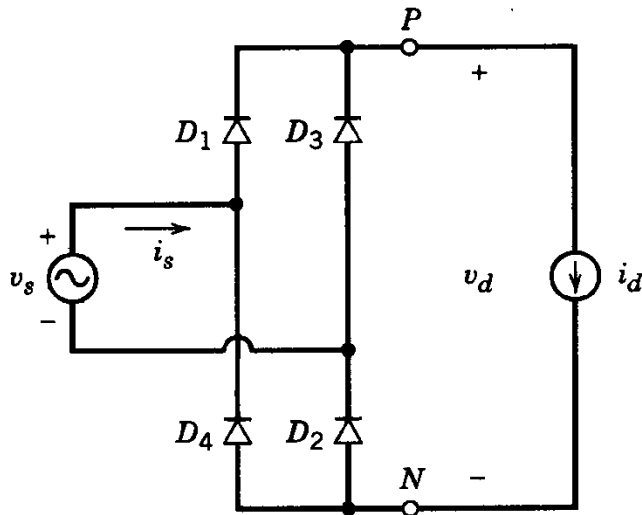Full Bridge Rectifier – Simple Constant Load Current



RSM value of source current

$$I_s = I_d$$

RMS value of fundamental current

$$I_{s1} = (2\sqrt{2} / \pi) I_d \approx 0.9 I_d$$

RMS value of harmonic current

$$I_{sh} = I_{s1} / h, \quad h = 3, 5, 7, \dots$$

Current THD

$$THD = 100[\sqrt{(\pi^2 / 8) - 1}] = 48.43\%$$


Displacement Power Factor

$$DPF = 1$$

Power Factor

$$PF = 0.9$$

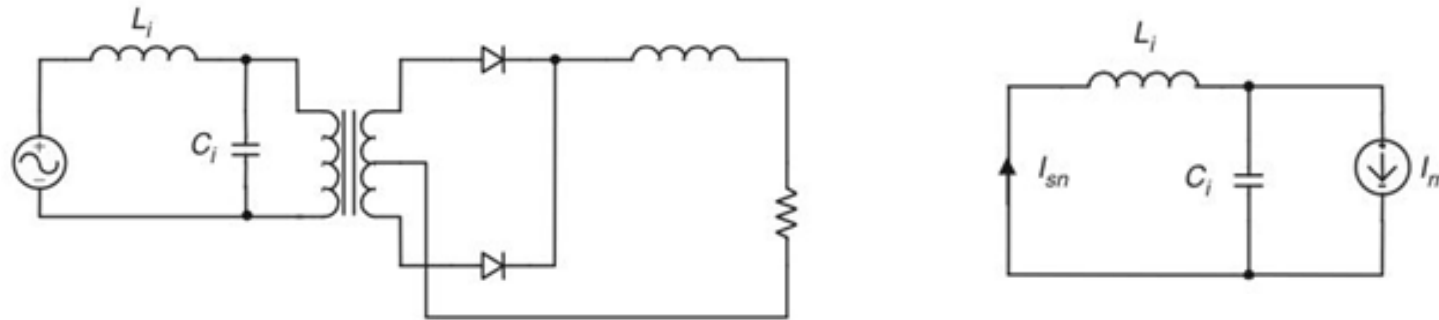Full Bridge Rectifier – Simple Constant Load Current (AC-side filtering)





RMS value of harmonic source current

$$I_{sn} = \left| \frac{1}{1 - (2n\pi f_i)^2 L_i C_i} \right| I_m$$

THD of Source Current:

$$\text{THD} = \sqrt{\sum_{n=3,5} \frac{1}{n^2} \left| \frac{1}{1 - (2n\pi f_i)^2 L_i C_i} \right|^2}$$

Diode-Rectifier with a Capacitor Filter

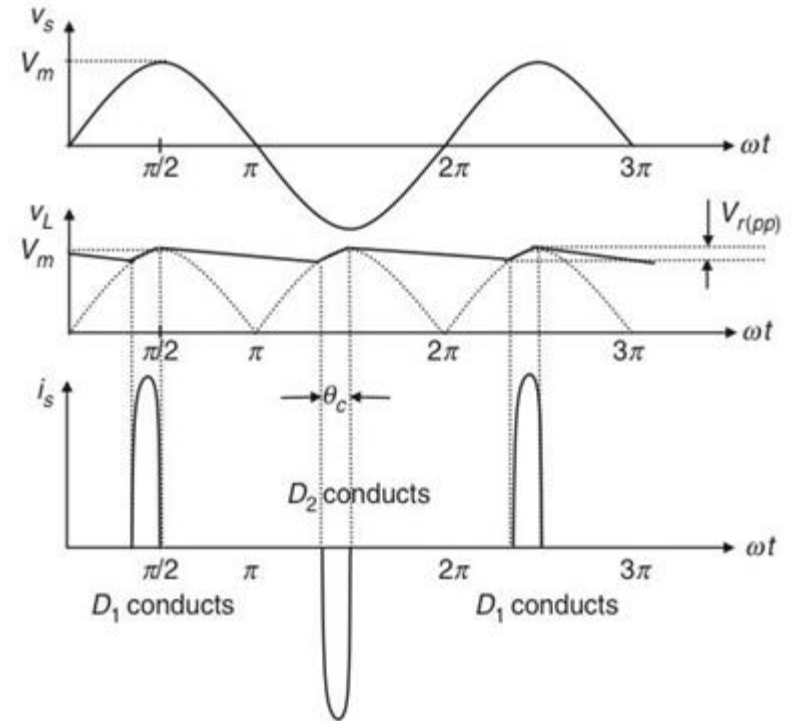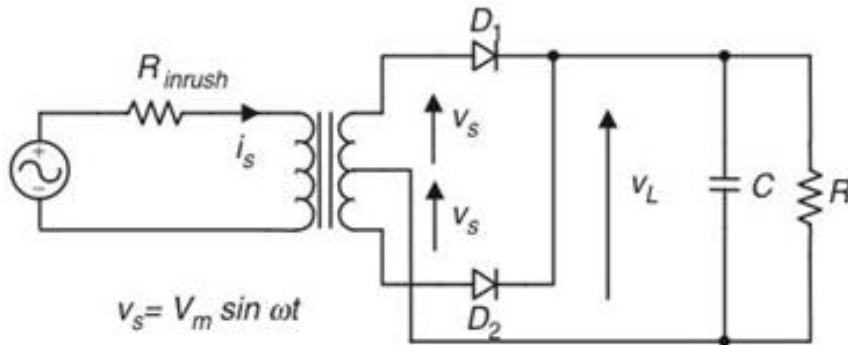

- Approximate value of peak-to-peak ripple:

$$V_{r(pp)} = \frac{V_m}{f_r RC}$$

- Average output voltage:

$$V_{dc} = V_m \left(1 - \frac{1}{2f_r RC} \right)$$

- RMS value of output ripple voltage:



$$V_{ac} = \frac{V_m}{2\sqrt{2}f_r RC}$$

- Ripple Factor:

$$RF = \frac{1}{\sqrt{2} (2f_r RC - 1)}$$

- Inrush resistance R_{inrush} is sometimes needed to limit the initial inrush current to a value below that of the diodes. It is usually placed on the DC side, then shorted out afterwards.
- In many cases, R_{inrush} is not needed if the Equivalent Series Resistance of the capacitor and cable/transformer wire resistance are sufficiently large.

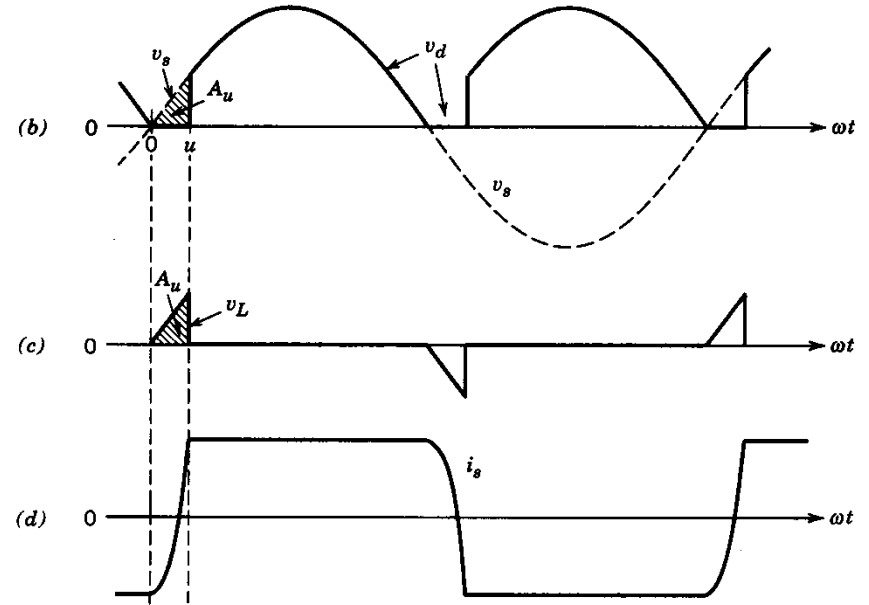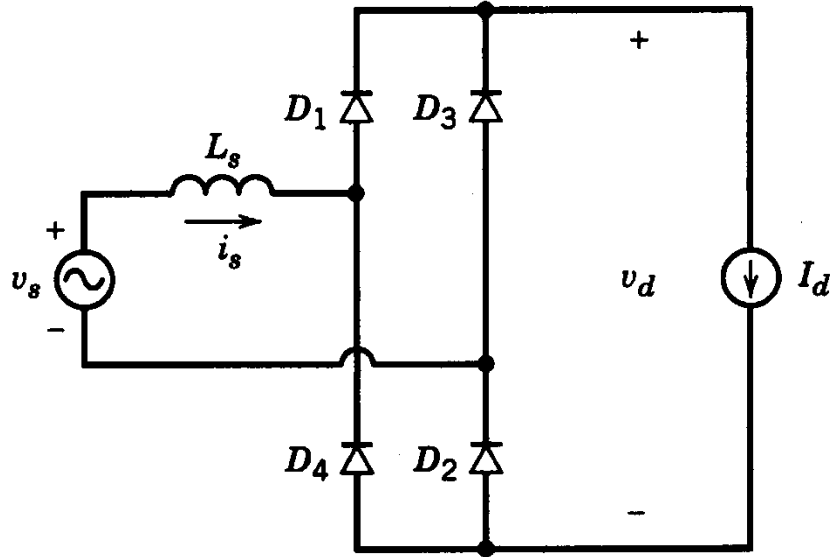Diode-Rectifier Bridge with AC-Side Inductance




Commutation angle:

$$\cos \mu = 1 - \frac{2\omega L_s I_d}{\sqrt{2}V_s}$$

Average of DC-side voltage:


$$V_d = 0.9V_s - \frac{2\omega L_s I_d}{\pi}$$

Voltage Distortion at PCC

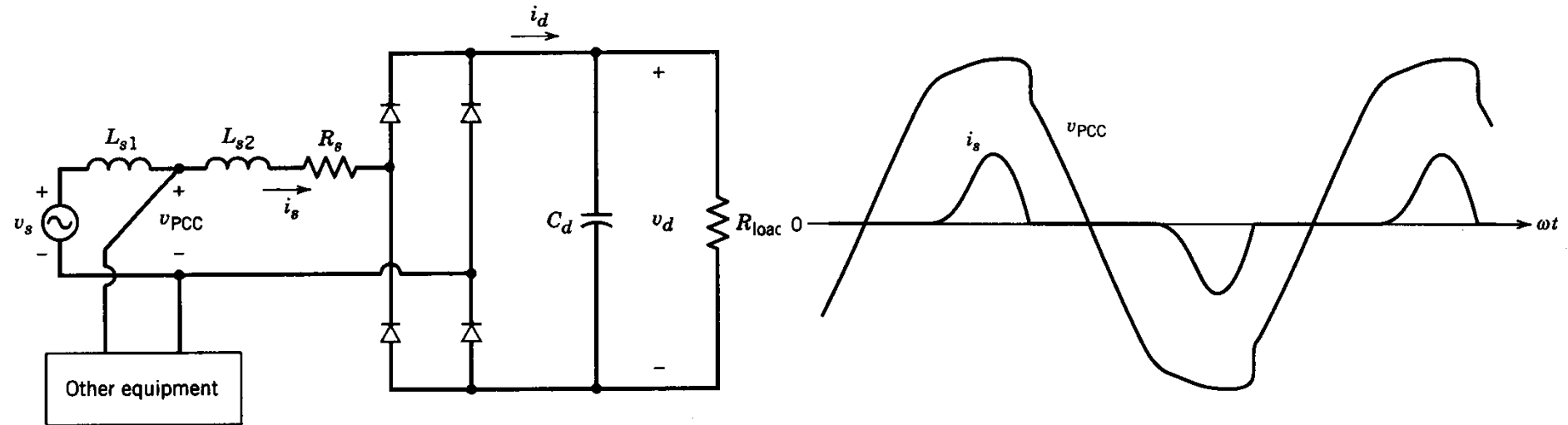


- PCC is the point of common coupling
- Distorted current flow results in distorted voltage

Dual Voltage Rectifier

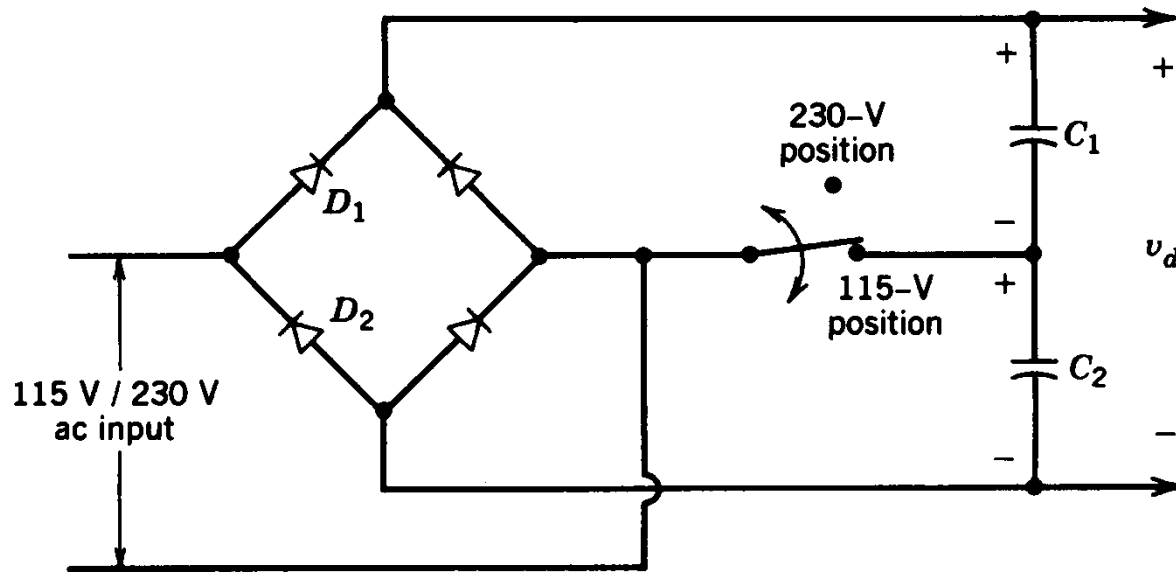

- In 115-V position, one capacitor at-a-time is charged from the input.


Three-Phase, Four-Wire System

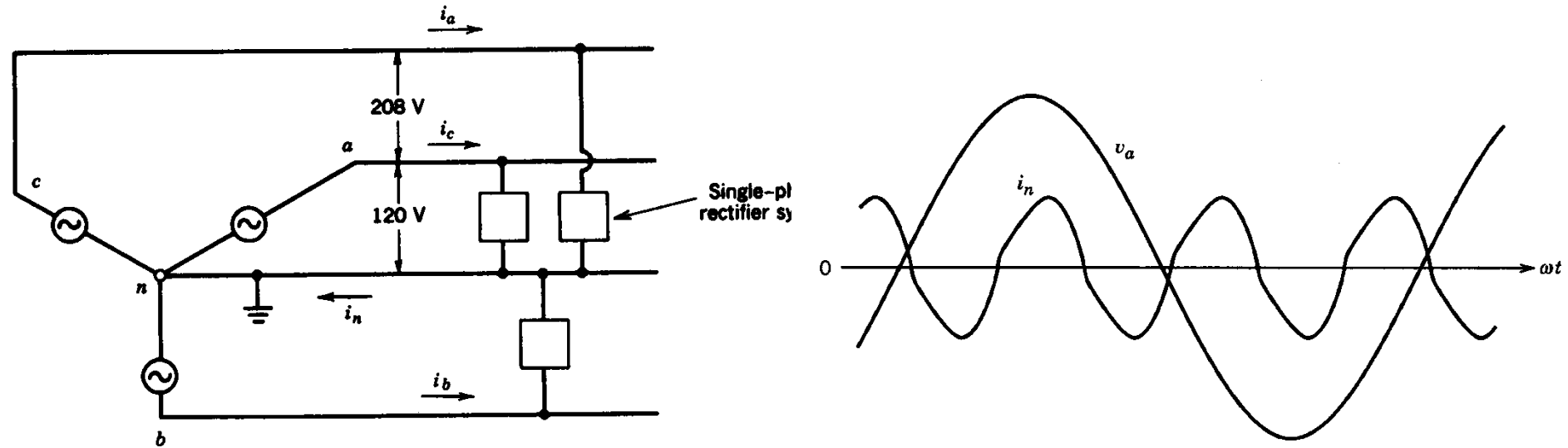


- A common neutral wire is assumed
- The current in the neutral wire is composed mainly of the third harmonic and can be higher than the phase currents

3-Phase Rectifier Circuit

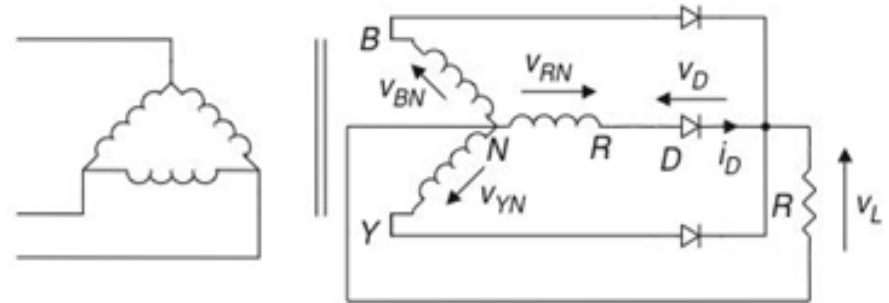
- Star Connection: direct currents in the secondary windings cause transformer core saturation problem.



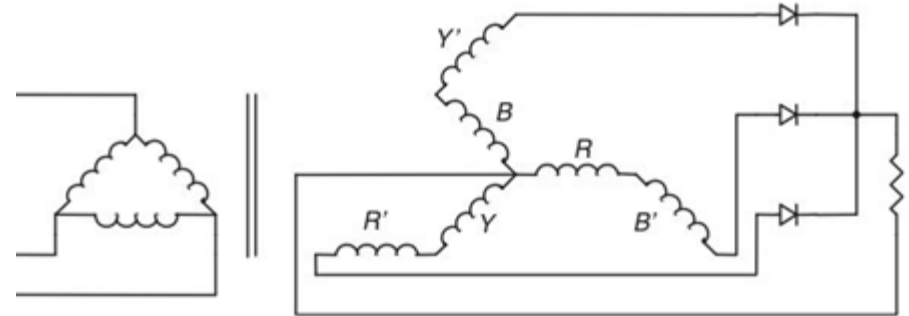- The transformer core saturation problem in the three-phase star rectifier can be avoided by zig-zag (or inter-star) connection.



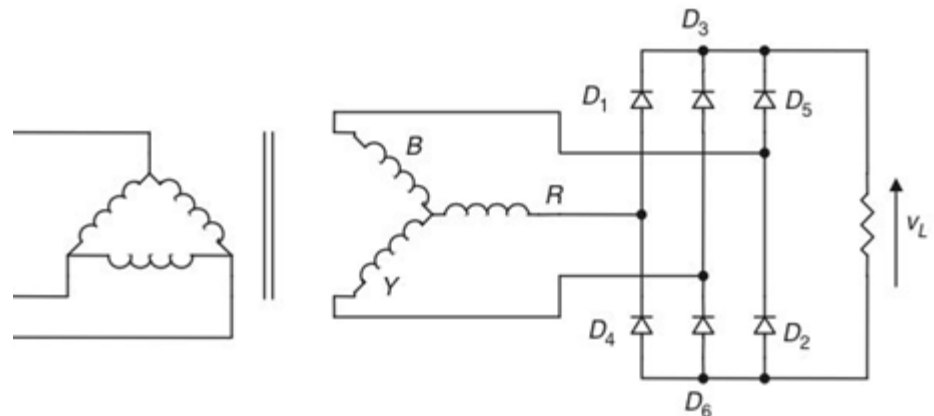- Three-phase Bridge (or 6-pulse) Rectifier – most commonly used in industry applications.



Three-Phase Bridge Rectifier with R Load


- Average value of DC-side voltage:

$$V_{do} = \frac{3}{\pi} \sqrt{3} V_m = 1.654 V_m$$

where V_m is the peak value of the phase voltage.

- RMS value of DC-side voltage:
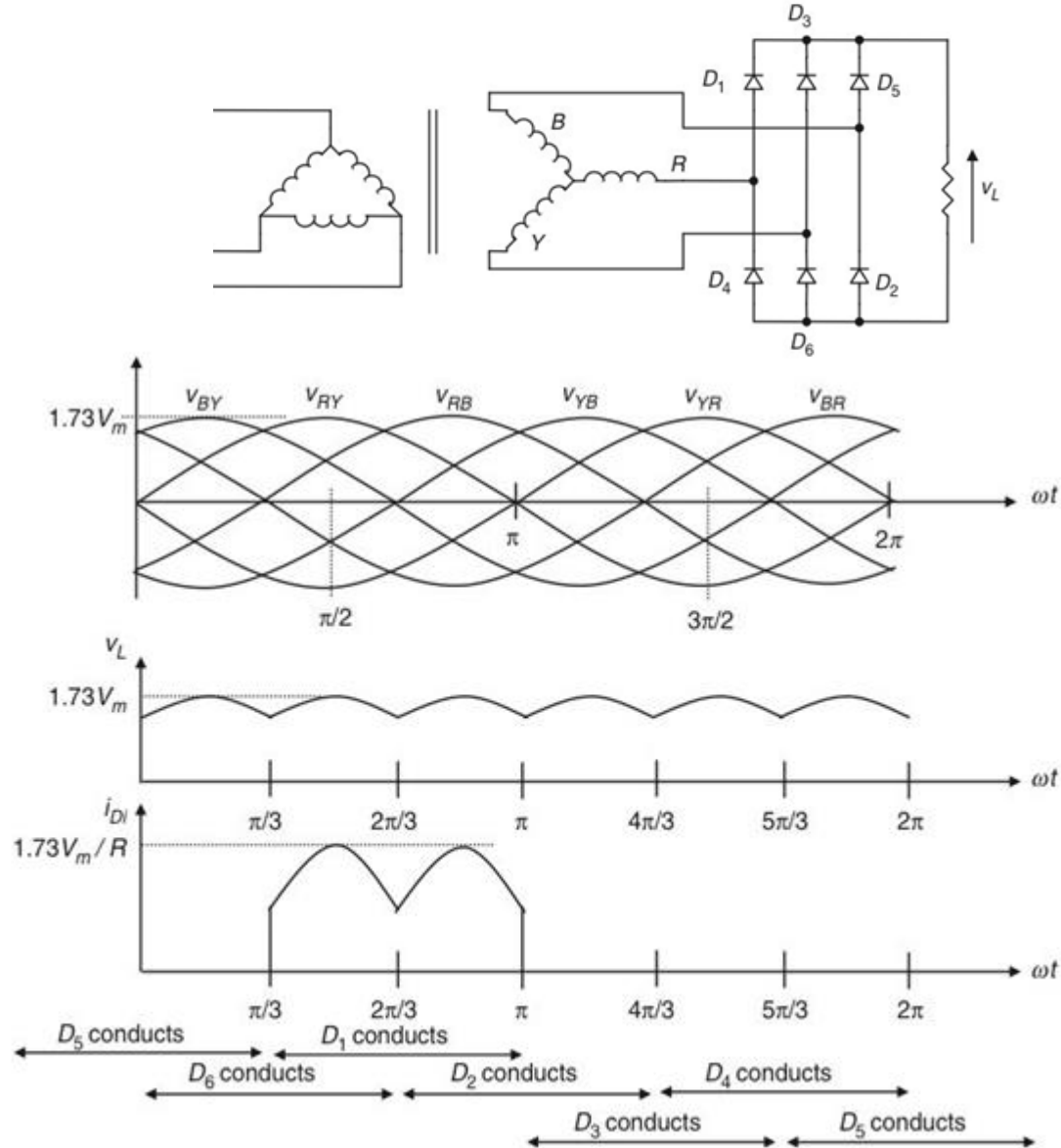
$$V_{rms} = V_m \sqrt{\frac{3}{2} + \frac{9\sqrt{3}}{4\pi}} = 1.655 V_m$$




Six-Phase Bridge Rectifier (12-Pulse)



- Average and RMS values of DC-side voltage:

$$V_{do} \approx V_{rms} \approx 1.712V_m$$


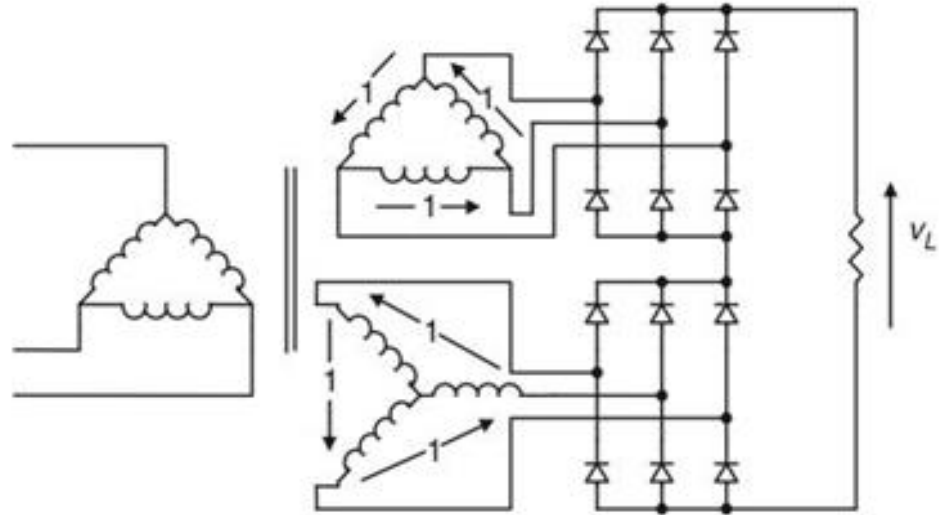
where V_m is the peak value of the phase voltage.



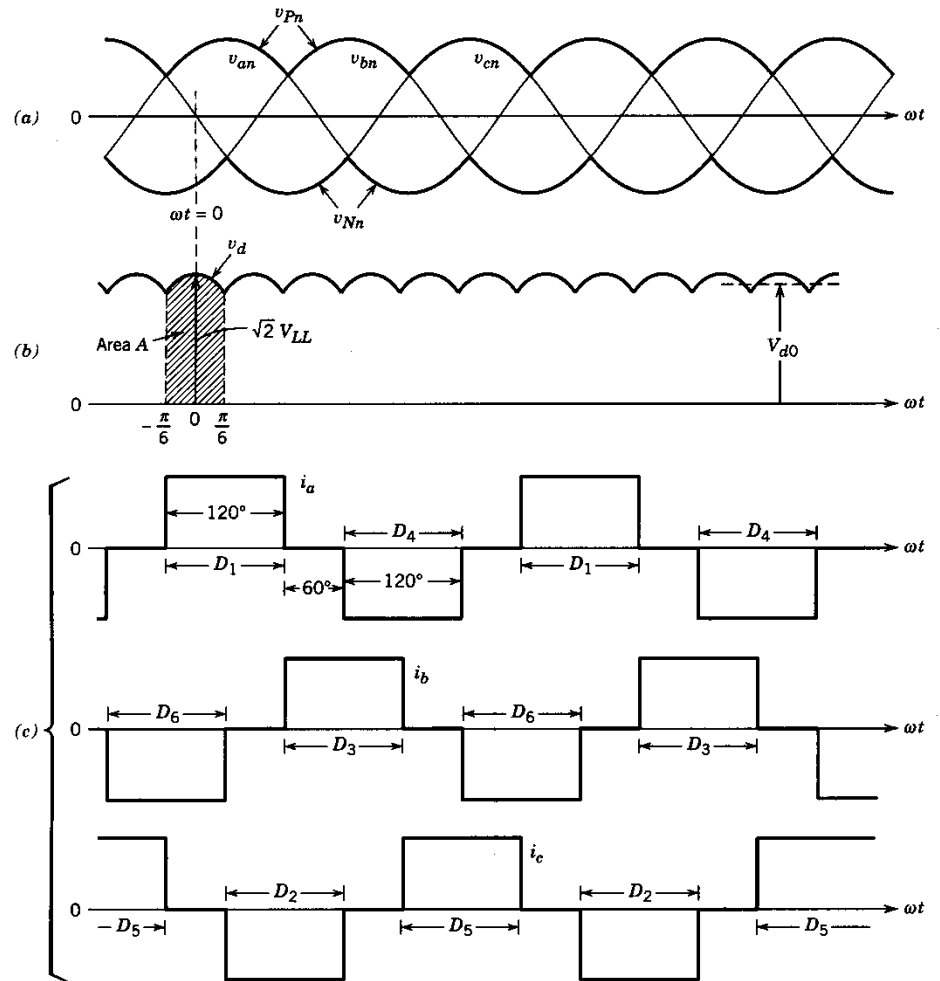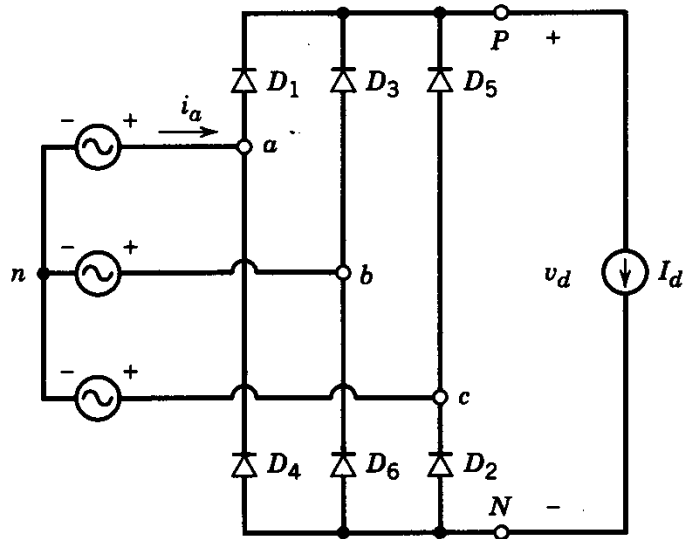Three-Phase Full-Bridge Rectifier with DC Current



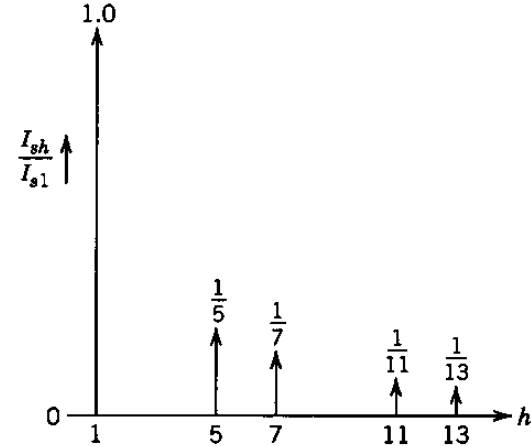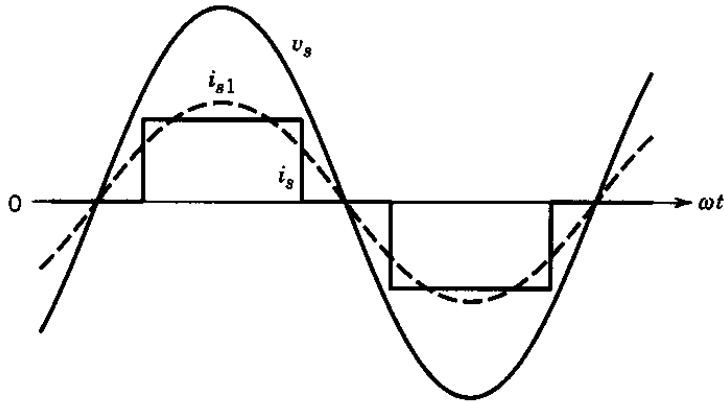Three-Phase, Full-Bridge Rectifier with DC Current



RSM value of source current

RMS value of fundamental current

RMS value of harmonic current

Current THD

Displacement Power Factor

Power Factor

$$I_s = \sqrt{2/3} I_d = 0.816 I_d$$

$$I_{s1} = (\sqrt{6} / \pi) I_d \approx 0.78 I_d$$




$$I_{sh} = I_{s1} / h, \quad h = 3, 5, 7, \dots$$

$$THD = 100[\sqrt{(\pi^2 / 9) - 1}] = 31\%$$

$$DPF = 1$$

$$PF = \frac{3}{\pi} = 0.955$$

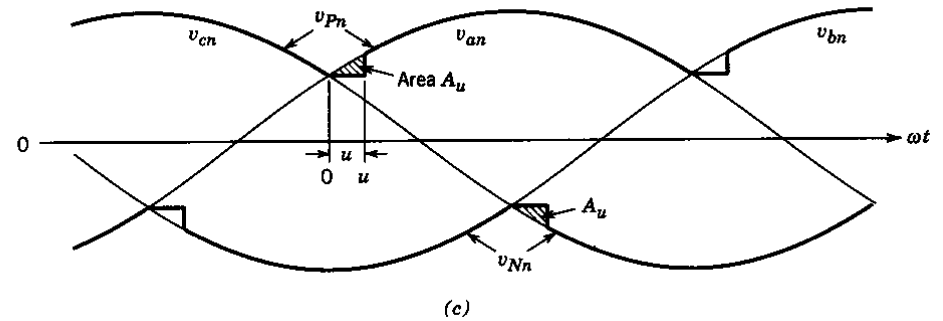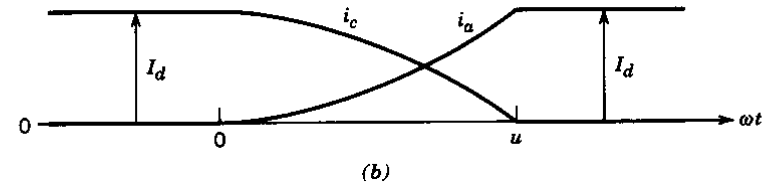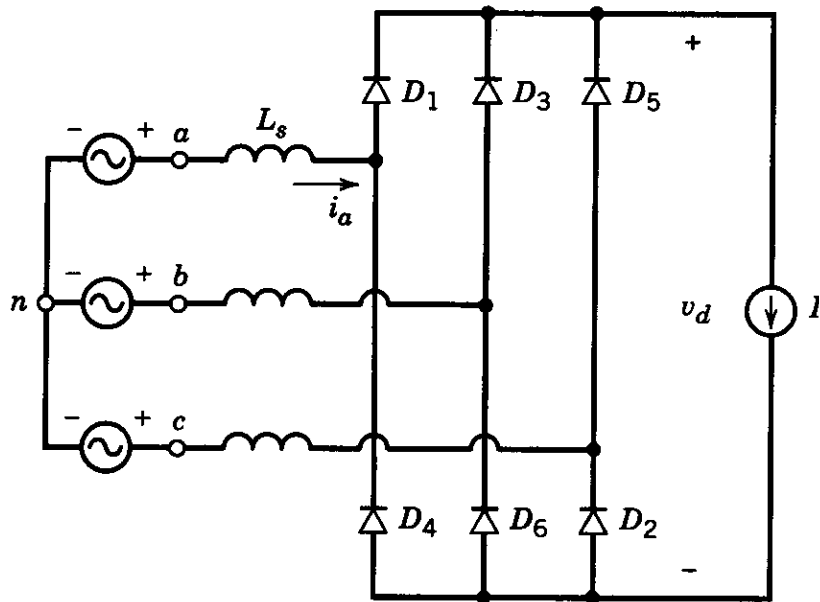3-Phase, Full-Bridge Rectifier with Inductance




Commutation angle:

$$\cos \mu = 1 - \frac{2\omega L_s I_d}{\sqrt{2}V_{LL}}$$


Average of DC-side voltage:

$$V_d = 1.35V_{LL} - \frac{3\omega L_s I_d}{\pi}$$


3-Phase Rectifier with DC Source

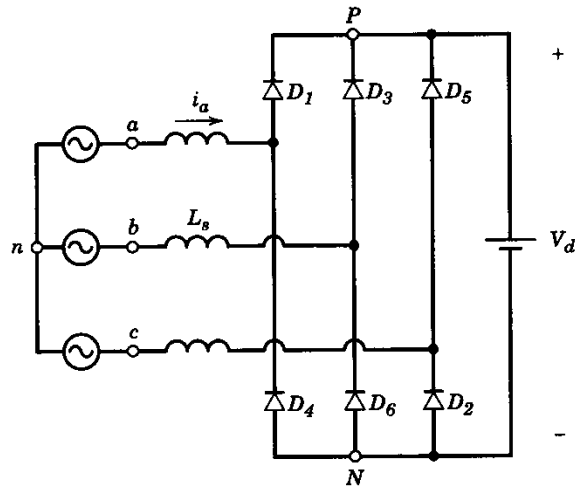

(a)


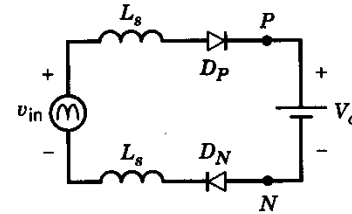


(b)

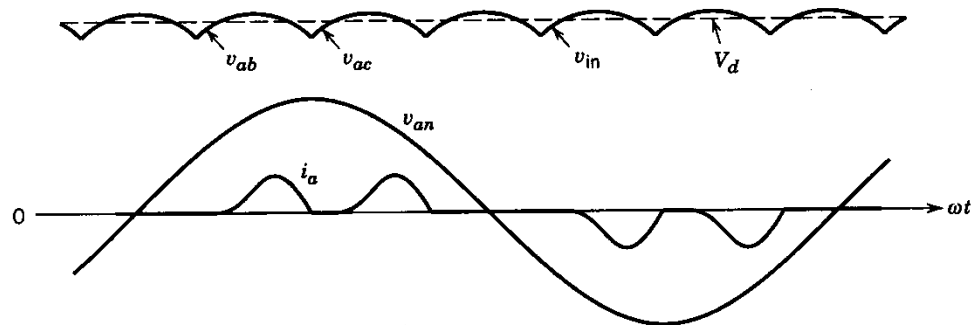


(c)

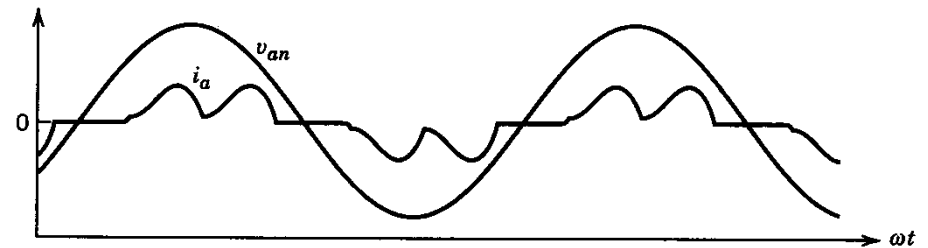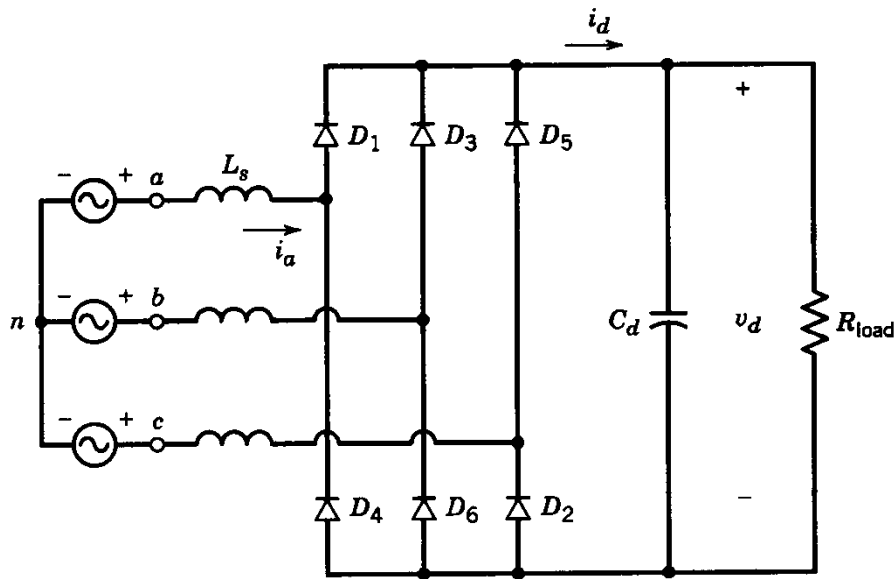Three-Phase Rectifier with Capacitor Filter



(a)

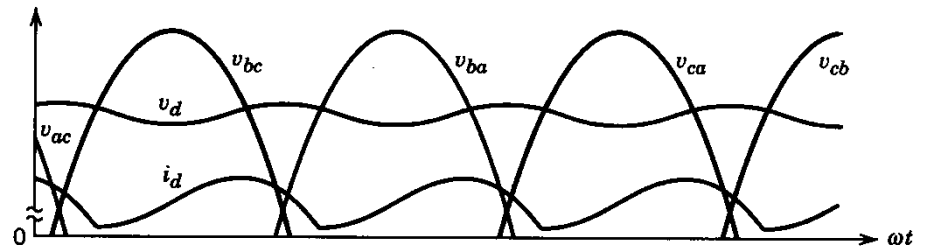

- PSpice-based analysis