# **Diode Rectifiers**

EE 442-642 Fall 2012

### Half-Bridge Rectifier Circuit: R and R-L Load







Figure 5-2 Basic rectifier with a load resistance.



Figure 5-3 Basic rectifier with an inductive load.

Current continues to flow for a while even after the input voltage has gone negative. Half Bridge Rectifier Circuit: Load with dc back-emf





- Current begins to flow when the input voltage exceeds the dc back-emf.
- Current continues to flows for a while even after the input voltage has gone below the dc back-emf.

### Full Bridge Rectifier – Simple R Load



Average value of output voltage where  $V_s$  is the RMS value of input voltage.

$$V_{do} = (2\sqrt{2} / \pi) V_s \approx 0.9 V_s$$

## Full Bridge Rectifier – Simple Constant Load Current



 $I_s = I_d$ RSM value of source current RMS value of fundamental current  $I_{s1} = (2\sqrt{2} / \pi)I_d \approx 0.9I_d$ RMS value of harmonic current Current THD **Displacement Power Factor** DPF = 1**Power Factor** 

 $I_{sh} = I_{s1} / h, \quad h = 3, 5, 7, \dots$  $THD = 100[\sqrt{(\pi^2/8)} - 1] = 48.43\%$ PF = 0.95-5

#### Diode-Rectifier Bridge with AC-Side Inductance



Commutation angle:

$$\cos\mu = 1 - \frac{2\omega L_s I_d}{\sqrt{2}V_s}$$

Average of DC-side voltage:

$$V_d = 0.9V_s - \frac{2\omega L_s I_d}{\pi}$$

## Full Bridge Rectifier with dc-side Voltage



Figure 5-16 (a) Rectifier with a constant dc-side voltage. (b) Equivalent circuit. (c) Waveforms.

#### **Diode-Rectifier with a Capacitor Filter**



Figure 5-20 Practical diode-bridge rectifier with a filter capacitor.



Figure 5-23 Waveforms in the circuit of Fig. 5-20, obtained in Example 5-2.

## Voltage Distortion at PCC



Figure 5-25 Line-voltage notching and distortion.

Figure 5-26 Voltage waveform at the point of common coupling in the circuit of Fig. 5-25.

- PCC is the point of common coupling
- Distorted current flow results in distorted voltage

## **Dual Voltage Rectifier**



Figure 5-27 Voltage-doubler rectifier.

• In 115-V position, one capacitor at-a-time is charged from the input.

#### Three-Phase, Four-Wire System



Figure 5-28 Three-phase, four-wire system.

Figure 5-29 Neutral-wire current  $i_n$ .

- A common neutral wire is assumed
- The current in the neutral wire is composed mainly of the third harmonic and can be higher than the phase currents

## Three-Phase, Full-Bridge Rectifier



Average value of DC-side voltage:

$$V_{do} = \frac{3}{\pi} \sqrt{2} V_{LL} = 1.35 V_{LL}$$

where  $V_{\text{LL}}$  is the rms value of the Line voltage



Figure 5-32 Waveforms in the circuit of Fig. 5-31.

#### Three-Phase, Full-Bridge Rectifier





RSM value of source current RMS value of fundamental current RMS value of harmonic current Current THD Displacement Power Factor Power Factor

 $I_{s} = \sqrt{2/3}I_{d} = 0.816I_{d}$   $I_{s1} = (\sqrt{6} / \pi)I_{d} \approx 0.78I_{d}$   $I_{sh} = I_{s1} / h, \quad h = 3,5,7,...$   $THD = 100[\sqrt{(\pi^{2} / 9) - 1}] = 31\%$  DPF = 1  $PF = \frac{3}{\pi} = 0.955$ 

#### 3-Phase, Full-Bridge Rectifier with ac-side inductance







Commutation angle:

$$\cos\mu = 1 - \frac{2\omega L_s I_d}{\sqrt{2}V_{LL}}$$

Average of DC-side voltage: V

$$V_d = 1.35 V_{LL} - \frac{3\omega L_s I_d}{\pi}$$

#### 3-Phase Rectifier with DC Source



**Figure 5-36** (a) Three-phase rectifier with a finite  $L_s$  and a constant dc voltage. (b) Equivalent circuit. (c) Waveforms.

## **Three-Phase Rectifier with Capacitor Filter**



Figure 5-30 Three-phase, full-bridge rectifier.

Figure 5-39 Waveforms in the rectifier of Fig. 5-30, obtained in Example 5-7.

PSpice-based analysis

## Inrush Current and Over-voltage at Turn ON

- Theroretical maximum voltage across the capacitor occurs when the capacitor is initially discharged and the AC input is switched at its peak:
  - twice the peak phase voltage (in 1-phase ckts),
  - twice the peak line voltage (in 3-phase ckts).
- Overvoltages and inrush currents that follow may be damaging to capacitors and diodes.
- Possible solution: Use current limiting resistor on the DC side between the rectifier output and filter capacitor. The resistor should be shorted out after few cycles to limit losses.