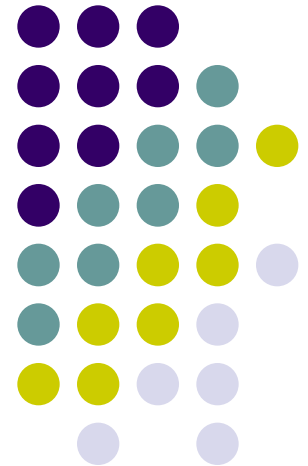



Review of 3-Phase AC Circuits

EE 340

Y. Baghzouz




Advantages of 3-Phase Systems

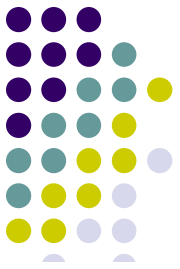






- Can transmit more power for same amount of wire (twice as much as single phase)
- Torque produced by 3ϕ machines is constant
- Three phase machines use less material for same power rating
- Three phase machines start more easily than single phase machines

Balanced 3-Phase Systems



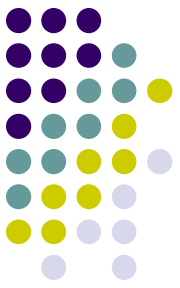


- A balanced 3 phase (ϕ) system has
 - three voltage sources with equal magnitude, but with an angle shift of 120°
 - equal loads on each phase
 - equal impedance on the lines connecting the generators to the loads
- Bulk power systems are almost exclusively 3ϕ
- Single phase is used primarily only in low voltage, low power settings, such as residential and some commercial



3-Phase Voltage Source

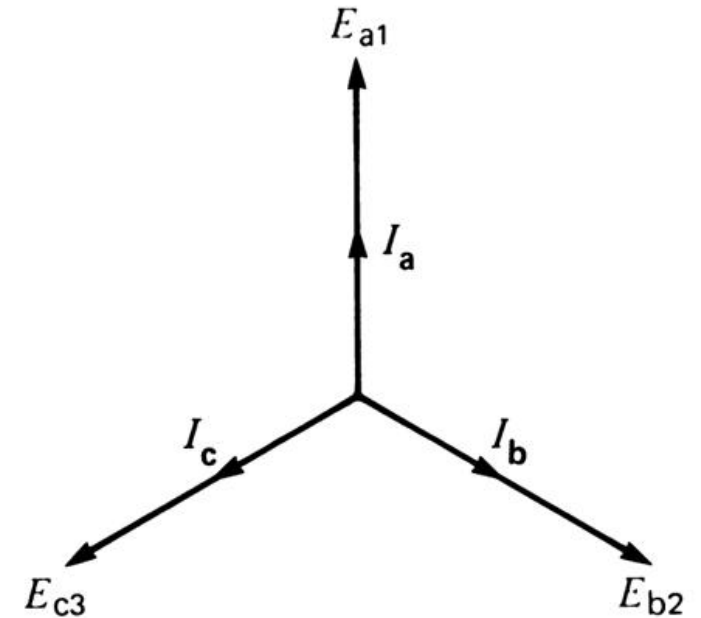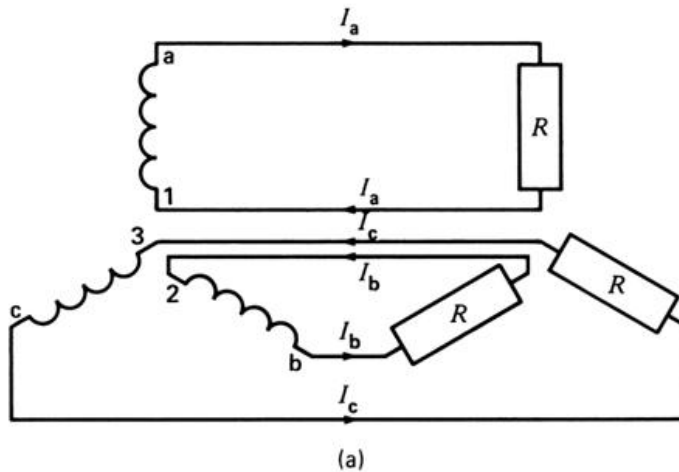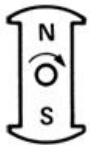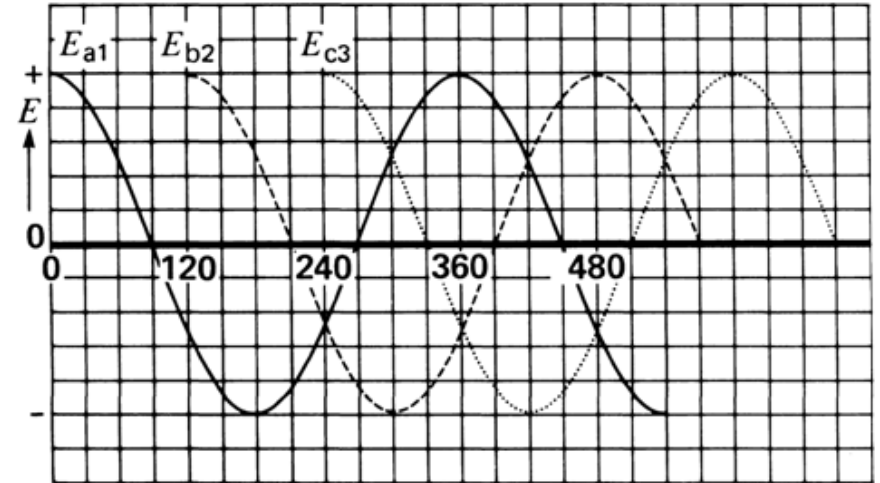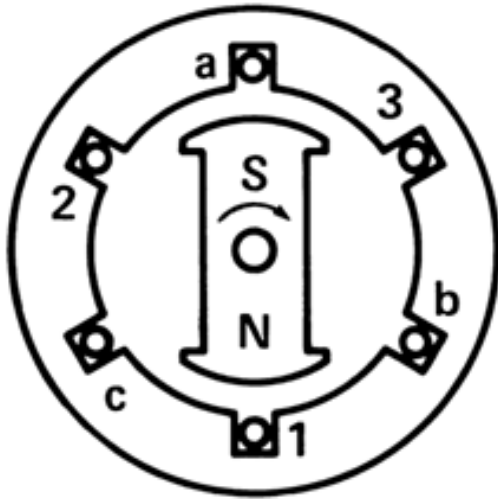

Neutral Wire Sharing

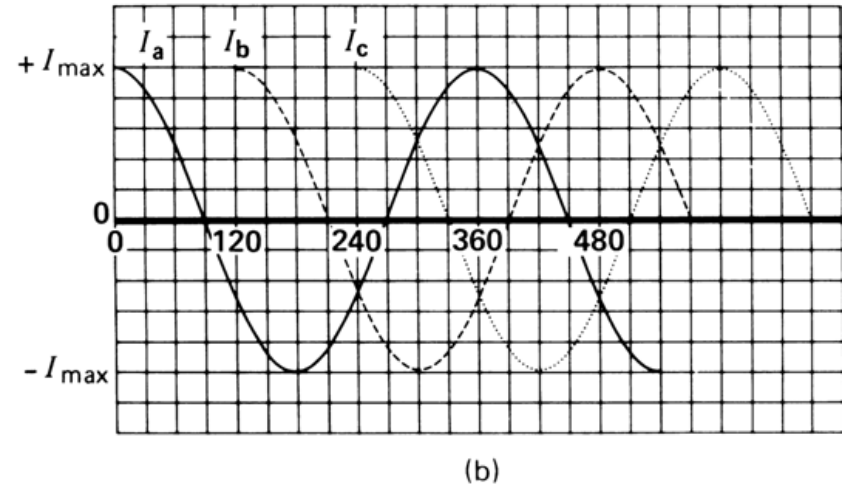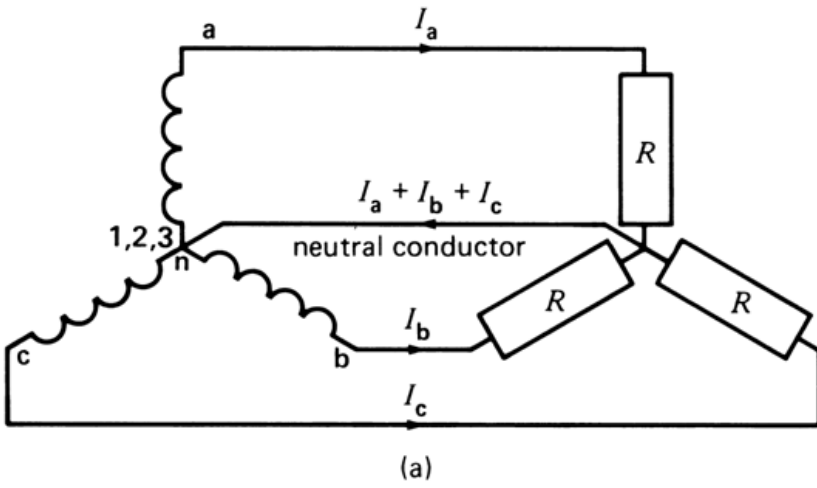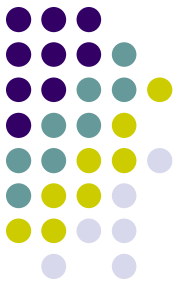

Neutral Current

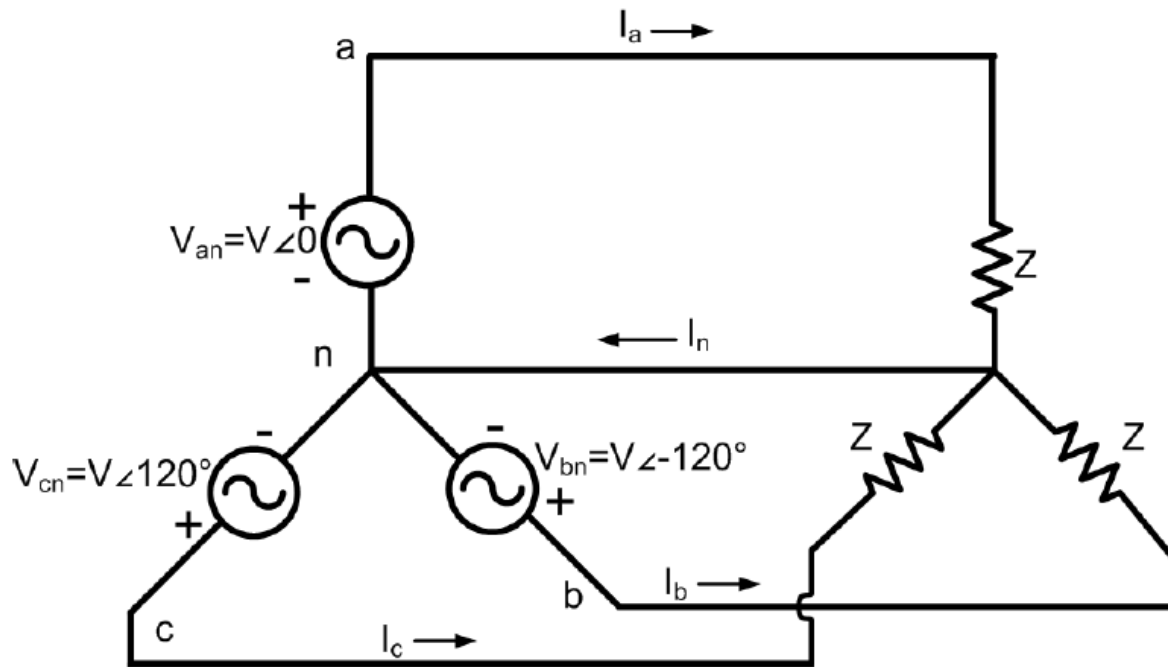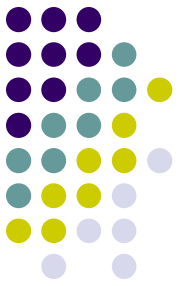


$$I_n = I_a + I_b + I_c$$

$$I_n = \frac{V}{Z} (1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle 120^\circ) = 0$$



Phase and Line Voltages

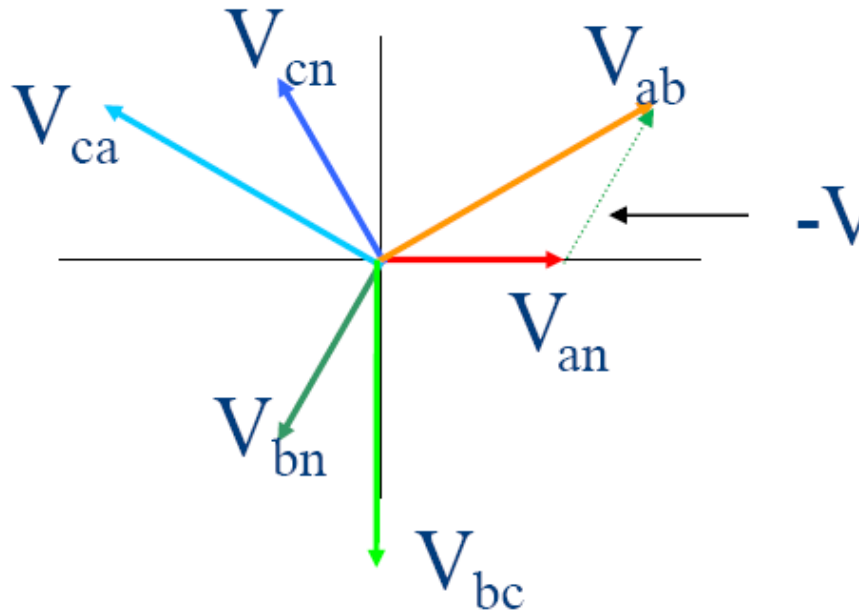

$$V_{an} = |V| \angle \alpha^\circ$$

$$V_{bn} = |V| \angle \alpha^\circ - 120^\circ$$

$$V_{cn} = |V| \angle \alpha^\circ + 120^\circ$$

($\alpha = 0$ in this case)

$$V_{ab} = V_{an} - V_{bn} = |V|(1 \angle \alpha - 1 \angle \alpha + 120^\circ)$$



$$= \sqrt{3} |V| \angle \alpha + 30^\circ$$

$$V_{bc} = \sqrt{3} |V| \angle \alpha - 90^\circ$$



$$V_{ca} = \sqrt{3} |V| \angle \alpha + 150^\circ$$

Line to line
voltages are
also balanced

Y-Connected Load

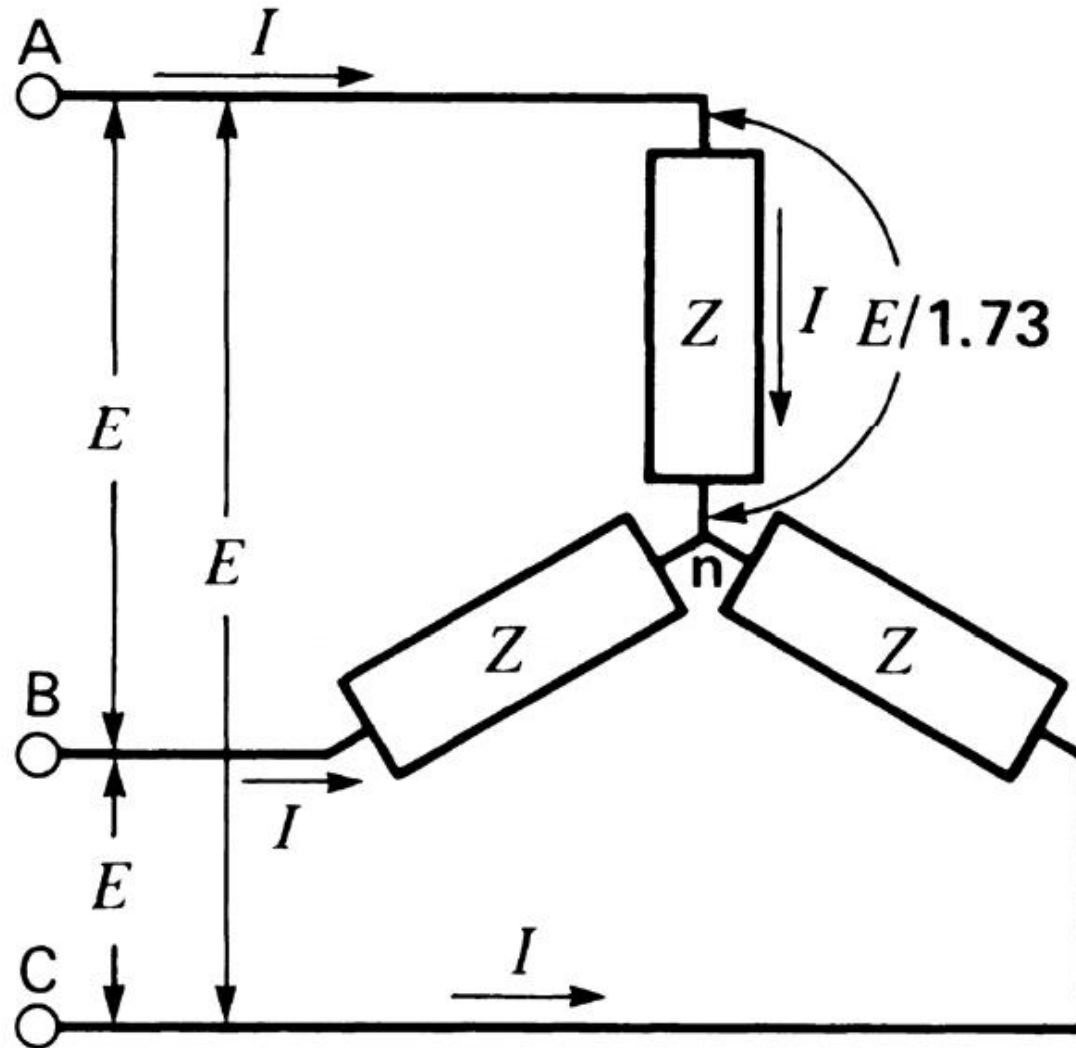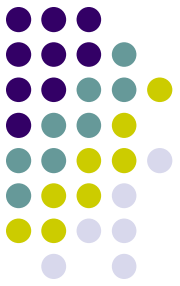

Δ -Connected Load

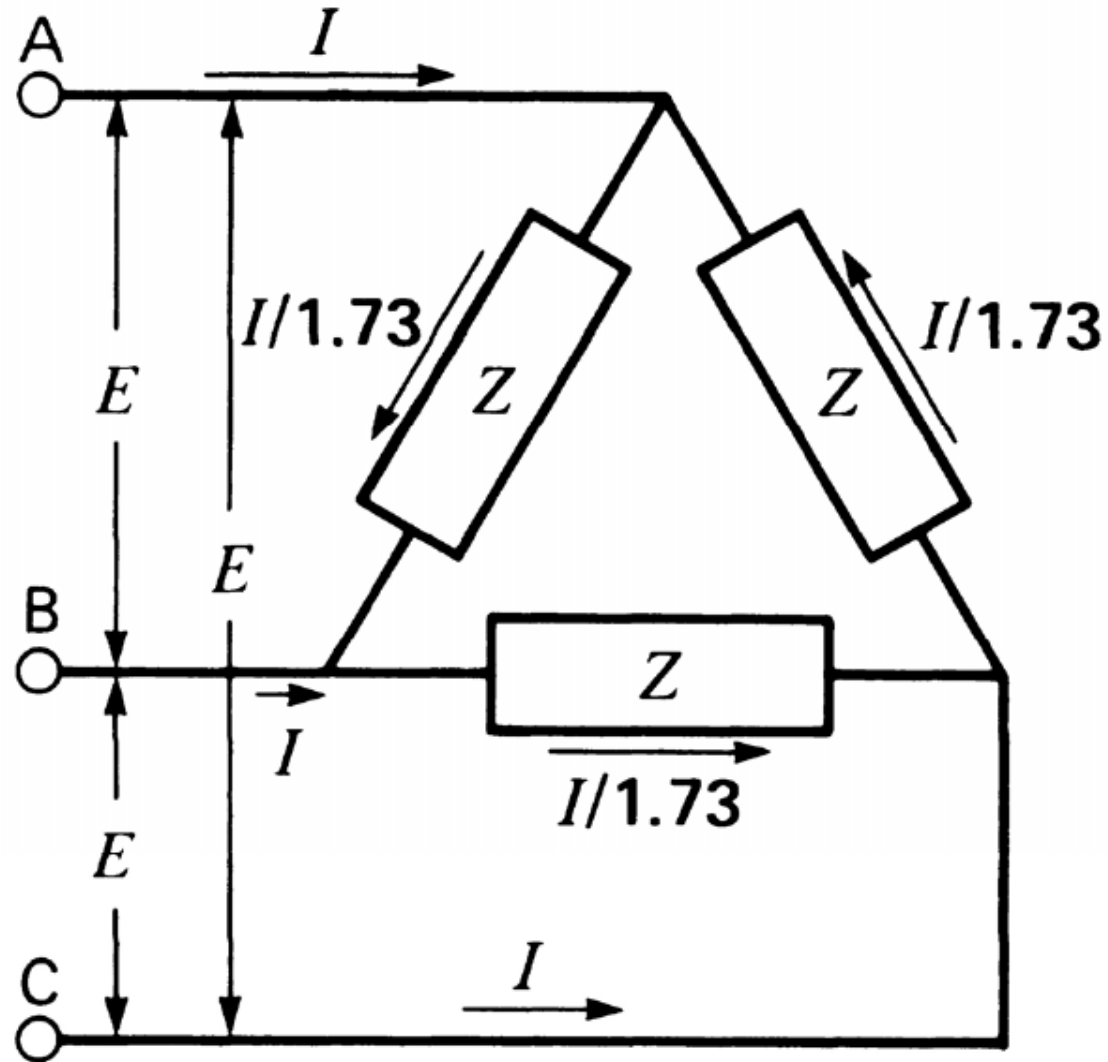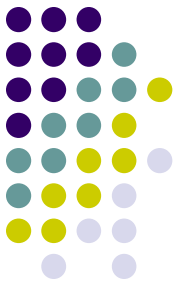

Power in Balanced 3-Phase Circuits



- The real power, reactive power, apparent power, complex power and power factor are the same in each phase.

$$P = 3V_p I \cos(\theta) = \sqrt{3}V_L I \cos(\theta)$$


$$Q = 3V_p I \sin(\theta) = \sqrt{3}V_L I \sin(\theta)$$

$$S = 3V_p I = \sqrt{3}V_L I$$


Power measurement in 3-phase 4-wire circuit



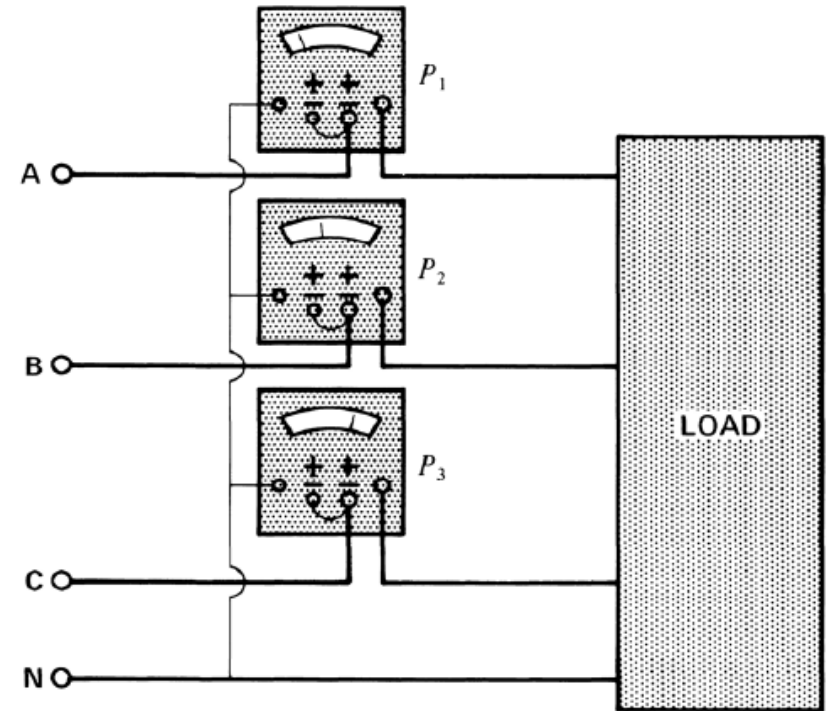
- If the load is balanced, then $P_1 = P_2 = P_3$, hence, $P_T = 3P_1$
- If the load is unbalanced, $P_1 \neq P_2 \neq P_3$, hence, $P_T = P_1 + P_2 + P_3$




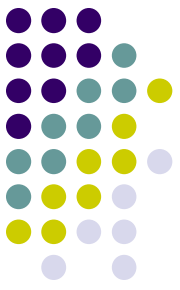
Power measurement in 3-phase 3-wire circuit: the 2-wattmeter method



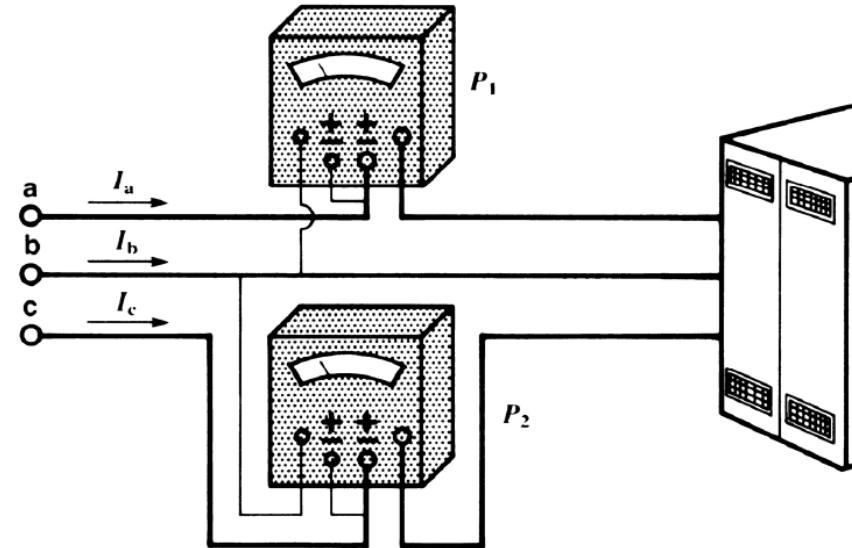
- $P_T = P_1 + P_2$
- The load can be Y-connected, Δ -connected, balanced, or unbalanced.
- Any one of the 3 phases can be used as a reference.
- If the load is balanced, then $P_1 = P_2$, hence, $P_T = 2P_1$



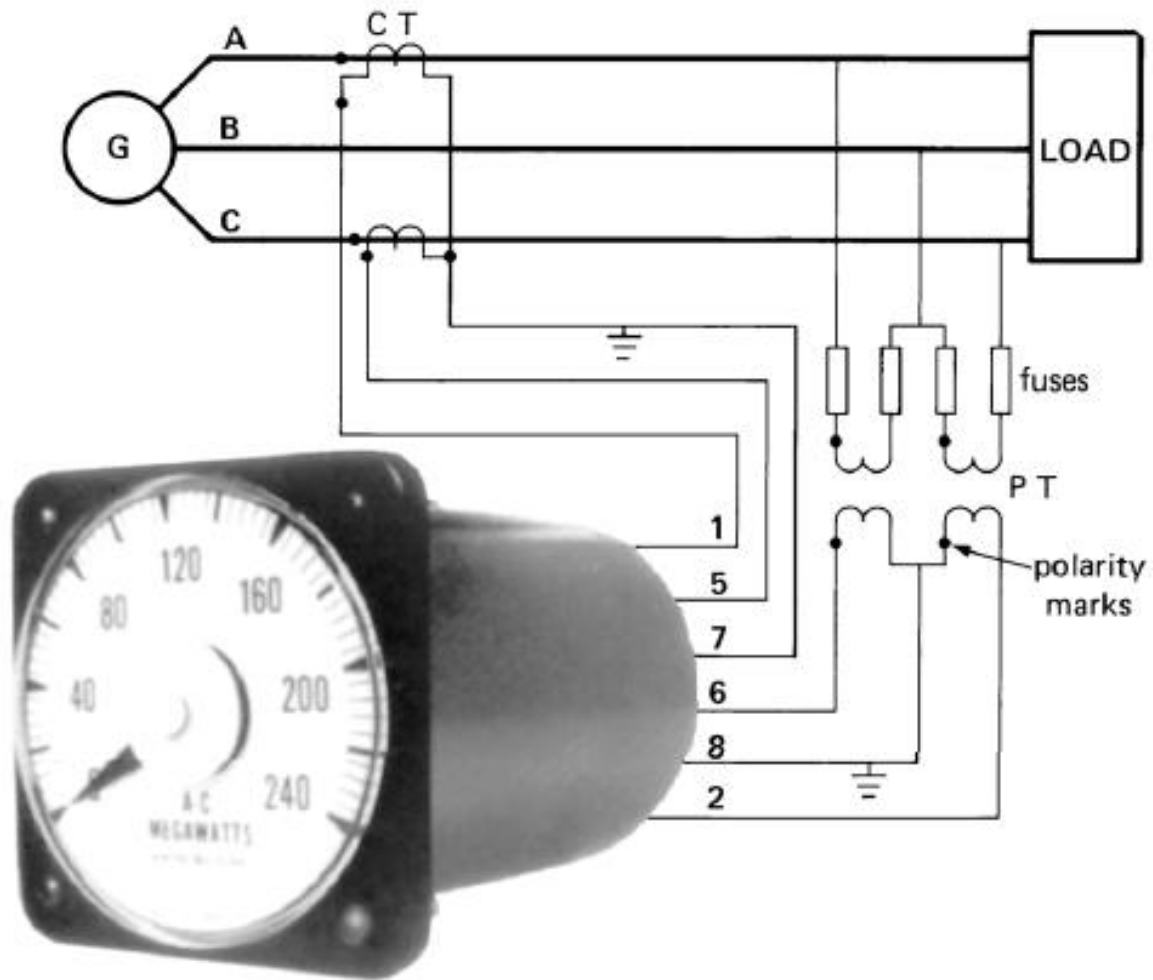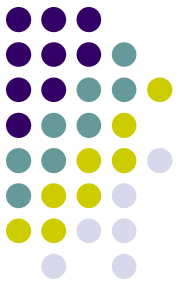Measuring active power in a high power circuit




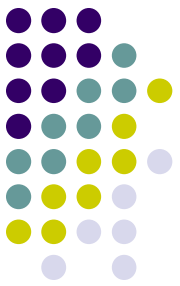Per-Phase Analysis in Balanced 3-Phase Circuits




- Per phase analysis allows analysis of balanced 3ϕ systems with the same effort as for a single phase system
- **To do per phase analysis**
 1. Convert all 3ϕ load/sources to equivalent Y's
 2. Solve phase "a" independent of the other phases
 3. Total system power $S = 3 V_a I_a^*$
 4. If desired, phase "b" and "c" values can be determined by inspection (i.e., $\pm 120^\circ$ degree phase shifts)
 5. If necessary, go back to original circuit to determine line-line values or internal 3ϕ values.



Example of per-phase analysis

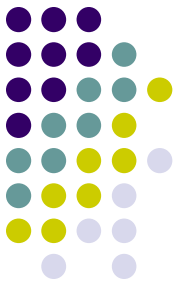

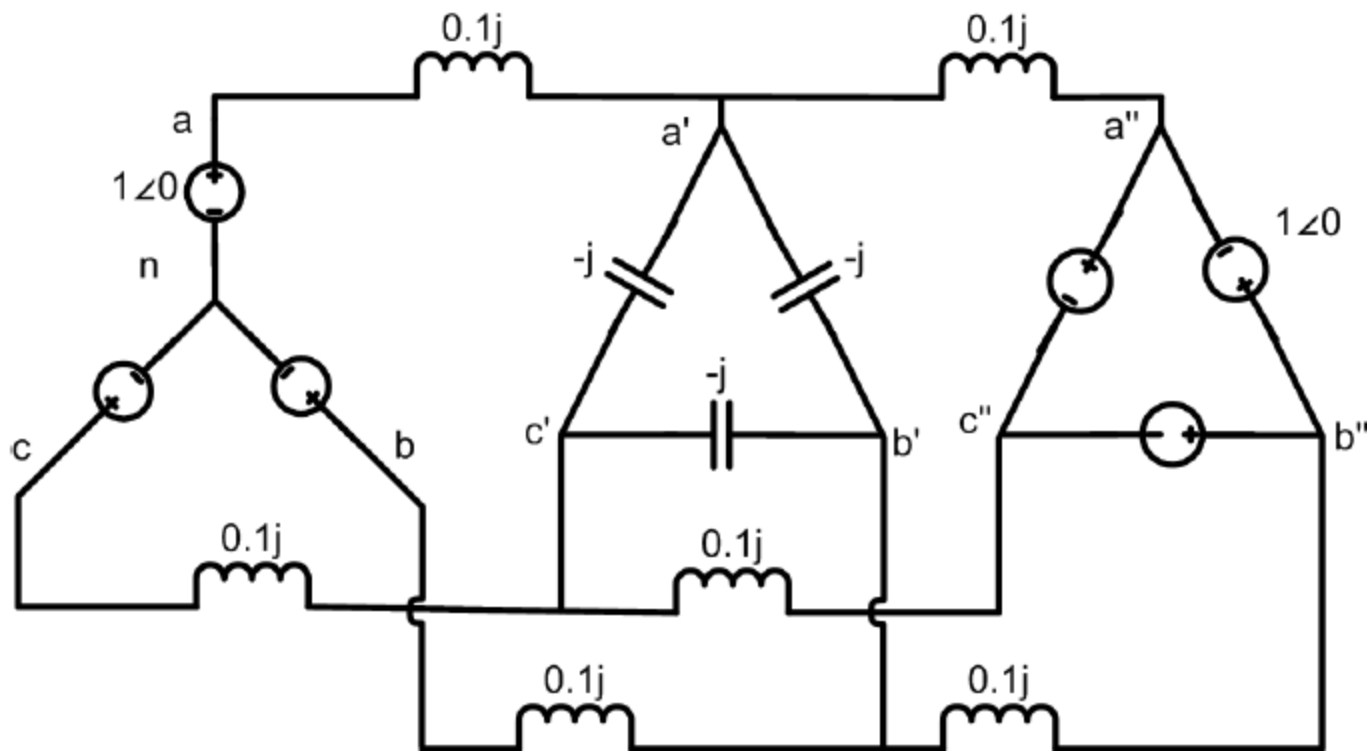- Find the complex power supplied by each of the two sources.



Solution

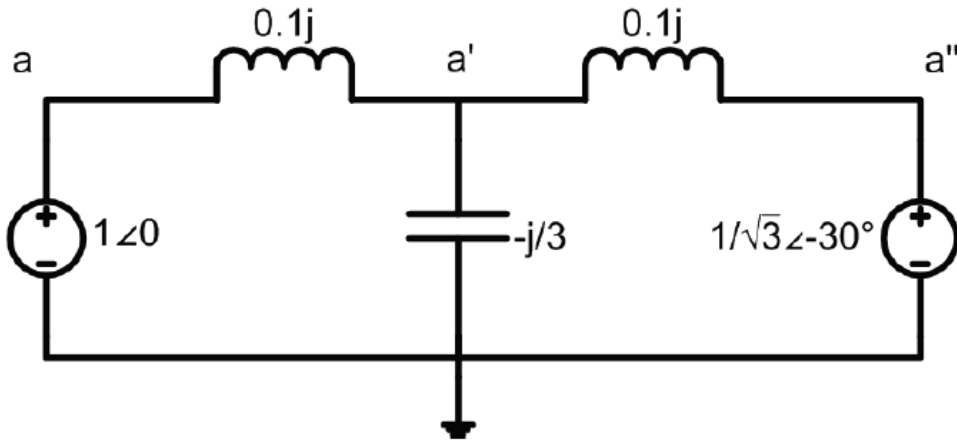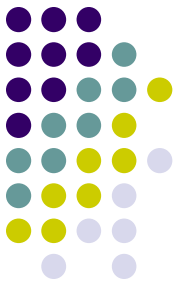

To solve the circuit, write the KCL equation at a'

$$(V'_a - 1\angle 0^\circ)(-10j) + V'_a(3j) + (V'_a - \frac{1}{\sqrt{3}}\angle -30^\circ)(-10j) = 0$$

$$(10j + \frac{10}{\sqrt{3}}\angle 60^\circ) = V'_a(10j - 3j + 10j)$$





$$V'_a = 0.9\angle -10.9^\circ \text{ volts} \quad V'_b = 0.9\angle -130.9^\circ \text{ volts}$$

$$V'_c = 0.9\angle 109.1^\circ \text{ volts} \quad V'_{ab} = 1.56\angle 19.1^\circ \text{ volts}$$

$$S_{Y_{gen}} = 3V_a I_a^* = V_a \left(\frac{V_a - V'_a}{j0.1} \right)^* = 5.1 + j3.5 \text{ VA}$$

$$S_{\Delta_{gen}} = 3V''_a \left(\frac{V''_a - V'_a}{j0.1} \right)^* = -5.1 - j4.7 \text{ VA}$$

Example of 3-phase balanced circuit

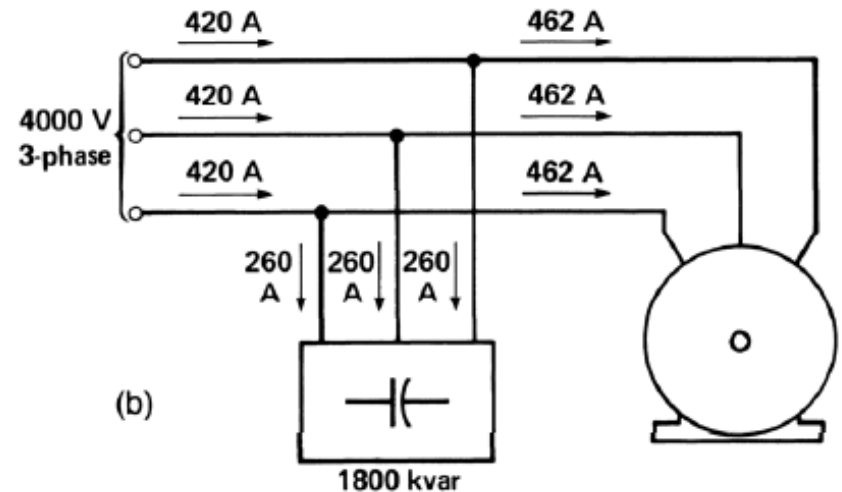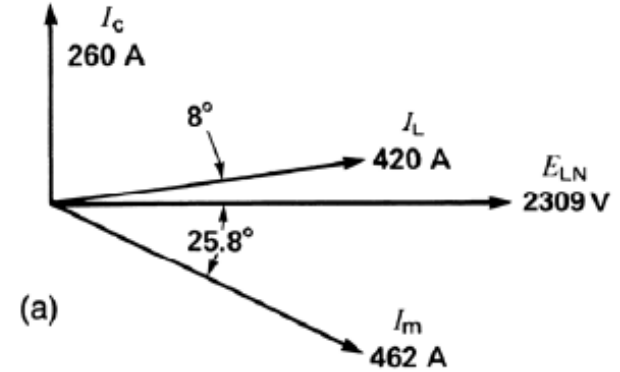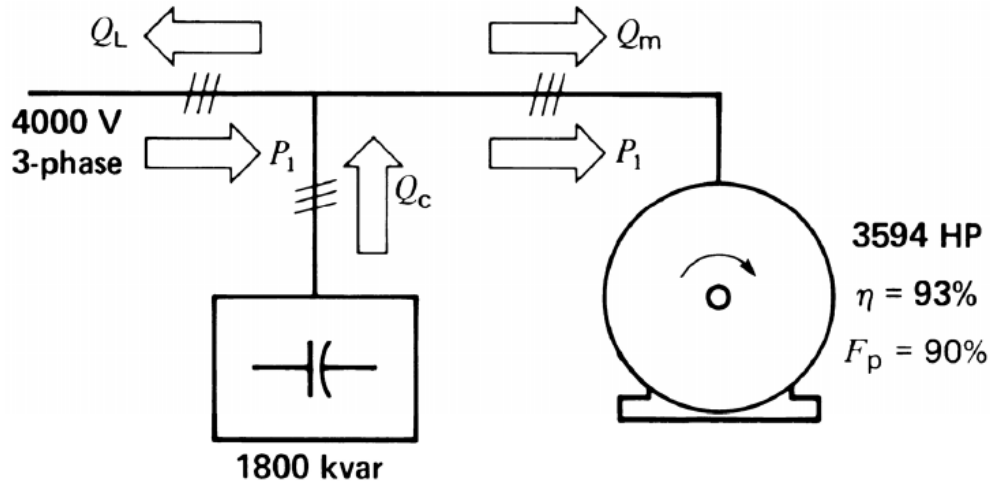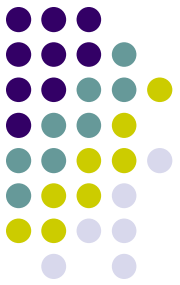

Problems from Chap 2:

1, 2, 3, 4, 5, 6.

