

# EE 340L

## EXPERIMENT # 7

### 3-PHASE INDUCTION MOTORS

#### 1. Equivalent Circuit Parameters

##### 1.1 No-Load Test

Connect the three-phase induction motor to a 3-phase power supply. The stator windings **in Wye-connection** and the shaft should be disconnected from other machines.

Turn on the 3-phase 120/208V supply. Then record the supply voltage, current, active and reactive powers and rotor speed. Turn off the supply after taking all the measurements.

##### 1.2 Locked-Rotor Test

Replace the fixed 3-Phase AC source by a **variable** 3-phase AC source. **Turn the control knob to minimum (zero) voltage.** Block the shaft manually, turn on the variable source, increase the supply voltage slowly until the current of the motor reaches 2 A. Record the voltage, current, active and reactive powers. Then decrease the supply voltage back to zero before releasing the shaft.

##### 1.3 DC Test


Connect a variable DC source across two terminals of the induction motor. Start with 0 Volts. Increase the DC supply voltage until a current of 1 A is reached. Record the voltage and current. Then shut down the power supply. You may also use an Ohm meter to measure the stator winding resistance.

#### **2. Torque-Speed Characteristics**

1. Connect the shafts of the induction motor to that of a dynamometer. Start the motor using 120/208 V three phase supply, then record the shaft speed, current, real and reactive power drawn by the motor.
2. Increase the torque on the shaft from 0 to 1.4 Nm in increments of 0.2 Nm , and record the above measurements for each load torque.

## QUESTIONS:

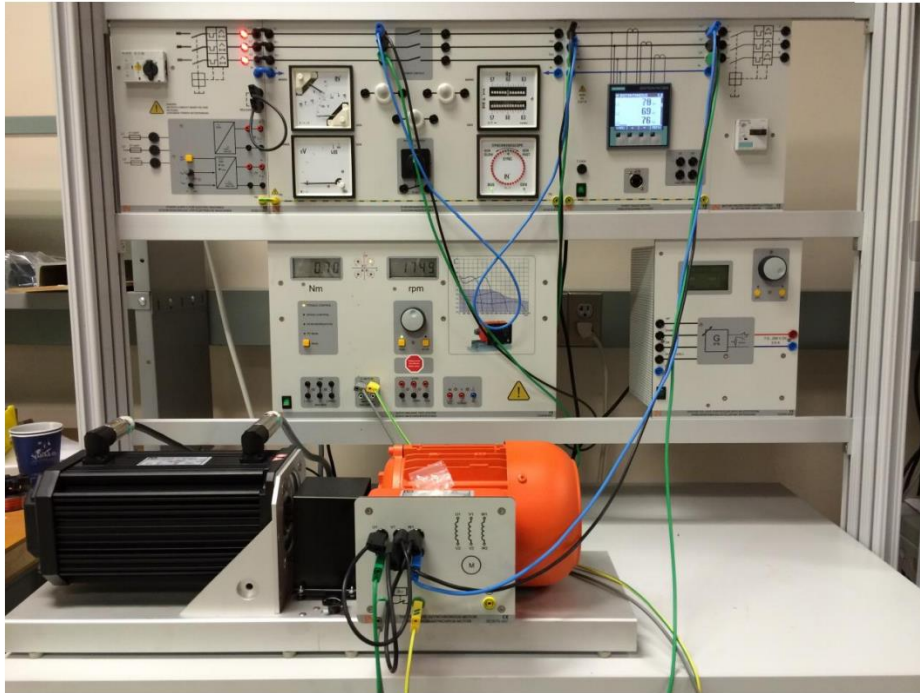1. Use the measurements under no-load, locked-rotor and DC test to compute  $R_1$ ,  $R_2$ ,  $X_1$ ,  $X_2$ , and  $X_m$ . Note that  $X_1 \approx X_2$  for this particular induction machine.
2. Plot the following
  - a. Torque versus speed.
  - b. Motor power factor versus speed.
  - c. Active and reactive power versus speed.



Experimental Data:

### **DC Test:**

Voltage (across two phases): .....V

Current: ..... A

### **Locked Rotor Test:**

Line current: .....A

Phase Voltage: .....V

Real Power (per phase): .....W

Reactive Power (per phase): .....VAR

### **No Load Test:**

Rotor Speed: .....rpm

Phase voltage: .....V

Line current: ..... A

Real Power (per phase): .....W

**Test under Load (supply volage per phase: 120 V)**

Load Torque (Nm)	Rotor Speed (RPM)	Stator Current (A)	Real Power per Phase (W)	Reactive Power per Phase (VAR)
0				
.2				
.4				
.6				
.8				
1.0				
1.2				
1.4				